 


Sequential Logic Circuits

REGISTERS and RAM (Memory)



Combinational Logic Circuits

- The logic circuits [adders, decoders, encoders and multiplexers ...] that we used or designed **up to now** are referred as “**combinational logic circuits**”
- In the combinational logic, time is not involved
- Output = f (current inputs)

Logic circuits with **no** memory = Memoryless

Memory

- In computer systems, memory is also a major component.
- The need to store prior information (data) is a must ...
- Computers store data in a variety of memories (RAM, Flash, ROM,)
- Logic circuits that store data dynamically are referred as “Sequential Logic Circuits”.

Sequential Logic Circuits

- Time is involved ...
- The output(s) depends on **past** as well as **present inputs**.
- Output = f (current inputs, past inputs, past outputs)
- The output(s) are known as **states**.

Logic circuits **with** memory

Sequential Logic Circuits

- The basic component of a sequential logic circuit is a logic device that is referred as **Latch/ Flip-Flop**
- Latches and Flip-Flops store a single bit of data until the stored value is overwritten.

Latches, Flip Flops

- Latch: [level sensitive storage element]
- Flip-Flop: [edge triggered storage element]

Types of Latches:

- S-R latch, J-K latch, D latch (= gated D latch)


Types of Flip-Flops (FF):

- D-FF, D-FF with enable, Scan-FF, JK-FF, T-FF.

D-Flip Flop (D-FF)

- A logic device that stores one bit of binary data.
- The value of the stored bit is “**Flipped**” back and forth between the two binary states (1 and 0).
- Note that the **D** type Flip-Flop is the easiest basic sequential device that can be “understood” and used in design.
- **D** = **D**ata of **D**elay

D-FF (Truth Table)

 

D	Q	State
0	0	reset
1	1	set




$$Q = D$$

D = Input

Q = Output

E = Enable or Clock (CLK)


Inside a D-FF ...

   

Flip Flops are “Tools”

- The Flip-Flops are the “Tools” to (understand) design ...
 - Registers
 - Digital (Binary) Counters
 - RAM

Registers

 


MIPS

Register Number	Mnemonic Name
\$0	zero
\$1	\$at
\$2, \$3	\$v0, \$v1
\$4-\$7	\$a0-\$a3
\$8-\$15	\$t0-\$t7
\$16-\$23	\$s0-\$s7

Register

Dynamic logic elements capable of storing an array of bits.

6-bit Register

 


32-bit Register

101011	10011	01000	0000 0000 0011 0100
--------	-------	-------	---------------------

Memory system

Dynamic logic elements of storing a matrix of bits.

36-bit Memory

 

Register

- A temporary storage logic component
- It is completely transparent to user, and even to programmer (except Assembly Language)
- A n-bit register is capable of storing n-bit numbers in the range:

1	1	1	...	1	1
---	---	---	-----	---	---

 High

0	0	0	...	0	0
---	---	---	-----	---	---

 Low

Therefore

Latch (Flip-Flop): Can store **a single bit**

Register: Can store an **array of bits**

Memory: Can store a **matrix of bits**

Registers: RISC-V CPUs

Register	ABI Name	Description	Saver
x0	zero	Hard-wired zero	—
x1	ra	Return address	Caller
x2	sp	Stack pointer	Callee
x3	gp	Global pointer	—
x4	tp	Thread pointer	—
x5–7	t0–2	Temporaries	Caller
x8	s0/fp	Saved register/frame pointer	Callee
x9	s1	Saved register	Callee
x10–11	a0–1	Function arguments/return values	Caller
x12–17	a2–7	Function arguments	Caller
x18–27	s2–11	Saved registers	Callee
x28–31	t3–6	Temporaries	Caller
f0–7	ft0–7	FP temporaries	Caller
f8–9	fs0–1	FP saved registers	Callee
f10–11	fa0–1	FP arguments/return values	Caller
f12–17	fa2–7	FP arguments	Caller
f18–27	fs2–11	FP saved registers	Callee
f28–31	ft8–11	FP temporaries	Caller

Types of Registers

- Processor registers
- Data registers
- Address registers
- Conditional registers
- Special registers
- Control and status registers (PC & IR)
- Floating point registers
-
- Shift registers.


Shift Register

- A register that its contents are shifted ...
- How?



4-bit Register

Shift right and left (4-bit register)


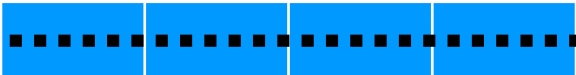
Data In  Data Out

Serial-in/Shift Right/Serial-out


Data Out  Data In

Serial-in/Shift Left/Serial-out


Parallel/Serial (4-bit register)

  

 
Buffer (Data Parallel-in/ Data Parallel-out)



Data movement

 

Rotation-right

 


Rotation-left

Registers (Examples)

1. Data Parallel-in / Data Parallel-out
2. Data Serial-in / Data Parallel-out
3. Data Serial-in / Data Serial-out

 
1) 4-bit Parallel-in Parallel-out Register



1) 4-bit Parallel-in Parallel-out Register




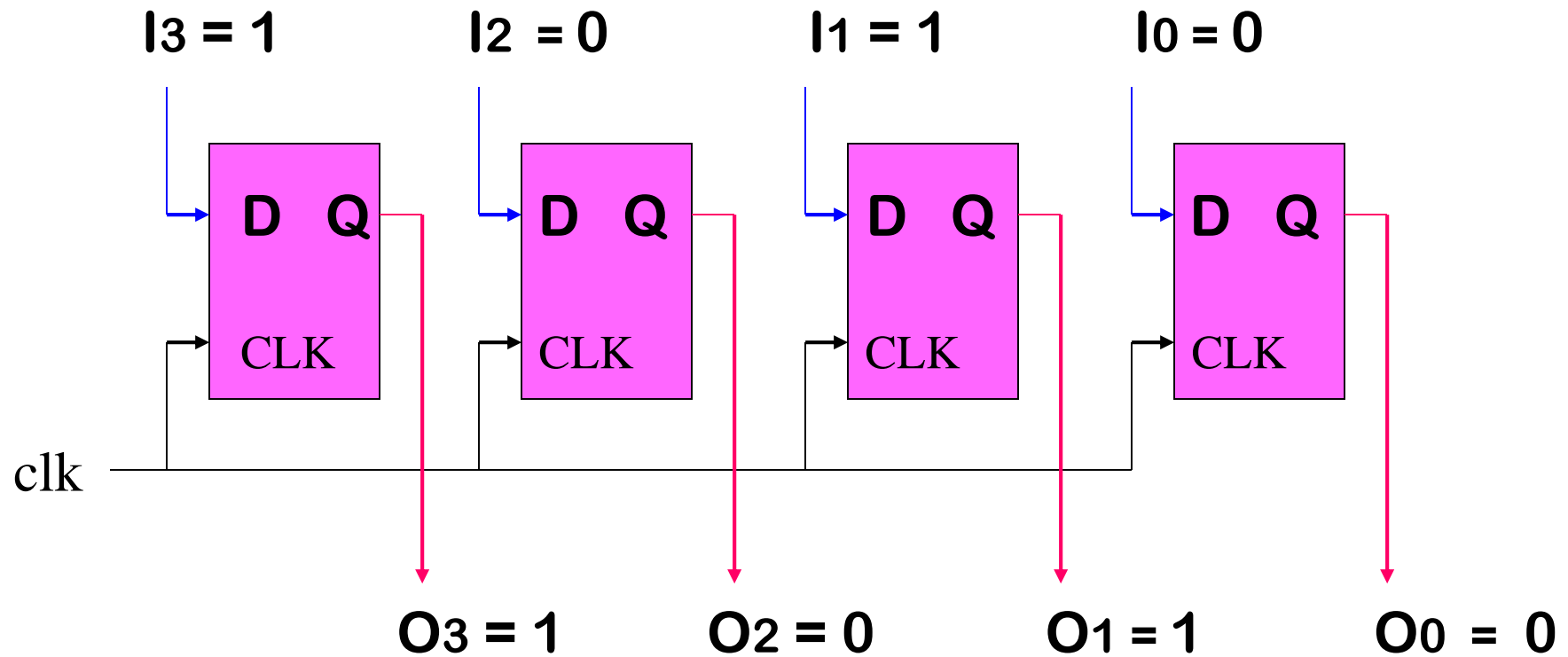1) 4-bit Parallel-in Parallel-out Register




The data stored in the register are available at all time at the output lines

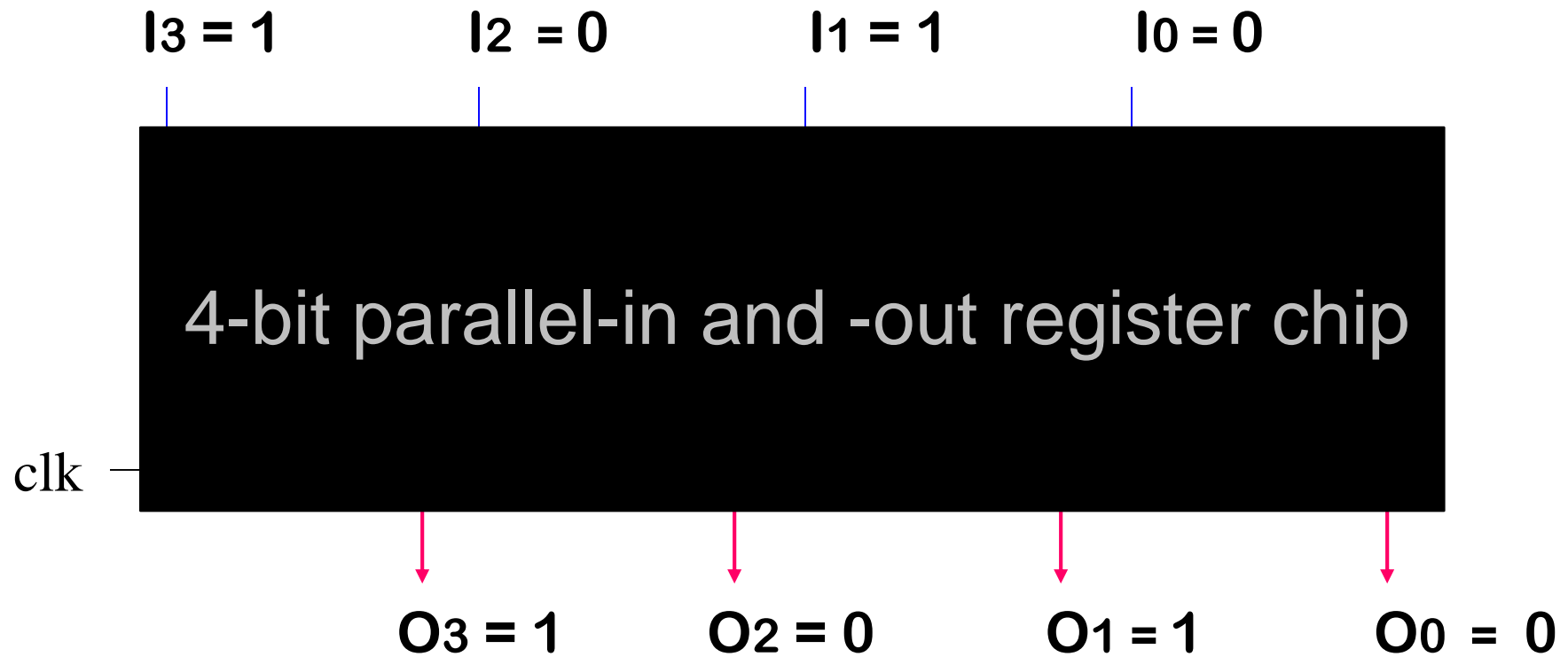
1) 4-bit Parallel-in Parallel-out Register



2) Serial-in parallel-out shift register

 

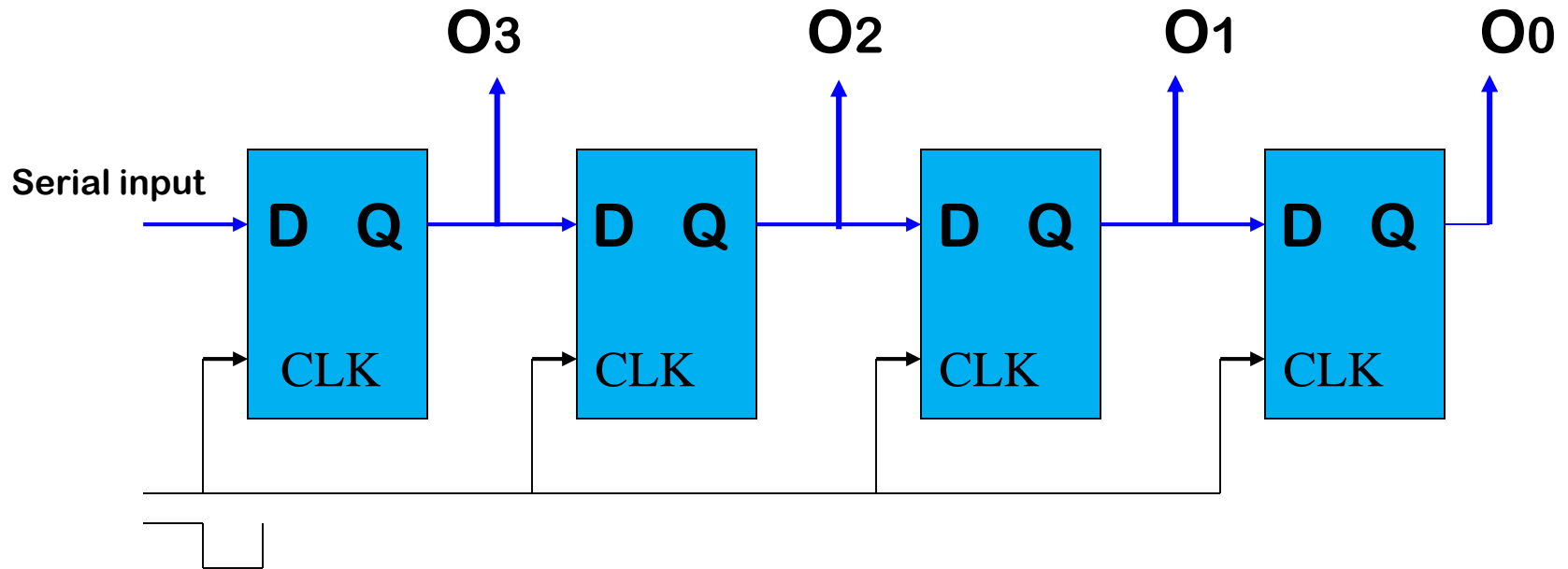
2) 4-bit serial-in parallel-out shift register




3) Serial-in Serial-out shift Register



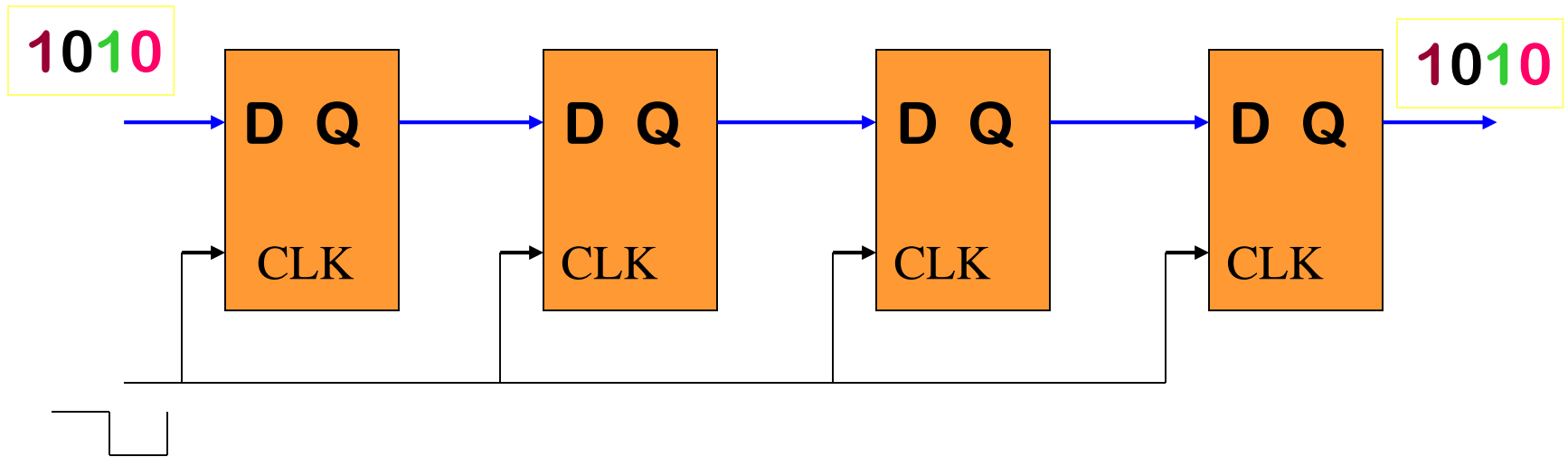
3) 4-Bit Serial-in Serial-out shift Register



 


Z80 CPU


Die of the Z80 microprocessor (CPU)

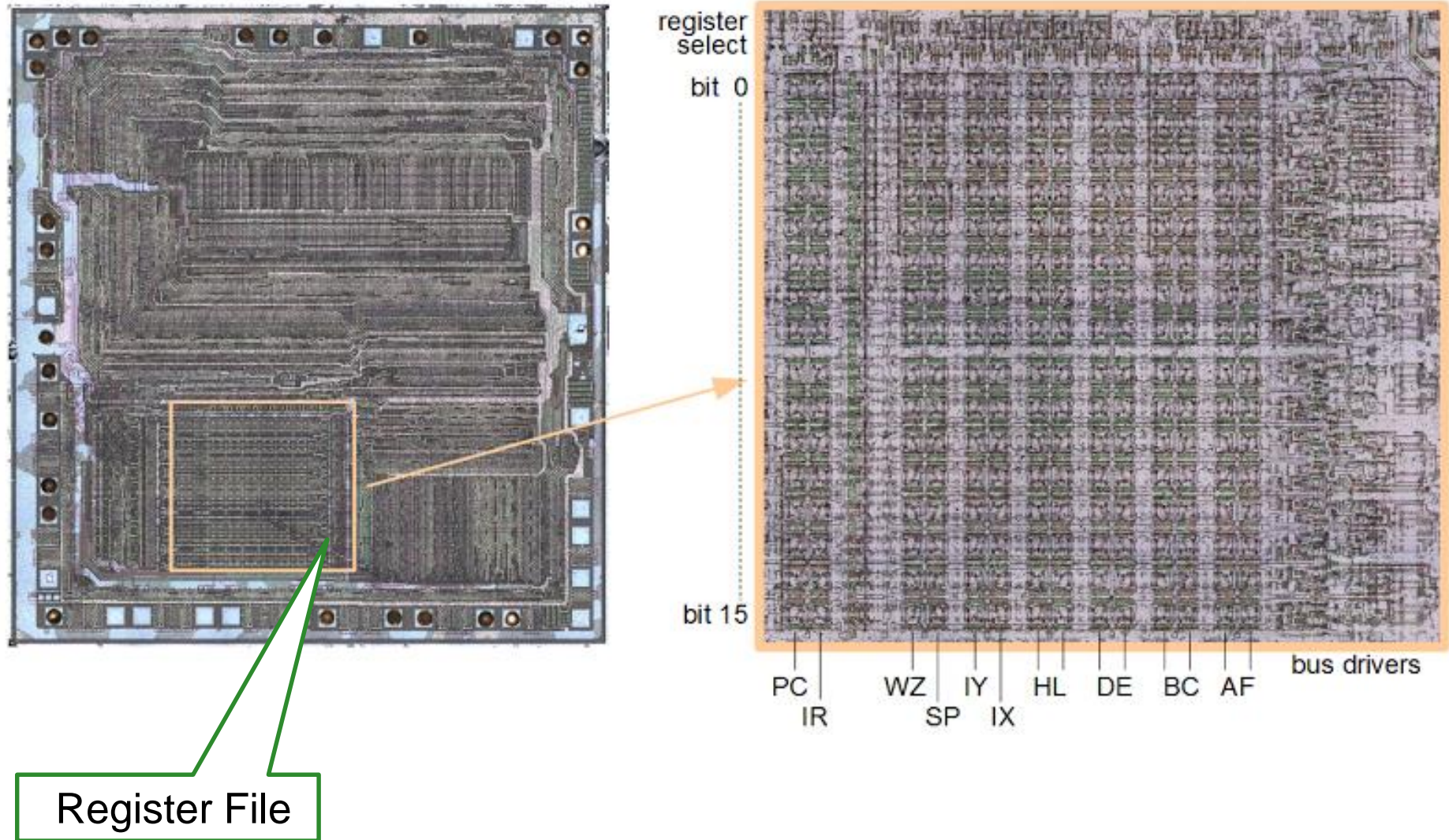

Memory

 

ROM...RAM...Cache (Memories)

 

Types of Memory

- ROM
- RAM
- Cache (?)
- Flash (?)

Types of Memory

- ROM (read-permanent)
- RAM (read/write-temporary)
- Cache (very fast RAM-temporary)
- Flash (new fast RAM-permanent)

Types of Memory

- ROM
- RAM
- Cache
- Flash
- Magnetic disc (Hard, Floppy, Zip, ...)
- Tape
- Optical (CD-ROM, CD-R, CD-RW, WORM, DVD-ROM)

ROM++

- PROM (Programmable ROM)
- EPROM (Erasable Programmable ROM)
- EEPROM (Electrically EPROM)




RAM

- Dynamic → D-RAM
 - Static → S-RAM
 - Video → V-RAM
-
- How do use D-RAM and S-RAM ?

D-RAM

- Good for large memory systems
- Low cost: Requires 1 transistor for storing
- Requires refreshing (recharging), thousands of times per second, of the stored information (electric charge in a capacitor) as it loses the data.

D-RAM basic memory cell

 

NMOS (N-type metal-oxide-semiconductor)

Refreshing


- Typical refresh rates: 7.8, 15.6, ..., 128 μsec
- Refreshing is done...
 - Counters, Voltage pulses
 - “Self-refresh mode”
 - [Memory chip controller (MCC)]

D-RAM is the ...


- ?...? Memory

D-RAM is the ...

- Main (system) Memory

 

RAM

 

In general the computer memory...

- The memory is build in powers of 2.
- Example:
 - 1Kb = 2^{10} = 1,024 bits
 - 64 Kb = 2^{16} bits

Main operations of the memory

- Write = Store information to RAM
- Read = Load information from RAM

S-RAM

- Stores binary information without the necessity of periodic refreshing
- High cost: Requires 4 or 6 transistors
- Good for small memory systems


S-RAM is the ...

- ?...? Memory


S-RAM is the ...

- Cache Memory


4 to 6 Transistors

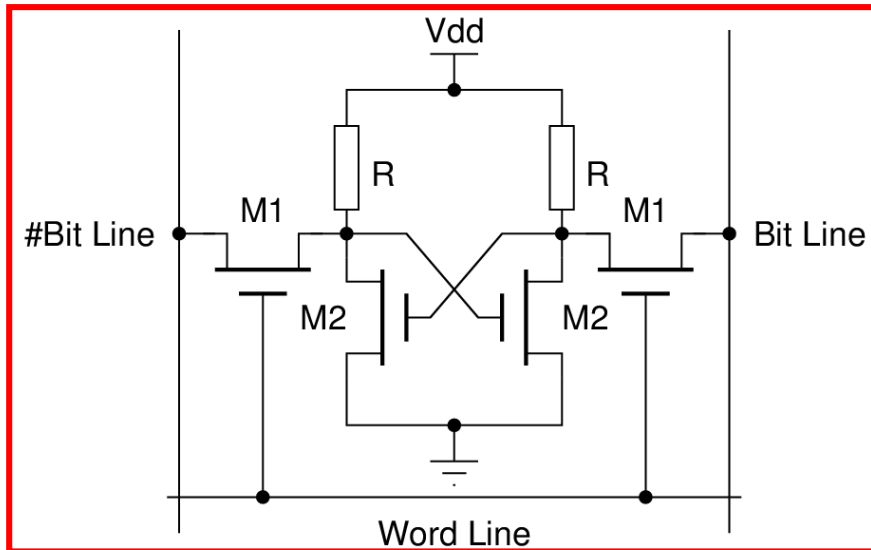

 "SRAM Cell (6 Transistors)" by Inductive load - Own work. Licensed under Public Domain via Wikimedia Commons - [http://commons.wikimedia.org/wiki/File:SRAM_Cell_\(6_Transistors\).svg#/media/File:SRAM_Cell_\(6_Transistors\).svg](http://commons.wikimedia.org/wiki/File:SRAM_Cell_(6_Transistors).svg#/media/File:SRAM_Cell_(6_Transistors).svg)




S-RAM is the ...Cache Memory

 

Cache Memory; Today ... 2 or 3 levels

 - On chip (L1) cache memory
- On/off chip (L2) cache memory
- On/off chip (L3) cache memory




Cache memory = Shared memory between the available cores

Today CORTEX –A77 (2020)

Cortex-A77: Redefined mobile device performance


- Built with upgrades in mind
 - Key architecture and interfaces aligned with Cortex-A76
 - Support for DynamIQ Shared Unit (DSU)
- Key features:
 - Armv8.2 architecture, AArch32 and AArch64 support
 - 64KB L1 I/D caches
 - 256KB and 512KB private L2 caches
 - Up to 4MB shared L3 cache
- big.LITTLE capable using Cortex-A55

arm CORTEX® -A77


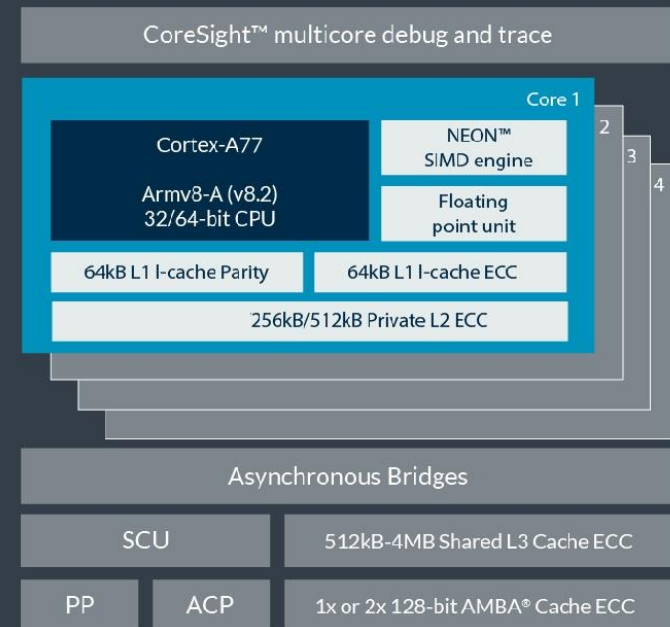


The embargo for this content presented at Arm Tech Day will lift on Sunday, May 26 at 9:00 p.m. PT. Corresponding UK and Taiwan times are: Monday, May 27 at 5:00 a.m. BST / Monday, May 27 at 12:00 p.m. China Standard Time

10-Core CPU with Cache Memory (i7-6950X)

 

10-Core CPU with Cache Memory (i7-6950X)

 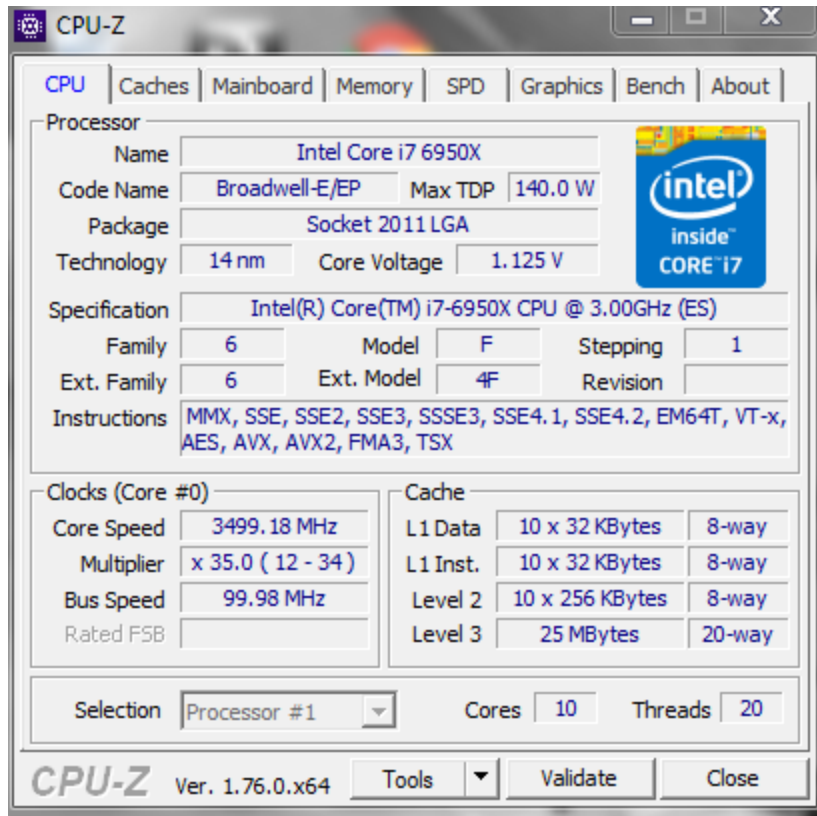

The Apple A7/Cyclone core



- CPU Codename----- Cyclone,
ARM ISA----- ARMv8-A(32/64),
Issue Width----- 6 micro-ops,
Reorder Buffer Size----- 192 micro-ops,
Branch Mispredict Penalty---16 cycles (14 – 19),
Integer ALUs----- 4,
Load/Store Units----- 2,
Load Latency----- 4 Cycles,
Branch Units----- 2,
Indirect Branch Units----- 1,
FP/NEON ALUs----- 3,
L1 Cache----- 64KB I\$ + 64KB D\$,
L2 Cache----- 1MB,
L3 Cache----- 4MB.

<https://www.top500.org/>

- Summit - IBM Power System AC922



- **More than 2,414,592 cores**

<https://en.wikichip.org/wiki/supercomputers/summit>


Typical values (2019)

- DRAM = up to ? GB
- SRAM = up to ? MB (level-3)


Typical PC values (2019)

- DRAM = up to 8-128 GB
- SRAM = up to 8 MB (level-3).


CPU

 


Cache Memory

 


Main Memory

 

Hard disk

 

Three Levels of Cache Memory

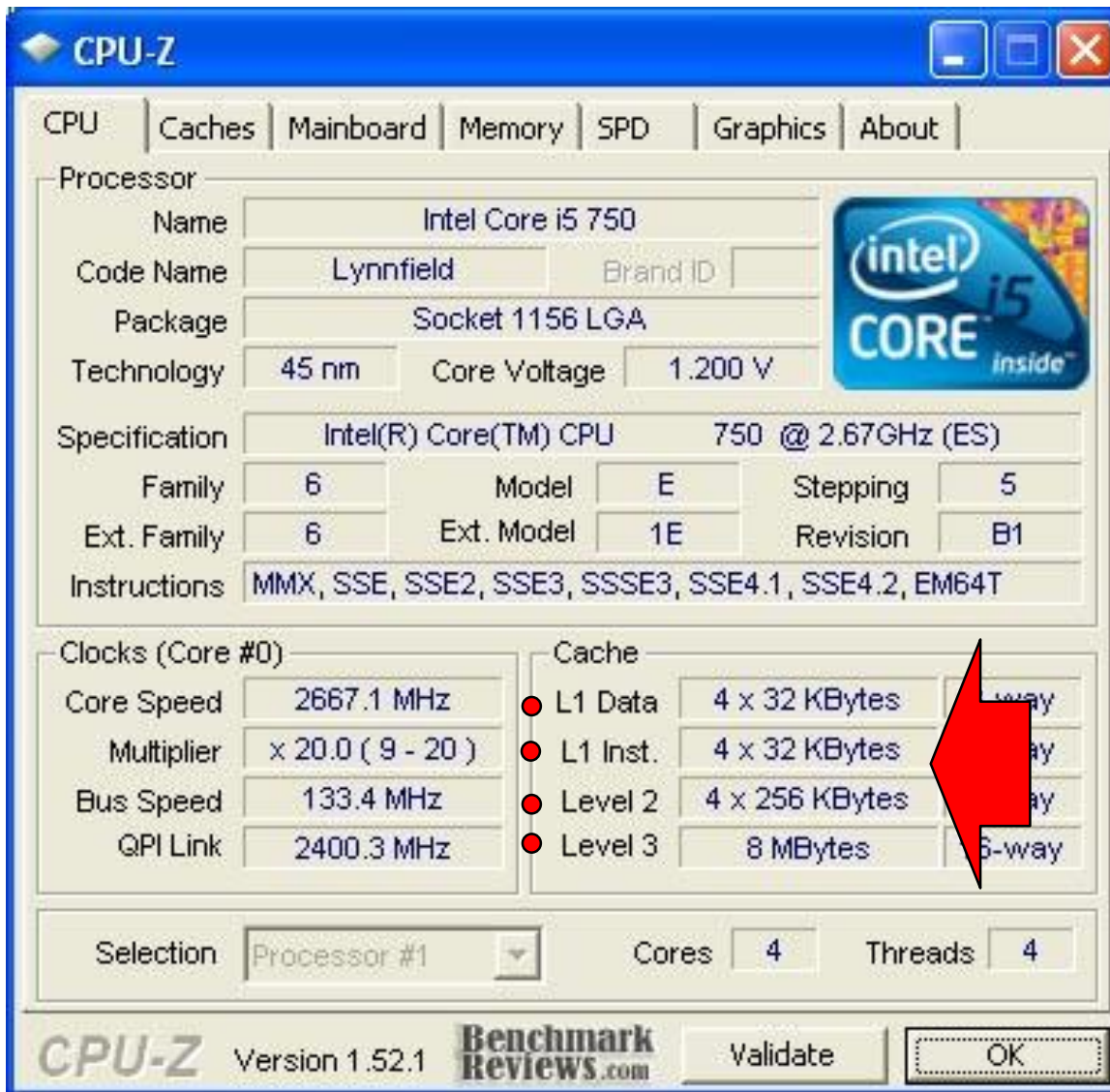

The screenshot shows the CPU-Z application window with the 'Caches' tab selected. The 'Cache' section is highlighted with a red arrow. The 'Cache' table lists the following information:


Cache	Size	Way
L1 Data	4 x 32 KBytes	4-way
L1 Inst.	4 x 32 KBytes	4-way
Level 2	4 x 256 KBytes	4-way
Level 3	8 MBytes	6-way

Other visible information in the CPU-Z window includes:


- Processor:** Intel Core i5 750, Code Name: Lynnfield, Package: Socket 1156 LGA, Technology: 45 nm, Core Voltage: 1.200 V.
- Specification:** Intel(R) Core(TM) CPU 750 @ 2.67GHz (ES).
- Clocks (Core #0):** Core Speed: 2667.1 MHz, Multiplier: x 20.0 (9 - 20), Bus Speed: 133.4 MHz, QPI Link: 2400.3 MHz.
- Instructions:** MMX, SSE, SSE2, SSE3, SSSE3, SSE4.1, SSE4.2, EM64T.
- Selection:** Processor #1, Cores: 4, Threads: 4.

The CPU-Z logo and version 1.52.1 are visible at the bottom left, and the Benchmark Reviews.com logo is at the bottom center.


Cache Memory ... RAM

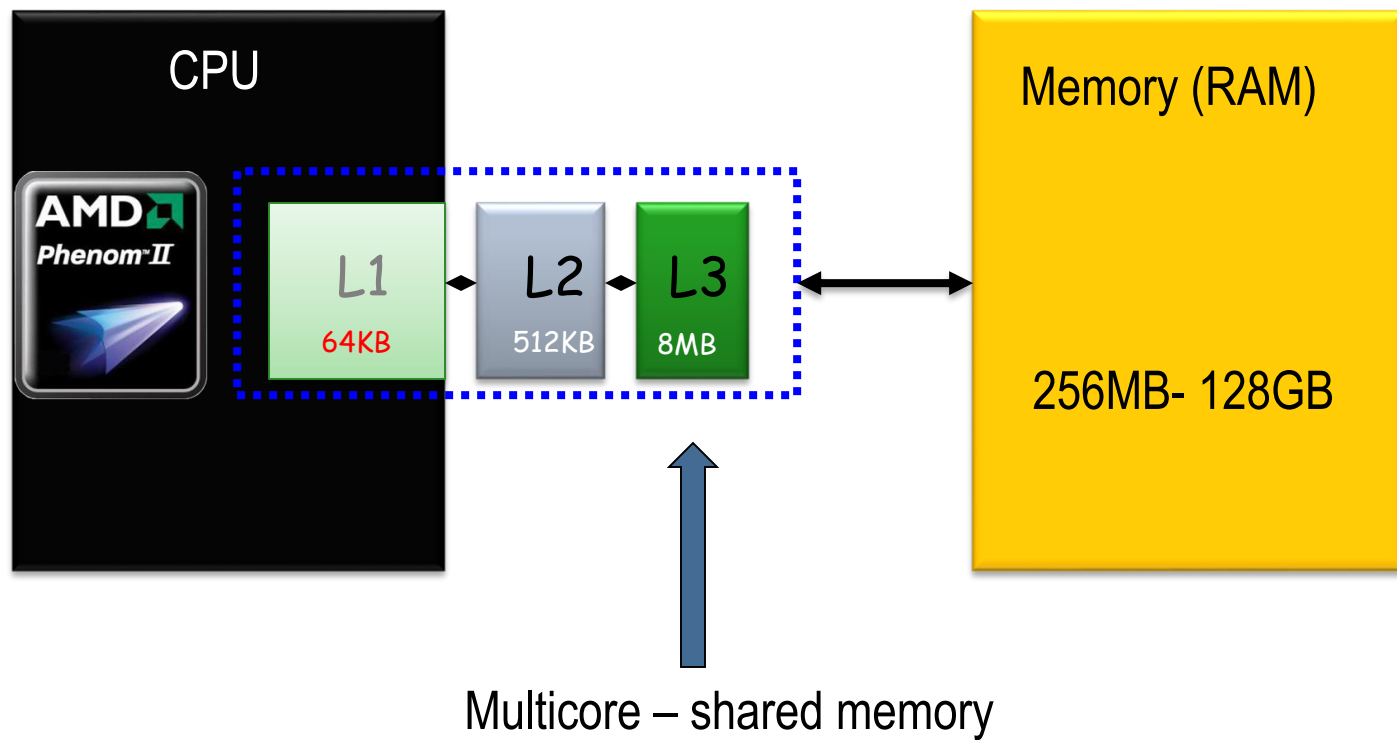

CPU and System Memory

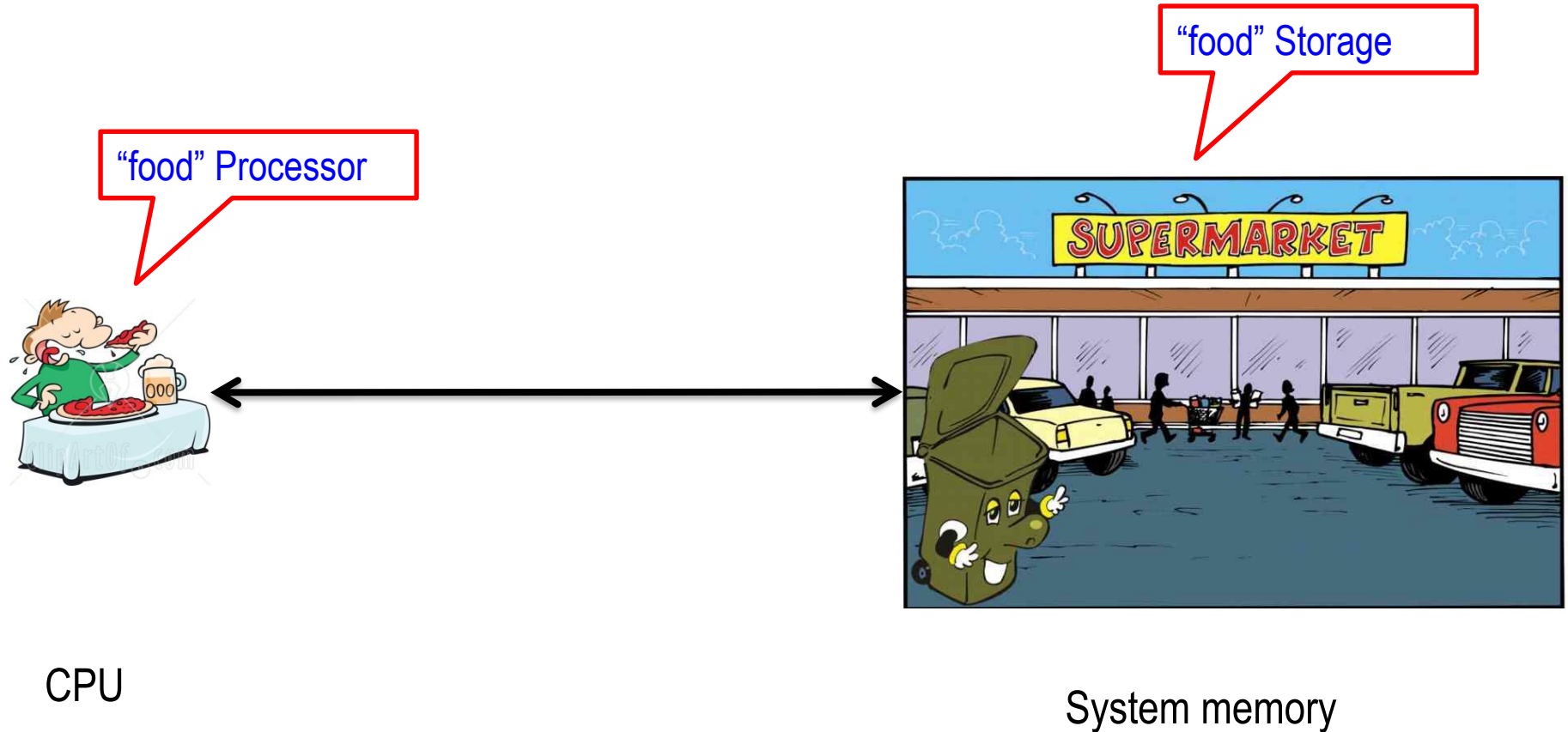

Cache Memory

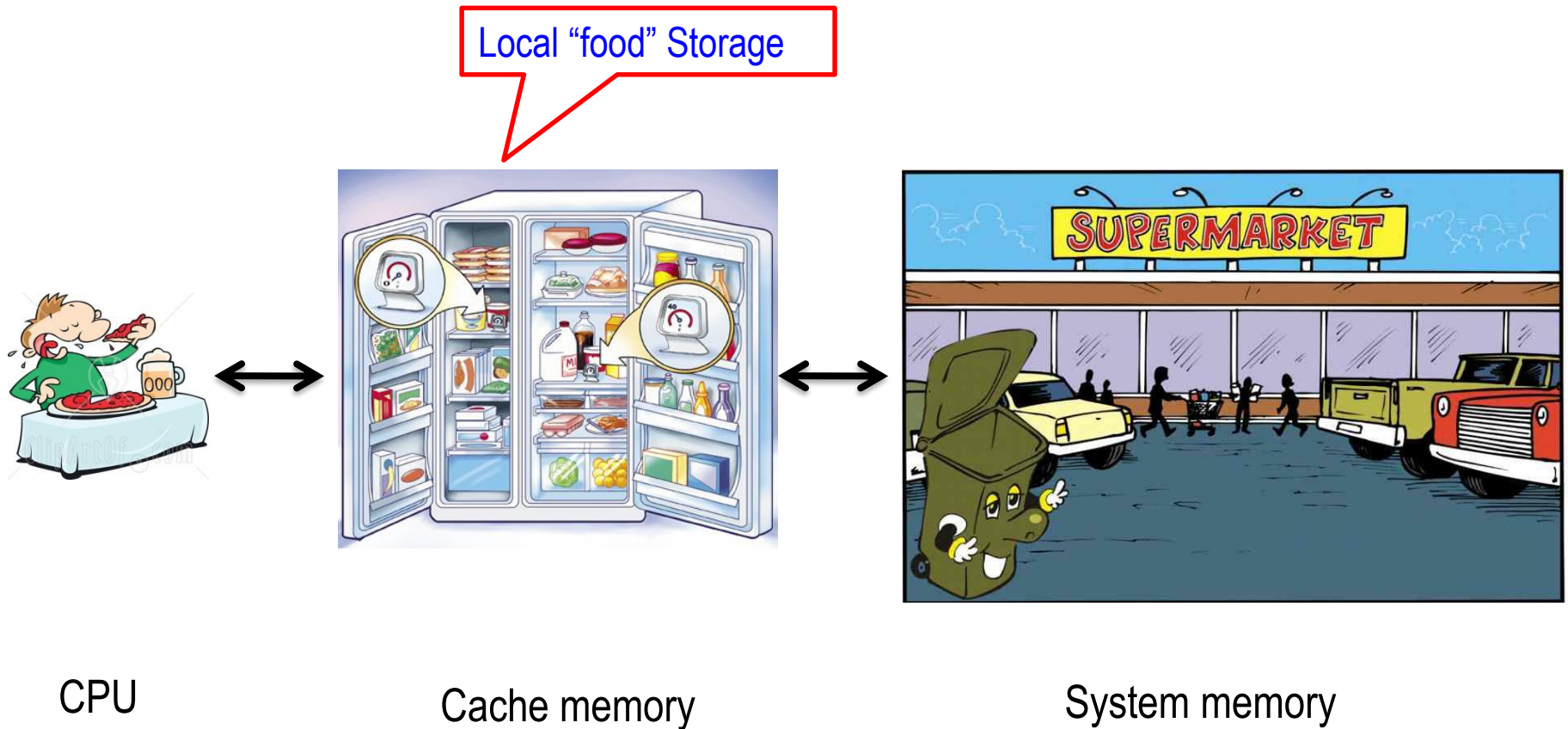

RAM


S-RAM (Cache)	D-RAM (Main)
<ul style="list-style-type: none">▪ Small & Fast▪ Complex▪ No refresh▪ More expensive	<ul style="list-style-type: none">▪ Slow & Large▪ Simple▪ Refresh needed▪ Less expensive

Specialized RAM is the VRAM



- VRAM = Video RAM
- Dual ported Dynamic RAM
- Can write while someone else reads.




The Memory Hierarchy

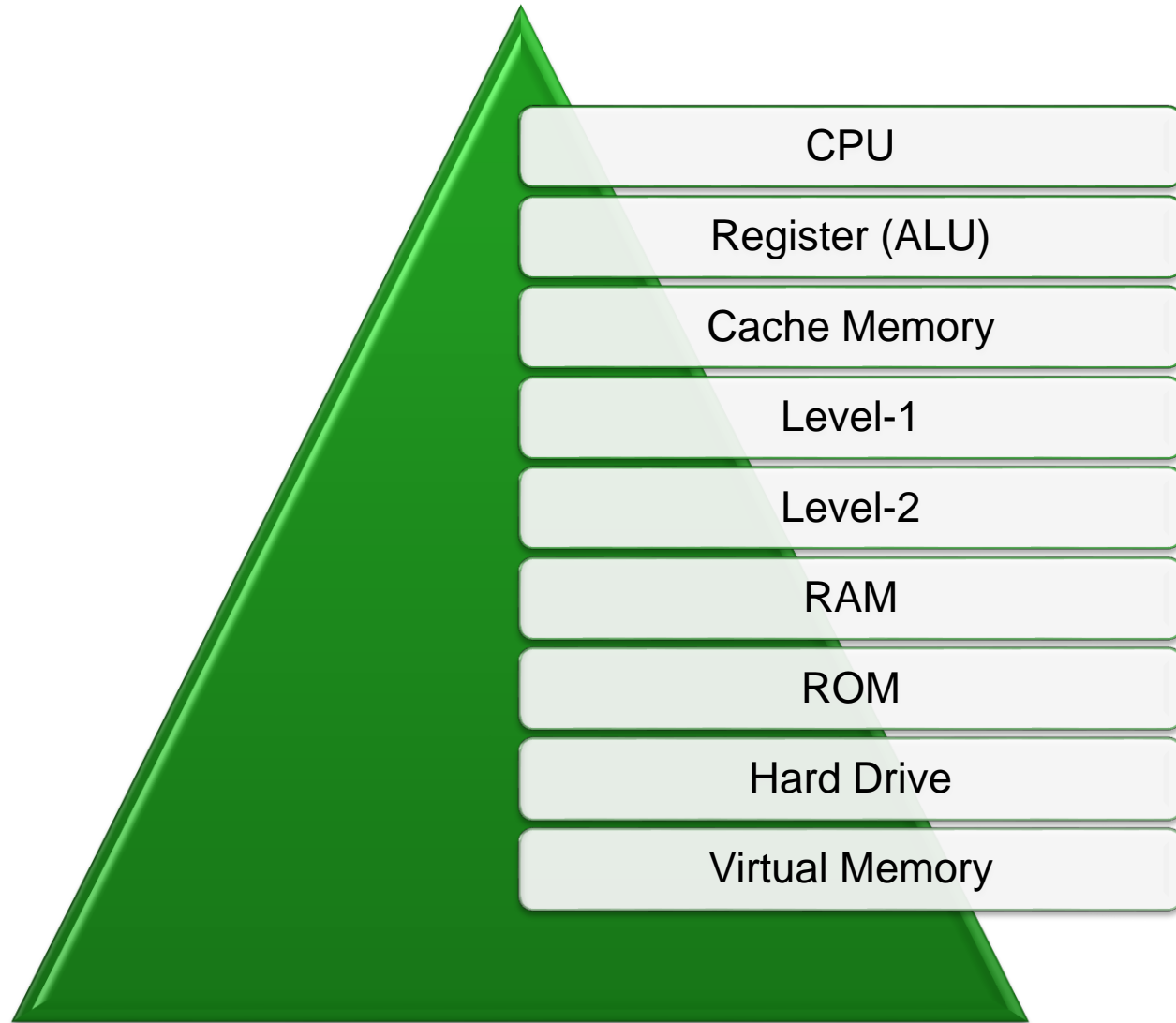

Memory cell

 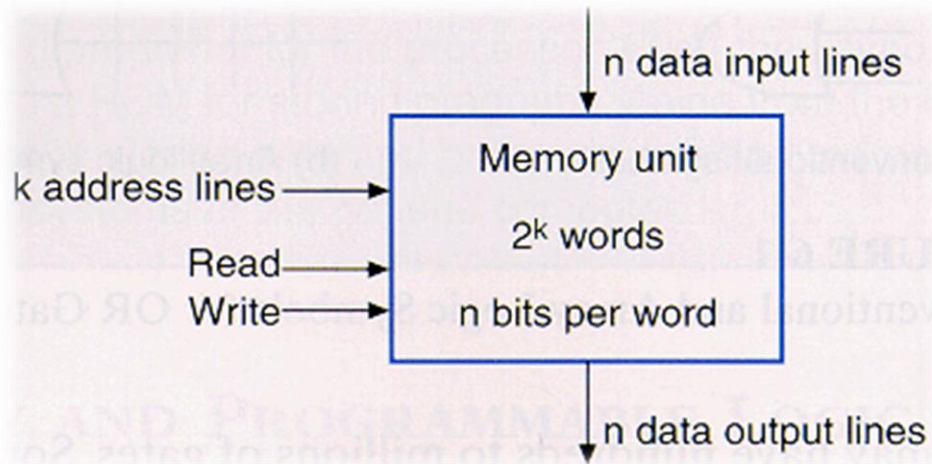


Basic memory cell

 


Design a 16x4 bits RAM memory

Memory system: 16 x 4 bits

 


Data inputs


Data Inputs

 


Data outputs

 


Read/Write (R/W) line

 

Address lines: 4 ($16 = 2^4$)

 

With a 2-4 Decoder 2 lines are fine ...

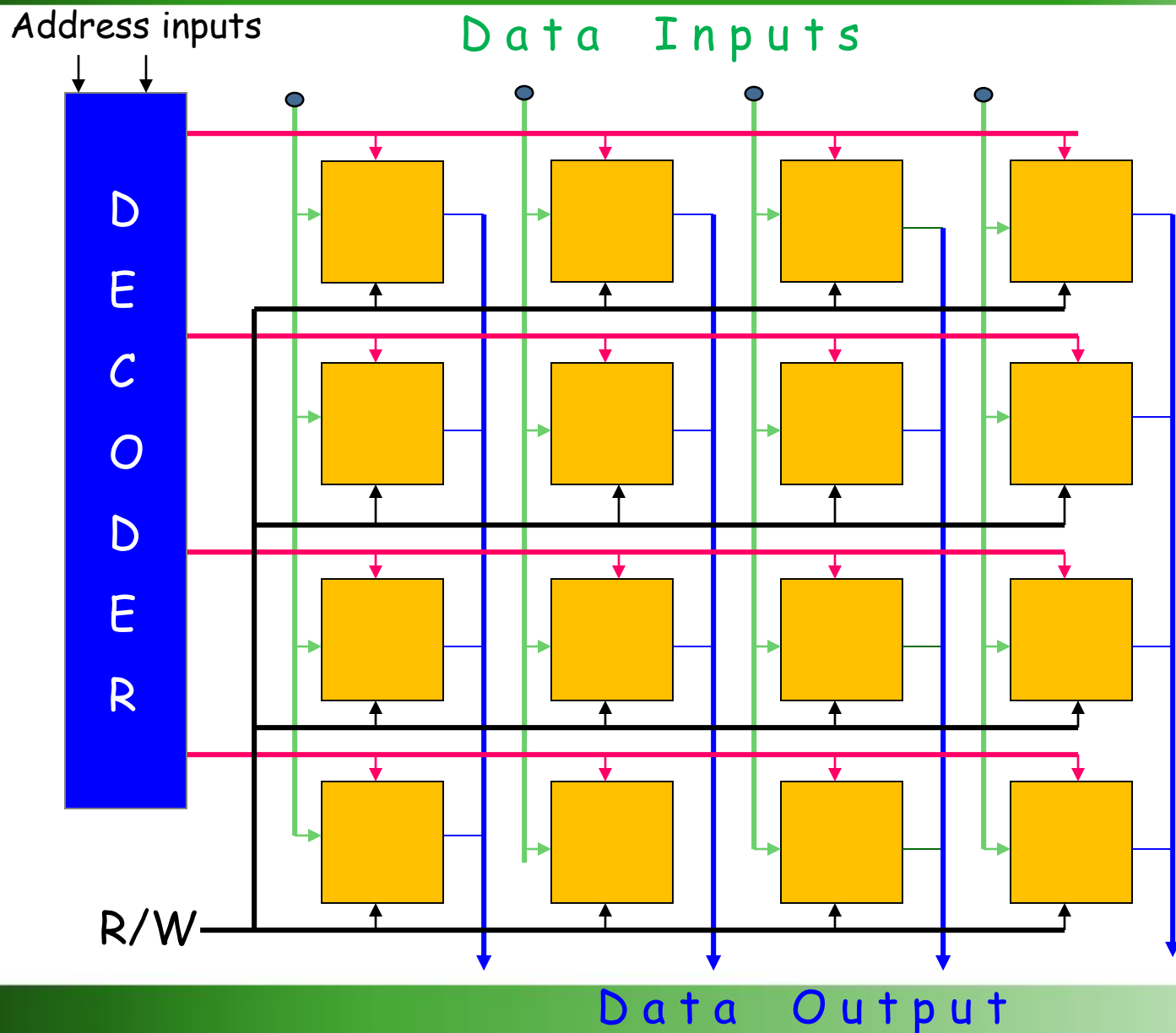


Address inputs

Data Inputs

16x4 bits Memory Chip

R/W

Data Outputs

 

A 1Kb DRAM memory chip

$$1\text{Kb} = 1024 = 2^{\{10\}} \text{ bits}$$


1024 x 16 memory (1Kb x 16)

<u>Memory address</u>		<u>Memory contents</u>
<u>Binary</u>	<u>Decimal</u>	
0000000000	0	10110101 01011100
0000000001	1	10101011 10001001
0000000010	2	00001101 01000110
	.	.
	.	.
	.	.
	.	.
	.	.
1111111101	1021	10011101 00010101
1111111110	1022	00001101 00011110
1111111111	1023	11011110 00100100

10 address lines.
Since $2^{10} = 1024$

data

Memory design using memory-chips

 


Use two 64K x 4 ROM memory modules to create a 64K x 8 ROM memory system.

How many bits has the:

→ Data bus (?)


→ Address bus (?)

64K x 8 ROM, using 2-64 x 4

 


64K x 8 ROM, using 2-64 x 4

Address bus: A0-A15 = 16

 

64K x 8 ROM, using 2-64 x 4

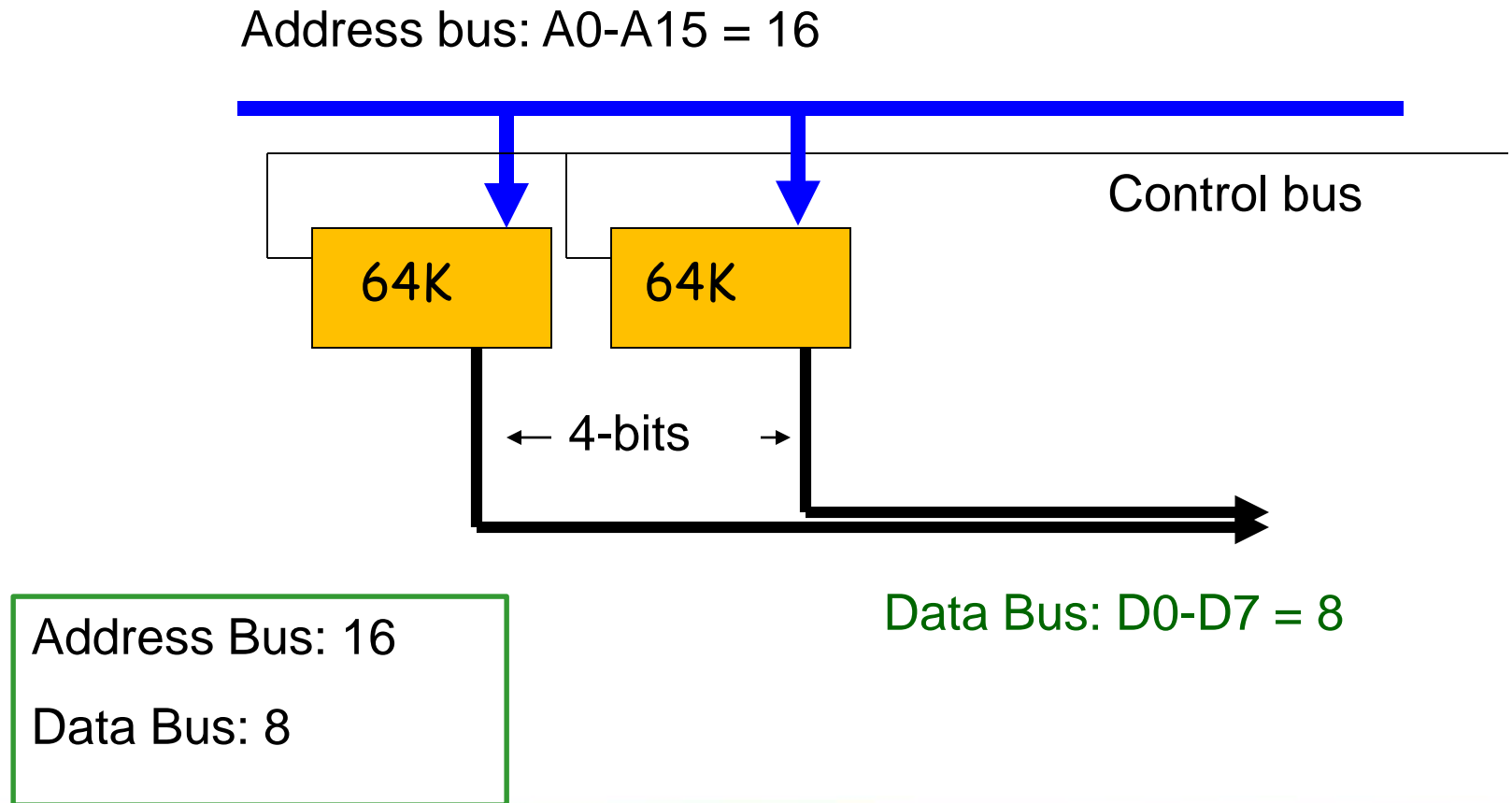






Use (?) 64K x 4 ROM memory modules to create a 64K x 16 ROM memory system.

How many bits has the:

→ Data bus (?)


→ Address bus (?)

64 K x 16 ROM

     

64 K x 16 ROM

Address bus: A0-A15 = 16

 

Address Bus: 16

Data Bus: 16

Data Bus: D0-D15 = 16

Use (?) 1k x 8 RAM memory modules to create a 4k x 8 RAM memory system.


How many bits has the:

→ Data bus (?)

→ Address bus (?)

4K x 8 (using 1Kx8) RAM


Address bus: A0-A9 = 10

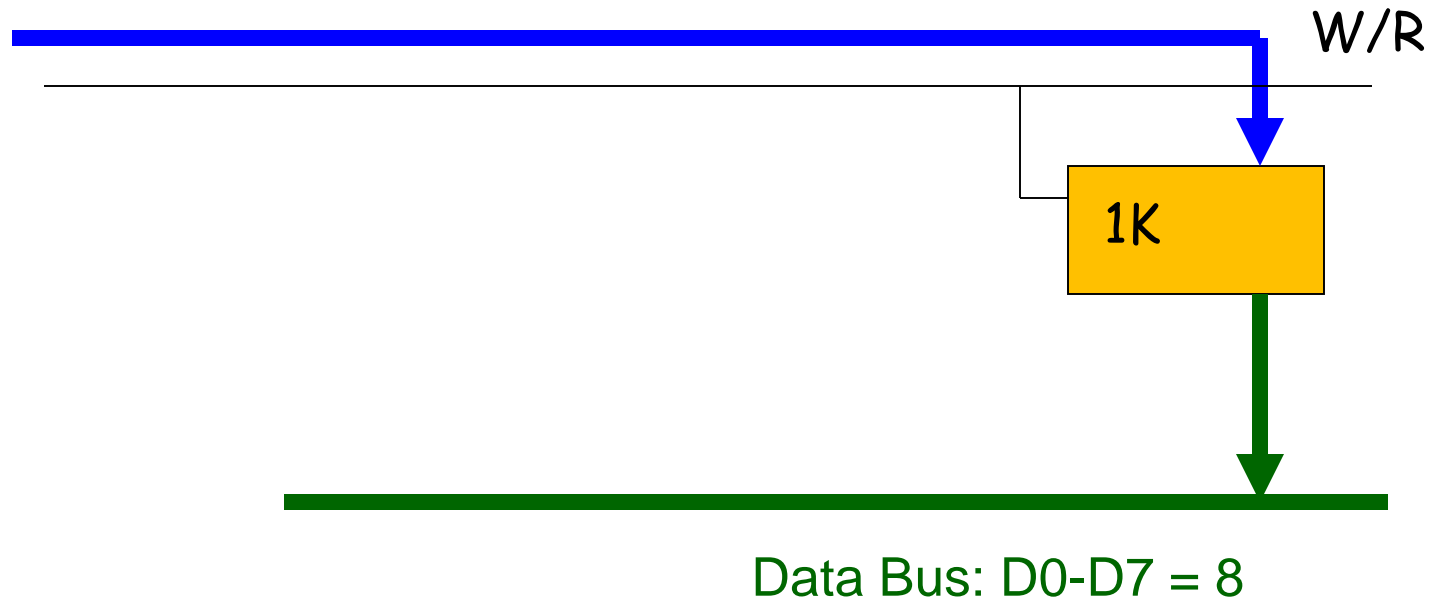

What else?




Address bus: A0-A9 = 10

 

Data Bus: D0-D7 = 8

What else?

4K x 8 (using 1Kx8's) RAM

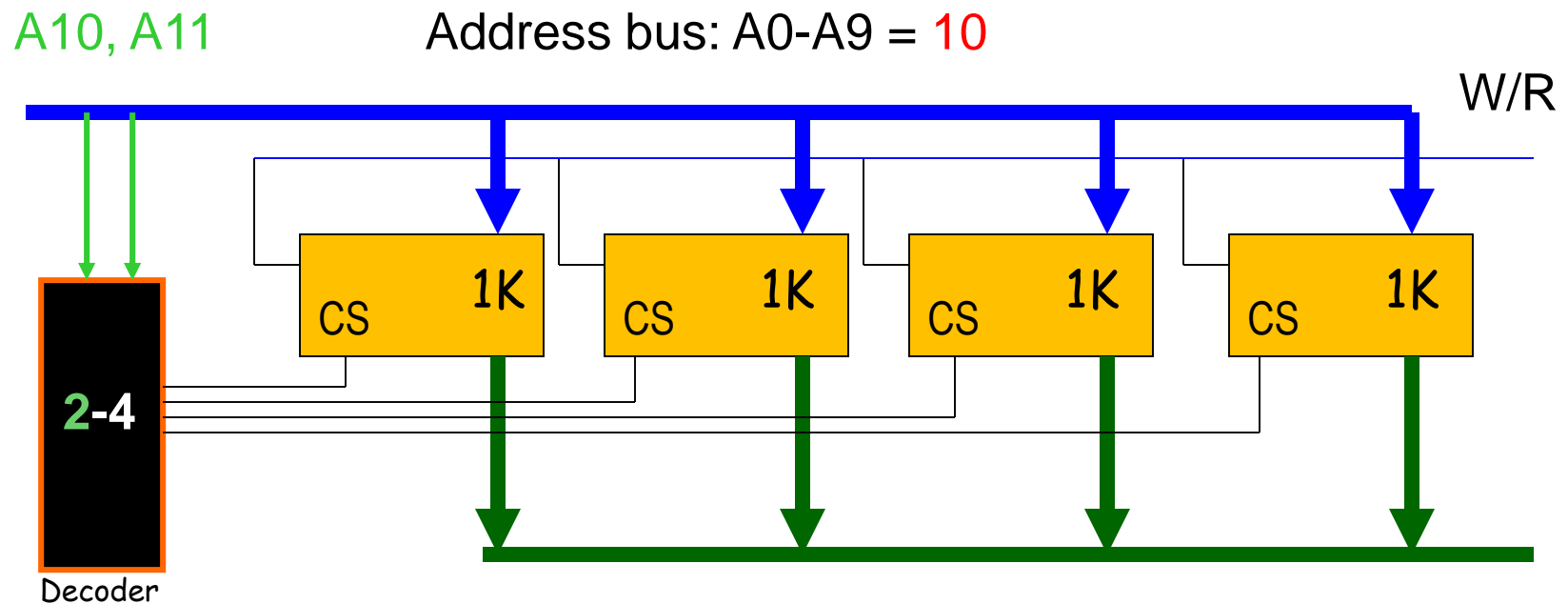

Address Bus: $10 + A10 + A11 = 12$

Data Bus: 8

Data Bus: D0-D7 = 8

CS = Chip Selector

RAM Memory board




**Design a 2K x 8 Memory system using:
RAM (1K x 8) + ROM (1K x 8)**

How many bits has the:

→ Data bus (?)


→ Address bus (?)

2K x 8: RAM + ROM

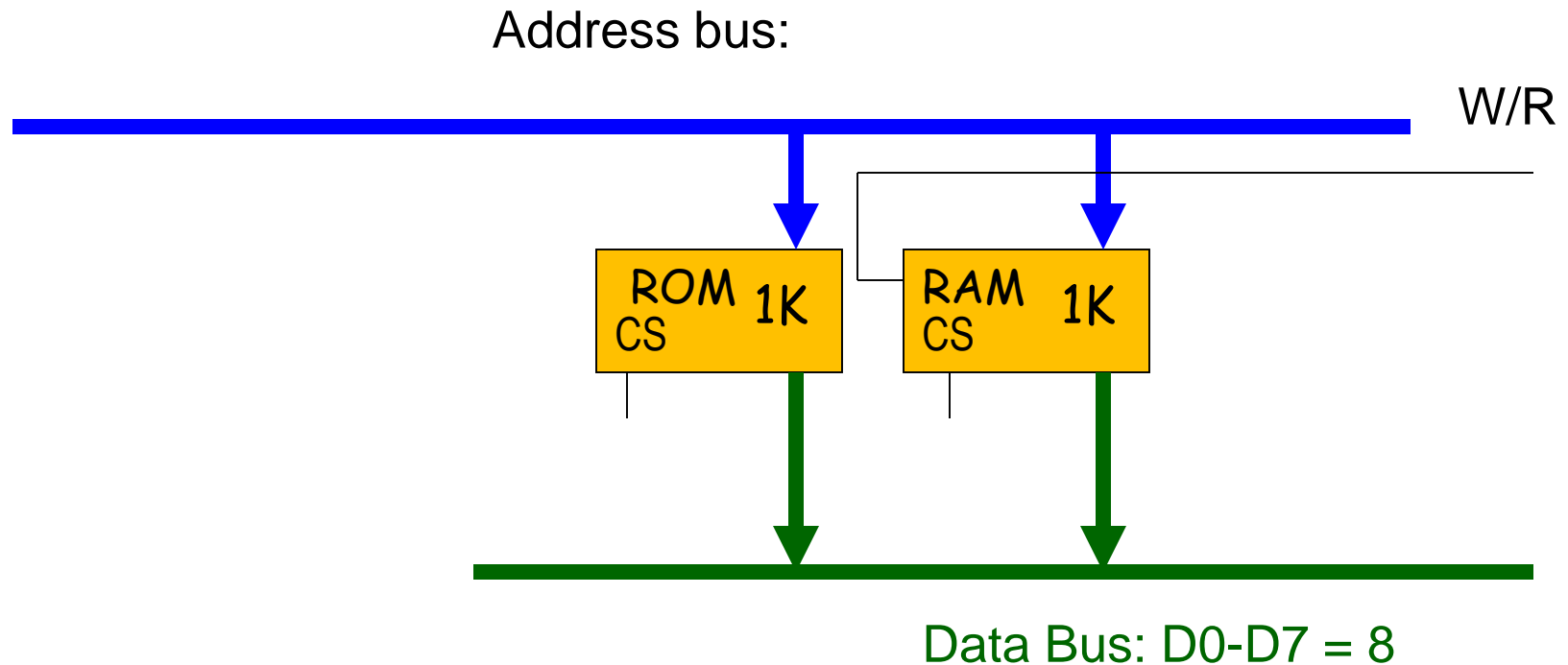


CS = Chip Selector

2K x 8: RAM + ROM

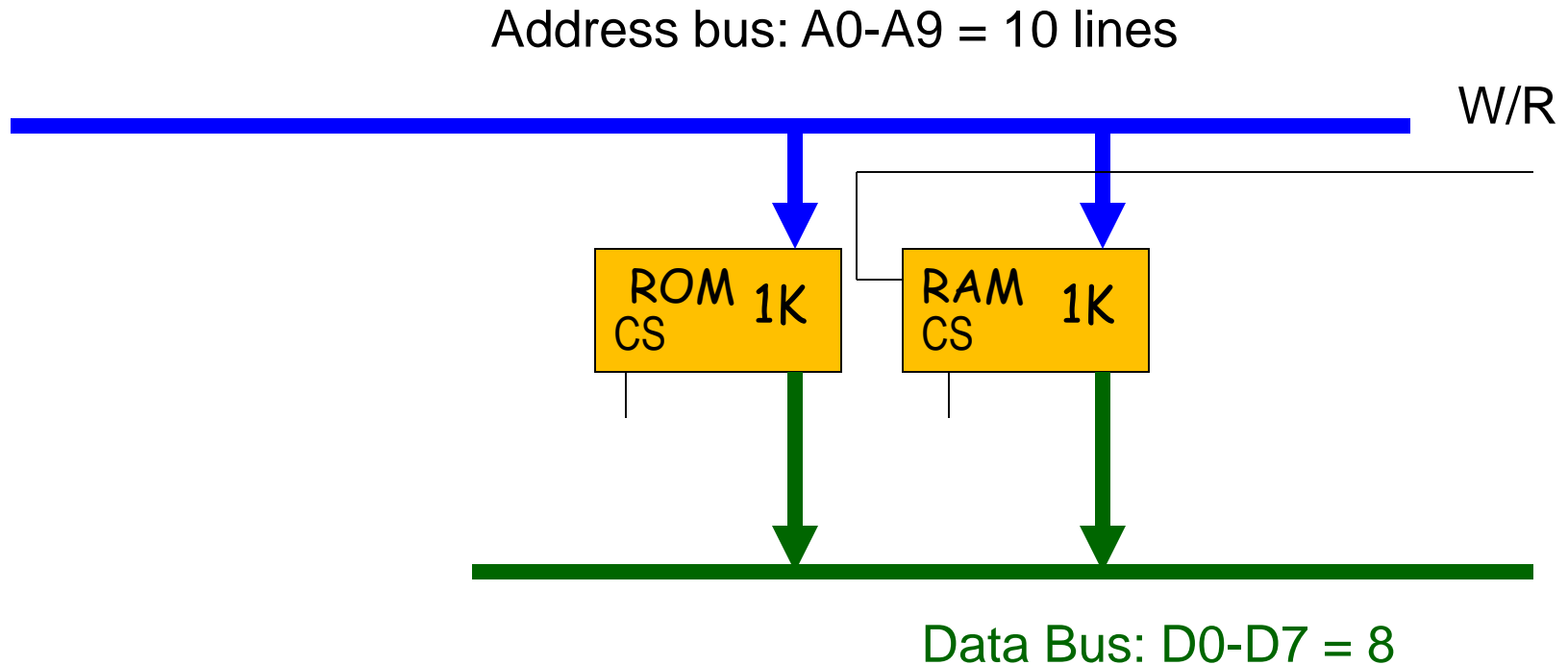


2K x 8: RAM + ROM

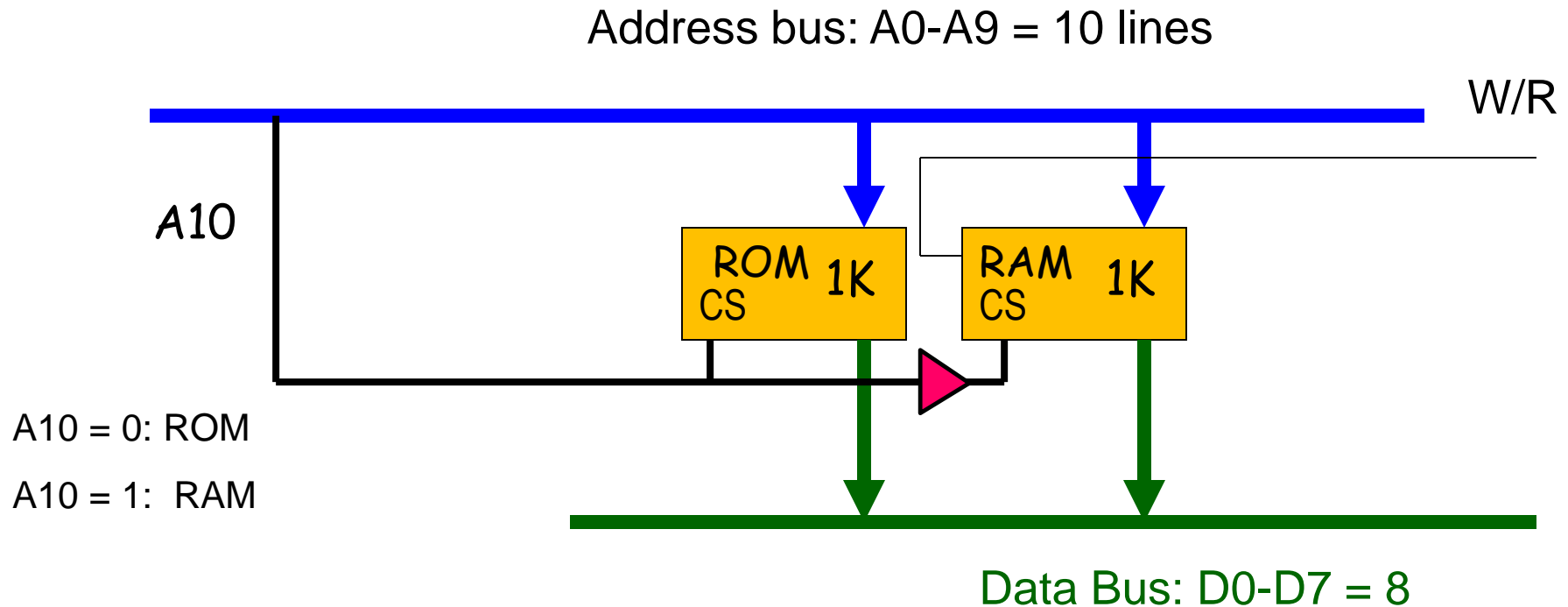

2K x 8: RAM + ROM

Address bus: A0-A9 = 10 lines

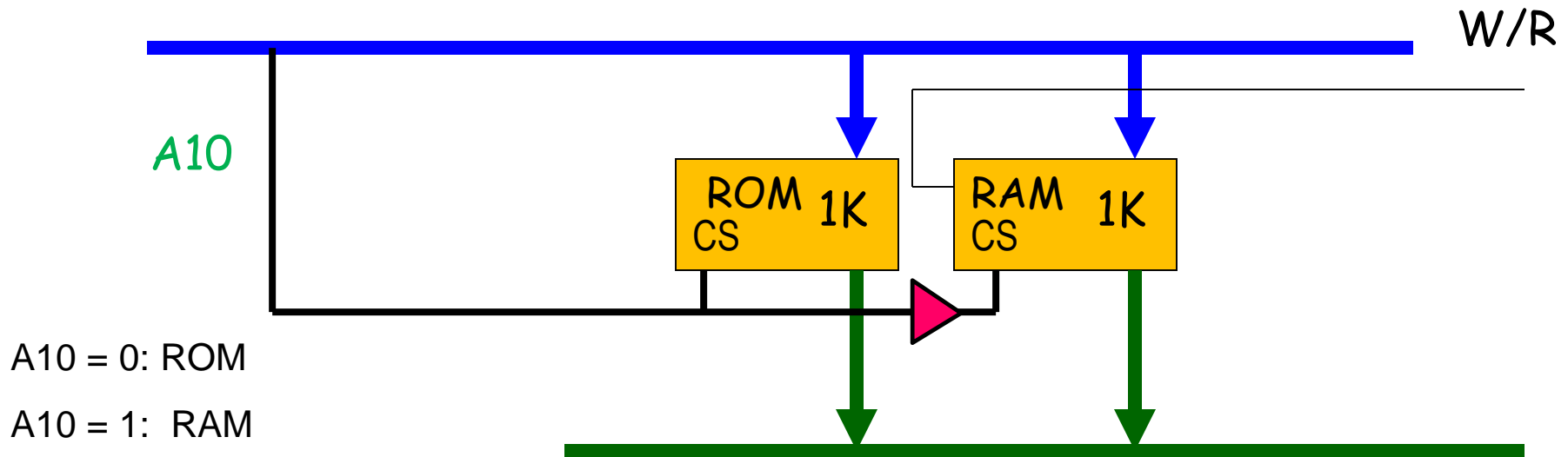


Address Bus: 10 + A10 = 11

Data Bus: 8

Data Bus: D0-D7 = 8

Equivalently using a decoder

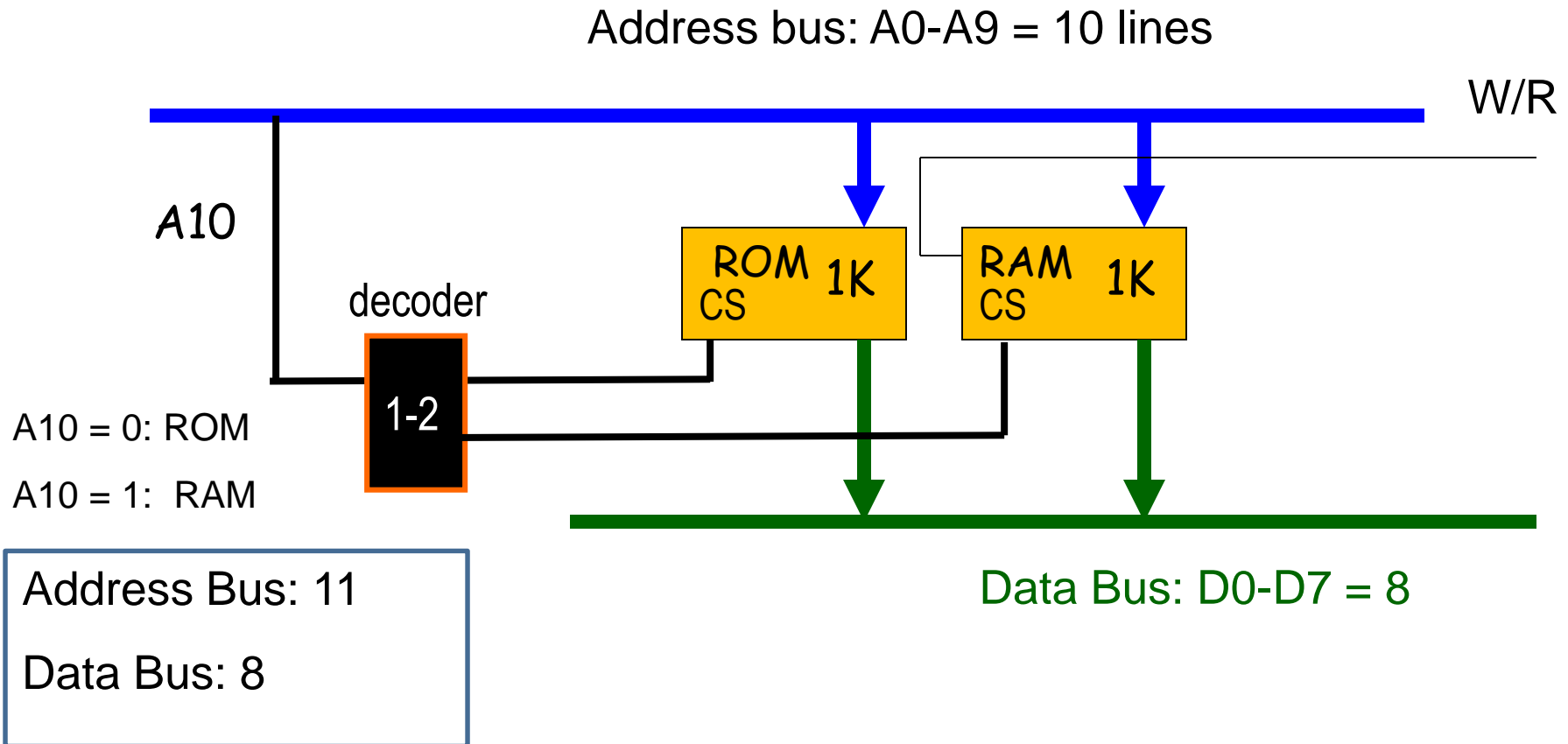

ROM & RAM

ROM

- Store instructions (**permanent**) to communicate with hardware components (Input/Output devices)
- Store instructions (**permanent**) to implement functions (logic, arithmetic, ...)
- ...

RAM

- Allows data (**temporary**) to be read or written ...
- Store (**temporary**) CPU and memory transfers
- Stores (**temporary**) currently used program instructions ...
- ...

We studied ...

