


Boolean Simplification



Two ways ...

1. A Boolean expression is given
2. A Logic Circuit is given.

1. A Boolean Expression is given

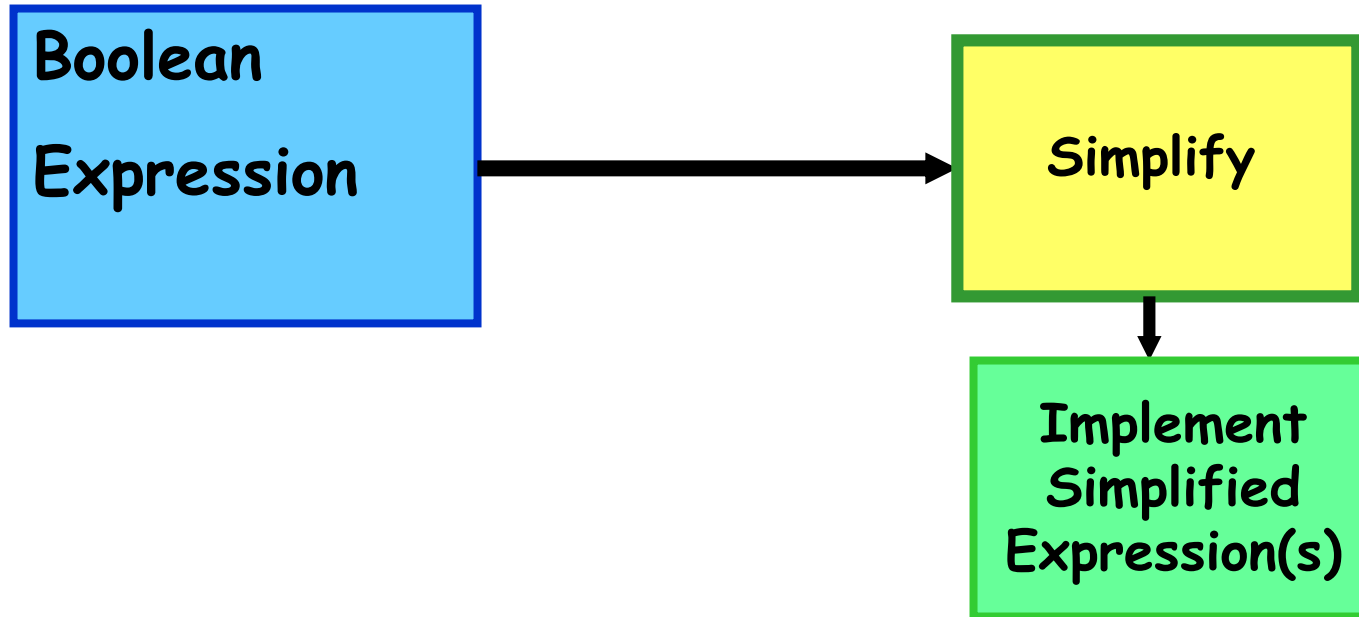


How can we simplify?

Boolean expression simplification algorithm

- Put the Boolean expression into sum of-products (SOP) form
- Apply the known Boolean simplification rules
- Implement.

2. A Logic Circuit is given

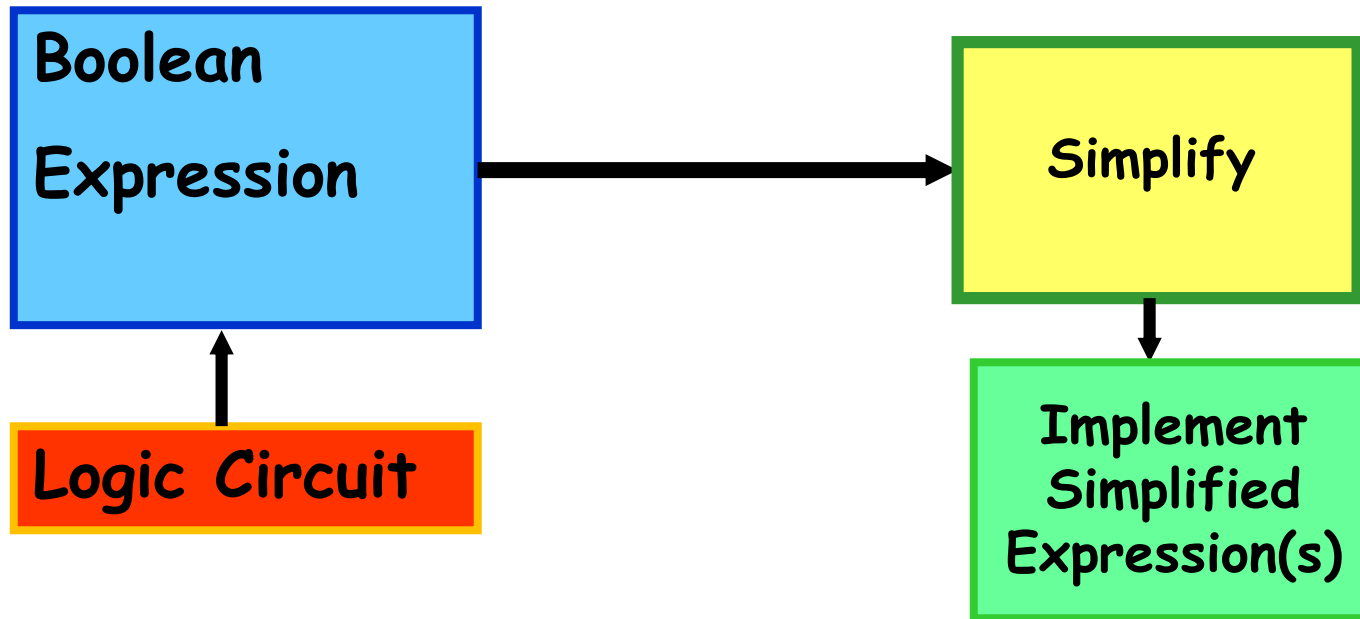

How can we simplify a Logic Circuit?

Logic Circuit simplification algorithm


- Derive the output Boolean expression
- Apply the known Boolean simplification rules
- Implement.




Example

Logic Circuit; Derive Z


Example

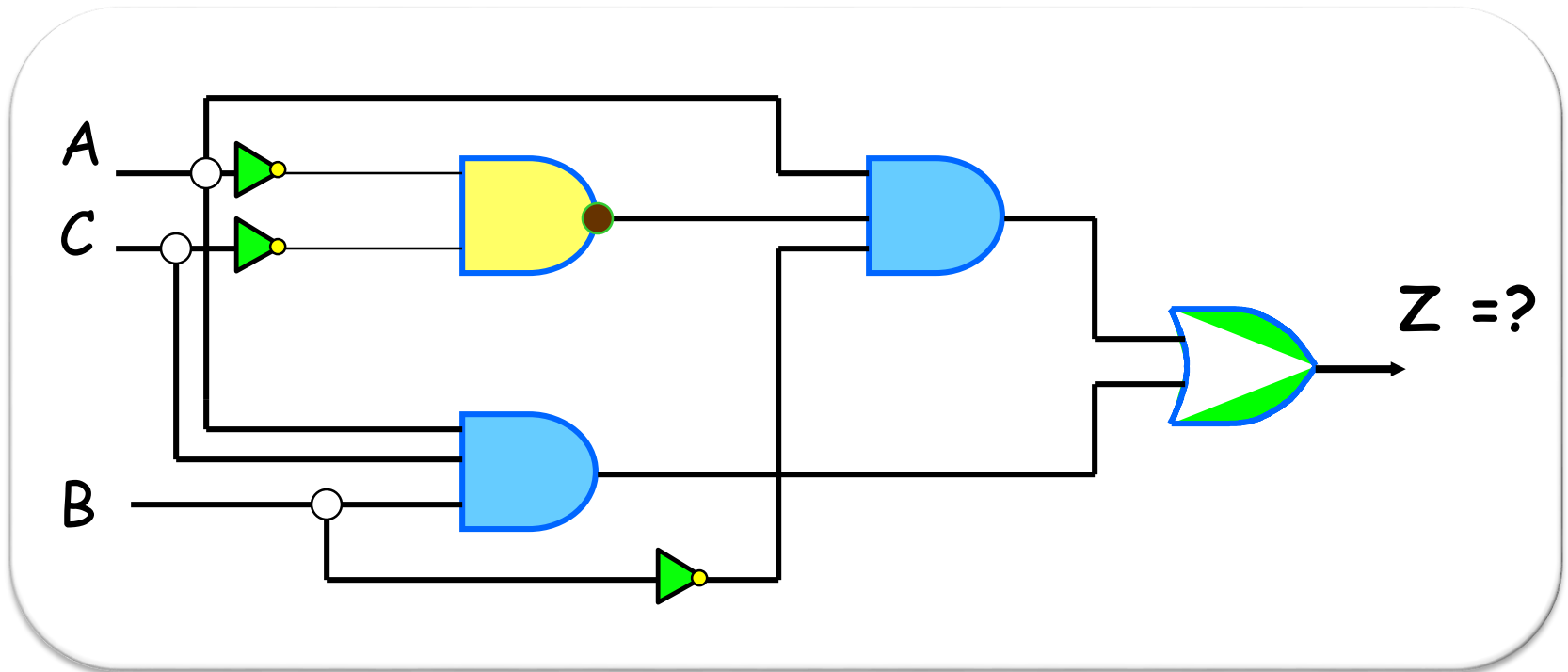


Derive Z

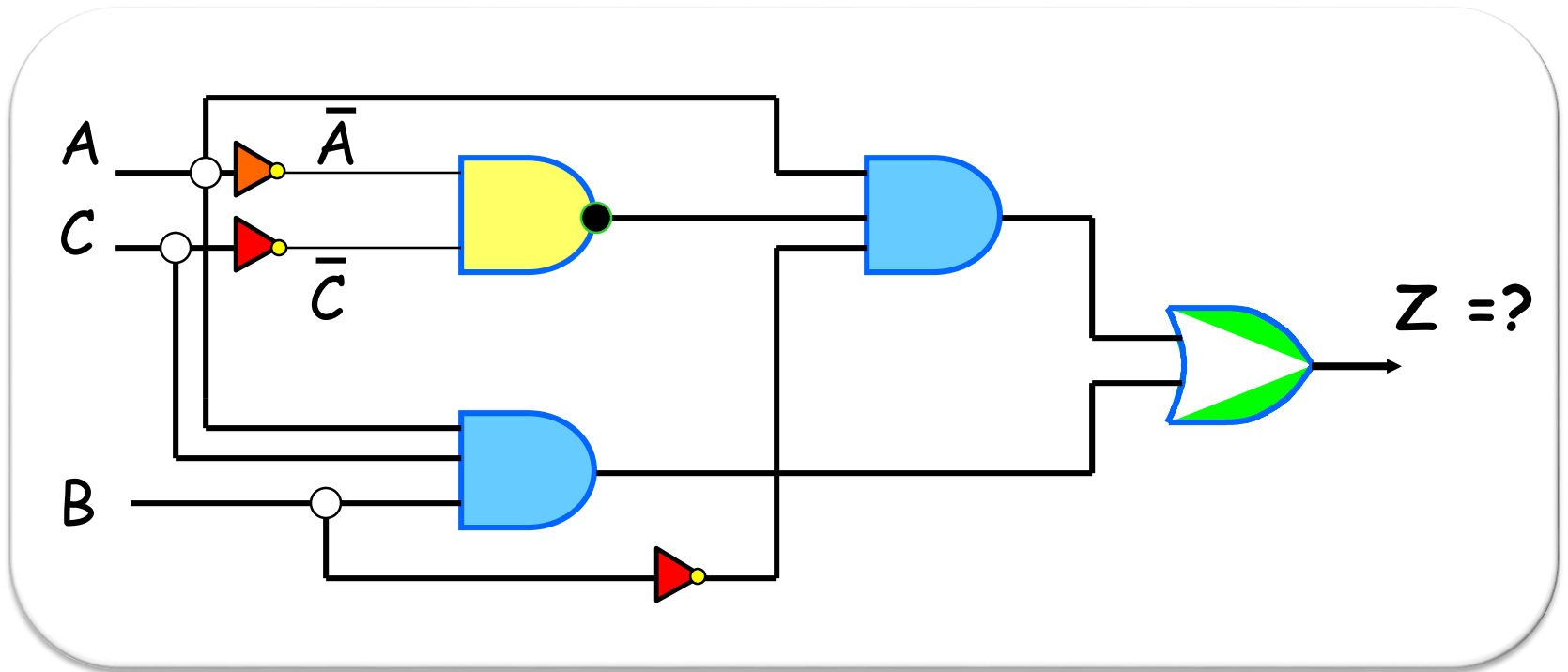


Derive Z

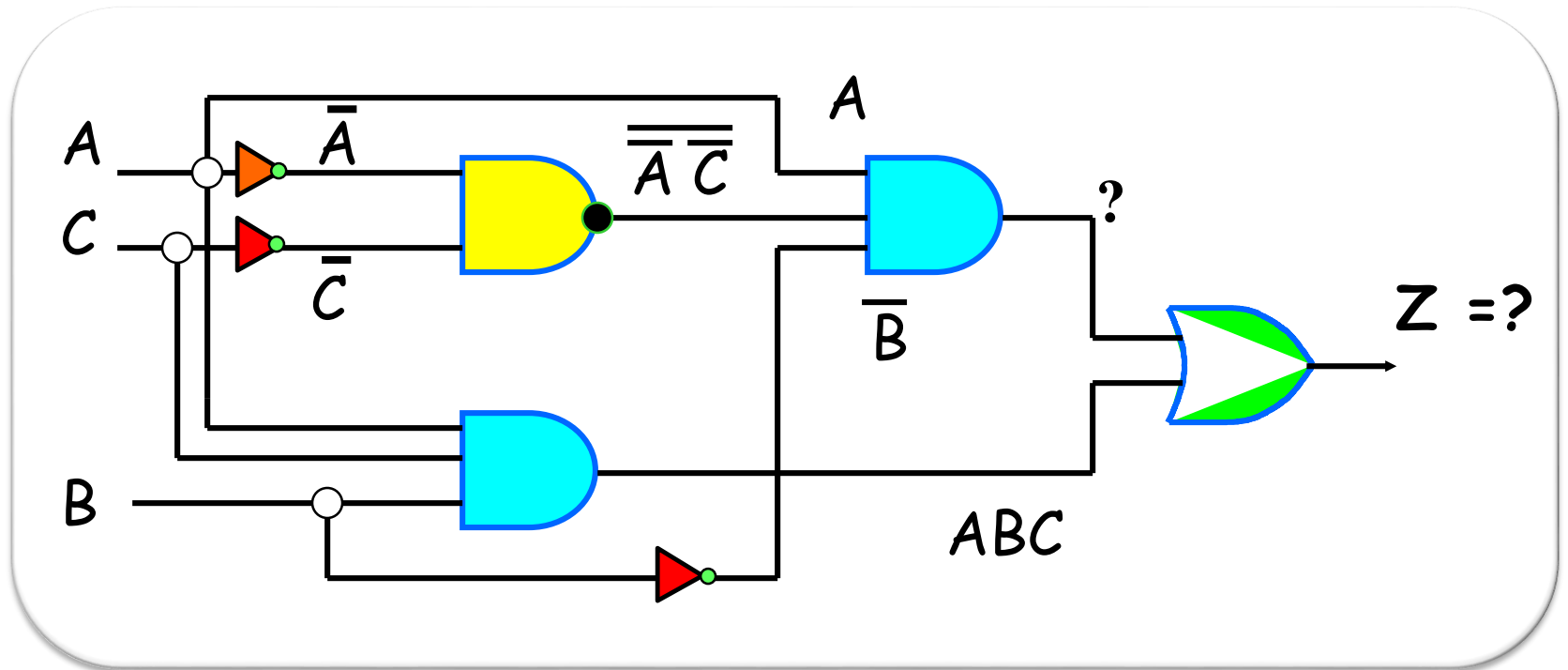

Finally the output expression is ...

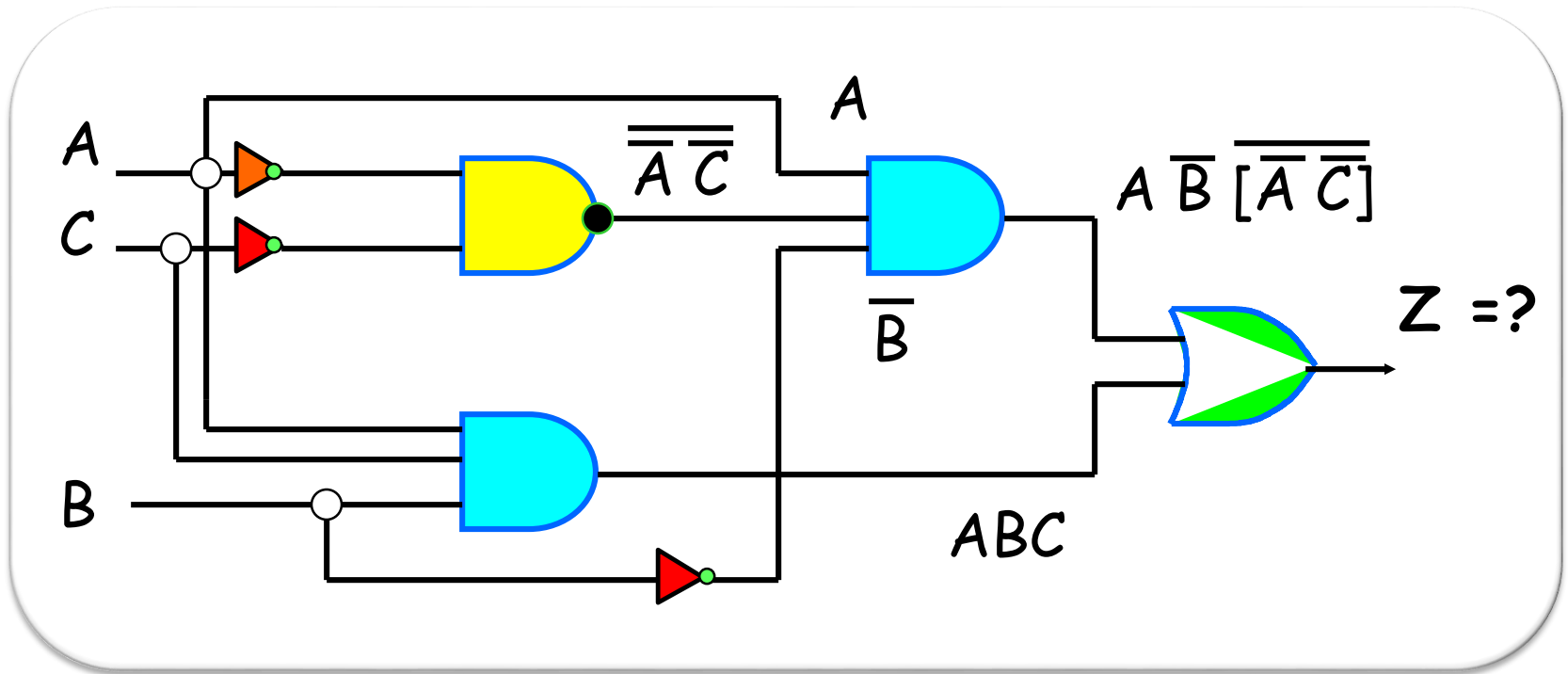

Output expression

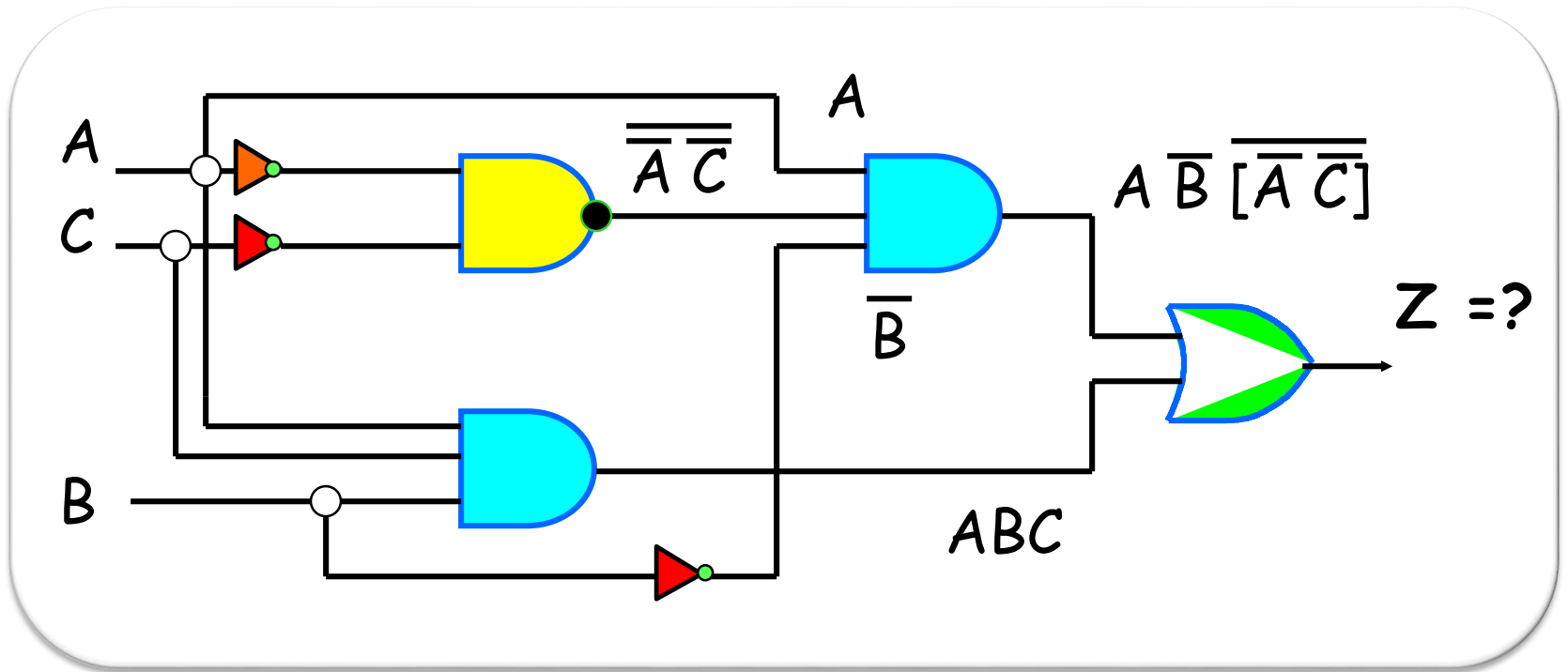

$$Z = ABC + A\bar{B}[\bar{A}\bar{C}]$$

Simplify the Boolean expression

$$Z = A B C + A \overline{B} [\overline{\overline{A} \overline{C}}]$$

- $\overline{x+y} = \overline{x} \bullet \overline{y}$

- $\overline{x \bullet y} = \overline{x} + \overline{y}$

DeMorgan theorem

$$Z = A B C + A \bar{B} [\bar{\bar{A}} \bar{\bar{C}}]$$

$$= A B C + A \bar{B} [\bar{\bar{A}} + \bar{\bar{C}}]$$

- $\overline{x+y} = \bar{x} \bullet \bar{y}$

- $\overline{x \bullet y} = \bar{x} + \bar{y}$

Sum-Of-Products (SOP) form

$$Z = A B C + A \bar{B} [\overline{\bar{A} \bar{C}}]$$

$$= A B C + A \bar{B} [\bar{\bar{A}} + \bar{\bar{C}}]$$

$$= A B C + A \bar{B} A + A \bar{B} C$$

Factor-out: AC

$$Z = A B C + A \bar{B} [\bar{A} \bar{C}]$$

$$= A B C + A \bar{B} [\bar{A} + \bar{C}]$$

$$= ABC + A \bar{B} A + A \bar{B} \bar{C}$$

$$= AC[B + \bar{B}] + A \bar{B}$$

Simplified logic expression

$$Z = A B C + A \bar{B} [\overline{\bar{A} \bar{C}}]$$

$$= ABC + A\bar{B}[\bar{\bar{A}} + \bar{\bar{C}}]$$

$$= ABC + A\bar{B}A + A\bar{B}\bar{C}$$

$$= AC[B + \bar{B}] + A\bar{B}\bar{C}$$

$$= AC + A\bar{B}\bar{C}$$


Implement (gates) the expression

$$Z = AC + A\bar{B}$$

2 Minutes...

Simplified logic circuit (gates)

$$Z = AC + A\bar{B}$$

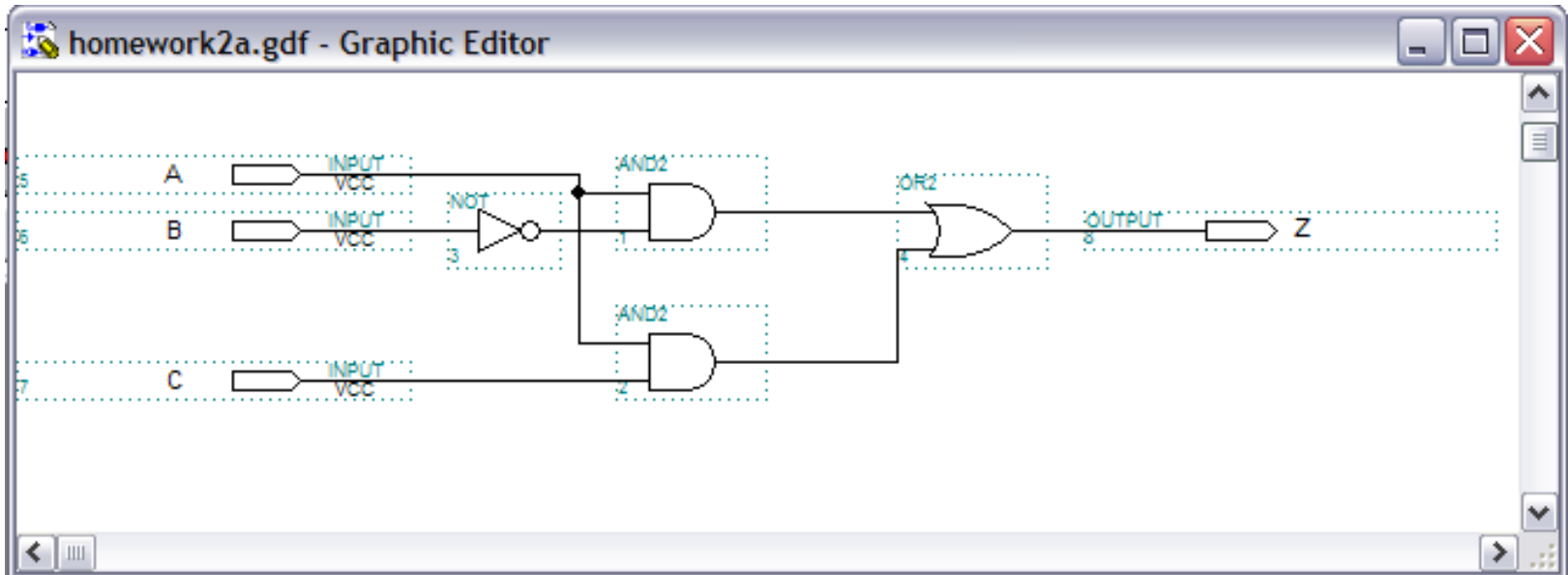

Two-level implementation


VHDL code for: $Z = AC + A\bar{B}$

```
homework2a_vhdl.vhd - Text Editor


entity homework2a_vhdl is
    port (a,b,c: in bit;
          z: out bit);
end homework2a_vhdl;

architecture dataflow of homework2a_vhdl is
begin
    z<=(a and not b) or (a and c);
end dataflow;
```

Line 8 Col 33 INS

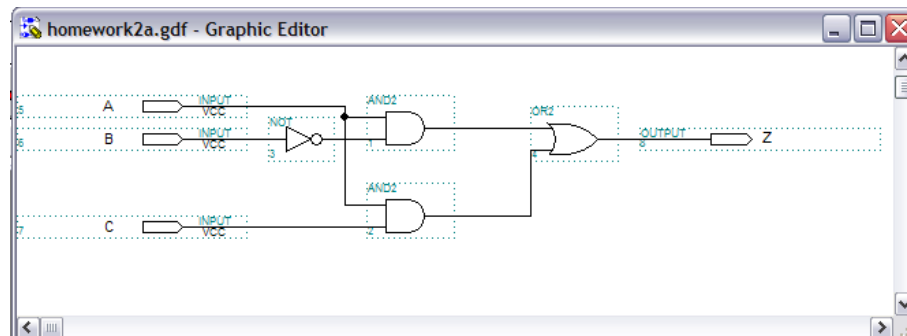

Simulation

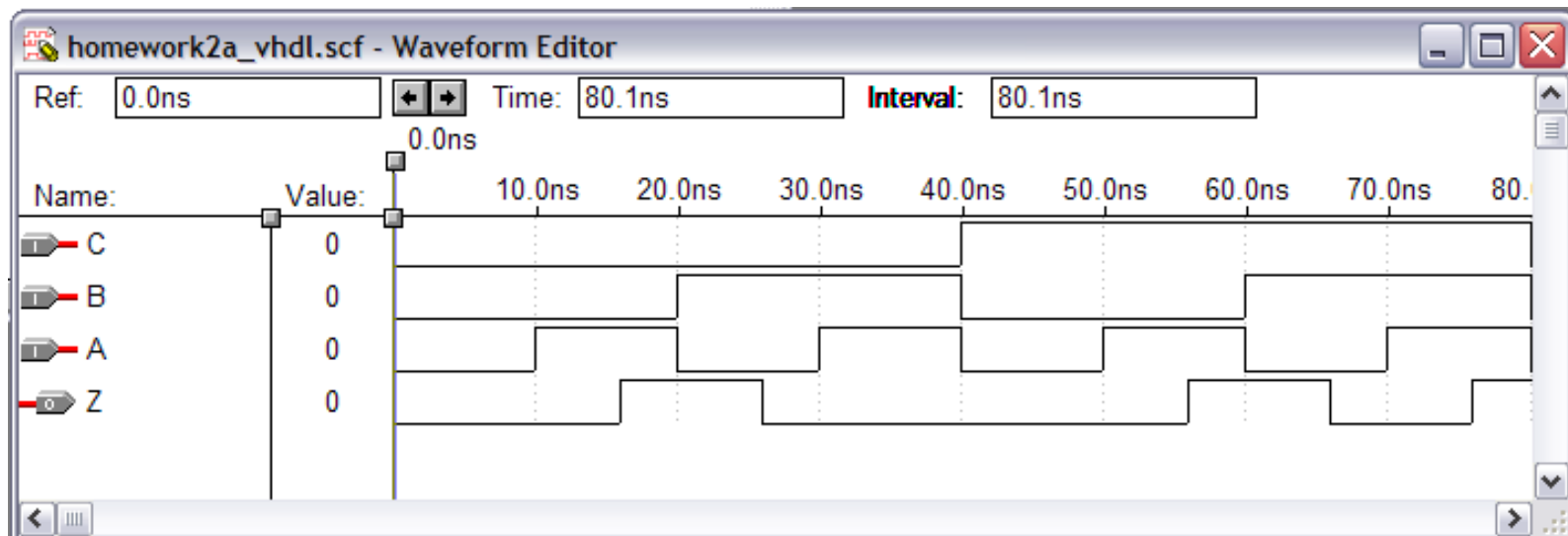

Simplification Examples

Simplify the expression ...

$$ABC + AB\bar{C} + A\bar{B}C$$

New Example

$$ABC + AB\bar{C} + A\bar{B}C$$

$$= AB(C + \bar{C}) + A\bar{B}C$$

$$ABC + AB\bar{C} + A\bar{B}C$$

$$= AB(C + \bar{C}) + A\bar{B}C$$

$$= AB + A\bar{B}C$$

$$ABC + AB\bar{C} + A\bar{B}C$$

$$= AB(C + \bar{C}) + A\bar{B}C$$

$$= AB + A\bar{B}C$$

$$= A(B + \bar{B}C)$$

$$ABC + AB\bar{C} + A\bar{B}C$$

$$= AB(C + \bar{C}) + A\bar{B}C$$

$$= AB + A\bar{B}C$$

$$= A(B + \bar{B}C)$$

$$= A(B + C) = AB + AC$$

$$ABC + AB\bar{C} + A\bar{B}C$$

$$= AB(C + \bar{C}) + A\bar{B}C$$

$$= AB + A\bar{B}C$$

$$= A(B + \bar{B}C)$$

$$= A(B + C) = AB + AC$$

Another proof:

$$ABC + AB\bar{C} + A\bar{B}C$$

$$= AB(C + \bar{C}) + A\bar{B}C$$

$$= AB + A\bar{B}C$$

$$= A(B + \bar{B}C)$$

$$= A(B + C) = AB + AC$$

Another proof:

Because: $A + A = A$

$$ABC + AB\bar{C} + A\bar{B}C$$

$$= AB(C + \bar{C}) + A\bar{B}C$$

$$= AB + A\bar{B}C$$

$$= A(B + \bar{B}C)$$

$$= A(B + C) = AB + AC$$

Another proof:

$$\downarrow$$
$$= ABC + ABC + AB\bar{C} + A\bar{B}C$$

Because: $A + A = A$
(Add another ABC)

$$ABC + AB\bar{C} + A\bar{B}C$$

$$= AB(C + \bar{C}) + A\bar{B}C$$

$$= AB + A\bar{B}C$$

$$= A(B + \bar{B}C)$$

$$= A(B + C) = AB + AC$$

Another proof:

Because: $A + A = A$

$$= ABC + ABC + AB\bar{C} + A\bar{B}C$$

$$= AB(C + \bar{C}) + AC(B + \bar{B})$$

$$ABC + AB\bar{C} + A\bar{B}C$$

$$= AB(C + \bar{C}) + A\bar{B}C$$

$$= AB + A\bar{B}C$$

$$= A(B + \bar{B}C)$$

$$= A(B + C) = AB + AC$$

Another proof:

Because: $A + A = A$

$$= ABC + ABC + AB\bar{C} + A\bar{B}C$$

$$= AB(C + \bar{C}) + AC(B + \bar{B})$$

$$= AB + AC$$

Simplify the expression

$$\bar{A}C[\overline{\bar{A}BD}] + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

- $\overline{x+y} = \bar{x}\bar{y}$

- $\overline{x\bullet y} = \bar{x} + \bar{y}$

New Example

Simplify the expression

$$\begin{aligned} & \bar{A} C [\overline{\bar{A} B D}] + \bar{A} B \bar{C} \bar{D} + A \bar{B} C \\ = & \bar{A} C [\bar{A} + \bar{B} + \bar{D}] + \bar{A} B \bar{C} \bar{D} + A \bar{B} C \end{aligned}$$

Simplify the expression

$$\begin{aligned} & \bar{A}C[\overline{\bar{A}BD}] + \bar{A}B\bar{C}\bar{D} + A\bar{B}C \\ &= \bar{A}C[A + \bar{B} + \bar{D}] + \bar{A}B\bar{C}\bar{D} + A\bar{B}C \\ &= \bar{A}CA + \bar{A}C\bar{B} + \bar{A}C\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}C \end{aligned}$$

Simplify the expression

$$\bar{A} C [\overline{\bar{A} B D}] + \bar{A} B \bar{C} \bar{D} + A \bar{B} C$$

$$= \bar{A} C [A + \bar{B} + \bar{D}] + \bar{A} B \bar{C} \bar{D} + A \bar{B} C$$

$$= \bar{A} C A + \bar{A} C \bar{B} + \bar{A} C \bar{D} + \bar{A} B \bar{C} \bar{D} + A \bar{B} C$$

$$\text{---}$$

$(A A = 0),$

Simplify the expression

$$\bar{A} C [\overline{\bar{A} B D}] + \bar{A} B \bar{C} \bar{D} + A \bar{B} C$$

$$= \bar{A} C [A + \bar{B} + \bar{D}] + \bar{A} B \bar{C} \bar{D} + A \bar{B} C$$

$$= \bar{A} C A + \bar{A} C \bar{B} + \bar{A} C \bar{D} + \bar{A} B \bar{C} \bar{D} + A \bar{B} C$$

\bar{A}
($A A = 0$), take 2nd with 5th and 3rd with 4th terms.

Simplify the expression

$$\begin{aligned}& \bar{A} C [\overline{\bar{A} B D}] + \bar{A} B \bar{C} \bar{D} + A \bar{B} C \\&= \bar{A} C [A + \bar{B} + \bar{D}] + \bar{A} B \bar{C} \bar{D} + A \bar{B} C \\&= \bar{A} C A + \bar{A} C \bar{B} + \bar{A} C \bar{D} + \bar{A} B \bar{C} \bar{D} + A \bar{B} C\end{aligned}$$

($A \bar{A} = 0$), take 2nd with 5th and 3rd with 4th terms.

$$= \bar{B} C [A + \bar{A}] + \bar{A} \bar{D} [C + B \bar{C}]$$

Simplify the expression

$$\bar{A}C[\overline{\bar{A}BD}] + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

$$= \bar{A}C[A + \bar{B} + \bar{D}] + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

$$= \bar{A}CA + \bar{A}C\bar{B} + \bar{A}C\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

\bar{A}
($A\bar{A} = 0$), take 2nd with 5th and 3rd with 4th terms.

$$= \bar{B}C[A + \bar{A}] + \bar{A}\bar{D}[C + B\bar{C}]$$

$$= \bar{B}C + \bar{A}\bar{D}[C + B]$$

Final result

$$\bar{A} C [\overline{\bar{A} B D}] + \bar{A} B \bar{C} \bar{D} + A \bar{B} C$$

$$= \bar{A} C [A + \bar{B} + \bar{D}] + \bar{A} B \bar{C} \bar{D} + A \bar{B} C$$

$$= \bar{A} C A + \bar{A} C \bar{B} + \bar{A} C \bar{D} + \bar{A} B \bar{C} \bar{D} + A \bar{B} C$$

$\bar{A} A = 0$, take 2nd with 5th and 3rd with 4th terms.

$$= \bar{B} C [A + \bar{A}] + \bar{A} \bar{D} [C + B \bar{C}]$$

$$= \bar{B} C + \bar{A} \bar{D} [C + B] = \bar{B} C + \bar{A} \bar{D} C + \bar{A} \bar{D} B$$

Simplify the expression

$$(\overline{A} + B)(A + B + D)\overline{D}$$

New Example

Simplify the expression

$$(\overline{A} + B)(A + B + D)\overline{D}$$

$$= [\overline{A}A + \overline{A}B + \overline{A}D + BA + BB + BD]\overline{D}$$

Simplify the expression

$$(\bar{A} + B)(A + B + D)\bar{D}$$

$$= [\bar{A}A + \bar{A}B + \bar{A}D + BA + BB + BD]\bar{D}$$

$$= \bar{A}A\bar{D} + \bar{A}B\bar{D} + \bar{A}D\bar{D} + BA\bar{D} + BB\bar{D} + BD\bar{D}$$

Simplify the expression

$$(\overline{A} + B)(A + B + D)\overline{D}$$

$$= [\overline{A}A + \overline{A}B + \overline{A}D + BA + BB + BD]\overline{D}$$

$$= \overline{A}A\overline{D} + \overline{A}B\overline{D} + \overline{A}D\overline{D} + BA\overline{D} + BB\overline{D} + BD\overline{D}$$

$$= 0 + \overline{A}B\overline{D} + 0 + BA\overline{D} + B\overline{D} + 0$$

Simplify the expression

$$\begin{aligned}& (\bar{A} + B)(A + B + D)\bar{D} \\&= [\bar{A}A + \bar{A}B + \bar{A}D + BA + BB + BD]\bar{D} \\&= \bar{A}A\bar{D} + \bar{A}B\bar{D} + \bar{A}D\bar{D} + BA\bar{D} + BB\bar{D} + BD\bar{D} \\&= 0 + \bar{A}B\bar{D} + 0 + BA\bar{D} + B\bar{D} + 0 \\&= B\bar{D}[\bar{A} + A + 1]\end{aligned}$$

Simplify the expression

$$\begin{aligned}& (\bar{A} + B)(A + B + D)\bar{D} \\&= [\bar{A}A + \bar{A}B + \bar{A}D + BA + BB + BD]\bar{D} \\&= \bar{A}A\bar{D} + \bar{A}B\bar{D} + \bar{A}D\bar{D} + BA\bar{D} + BB\bar{D} + BD\bar{D} \\&= 0 + \bar{A}B\bar{D} + 0 + BA\bar{D} + B\bar{D} + 0 \\&= B\bar{D}[\bar{A} + A + 1] \\&= B\bar{D}[1 + 1]\end{aligned}$$

Final result

$$\begin{aligned}& (\bar{A} + B)(A + B + D)\bar{D} \\&= [\bar{A}A + \bar{A}B + \bar{A}D + BA + BB + BD]\bar{D} \\&= \bar{A}A\bar{D} + \bar{A}B\bar{D} + \bar{A}D\bar{D} + BA\bar{D} + BB\bar{D} + BD\bar{D} \\&= 0 + \bar{A}B\bar{D} + 0 + BA\bar{D} + B\bar{D} + 0 \\&= B\bar{D}[\bar{A} + A + 1] \\&= B\bar{D}[1 + 1] \\&= B\bar{D}(1) = B\bar{D} \quad \leftarrow\end{aligned}$$

Another example


Given: $(\bar{A}+B)(\bar{B}+A)$

1. Implement using basic (AND, OR, NOT) gates
2. Simplify
3. Implement the simplified expression

New Example

1. First implementation

$$(\bar{A}+B)(\bar{B}+A)$$

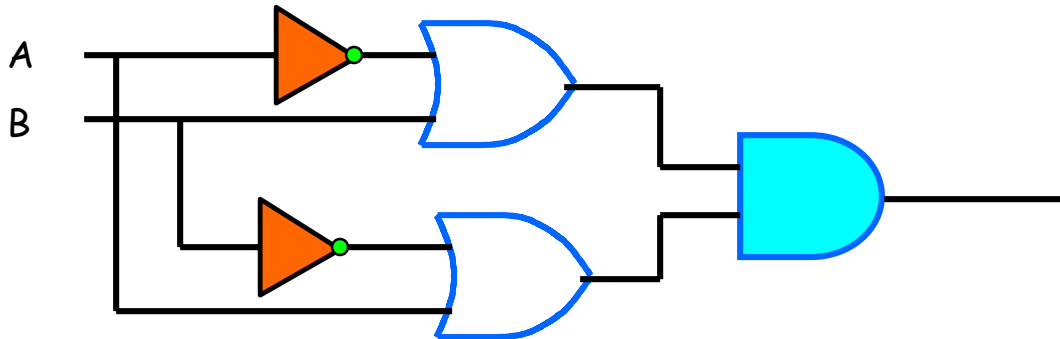


2. Simplify



$$\begin{aligned}(\bar{A}+B)(\bar{B}+A) &= \bar{A}\bar{B} + \bar{A}A + \bar{B}B + BA \\ &= \bar{A}\bar{B} + AB\end{aligned}$$

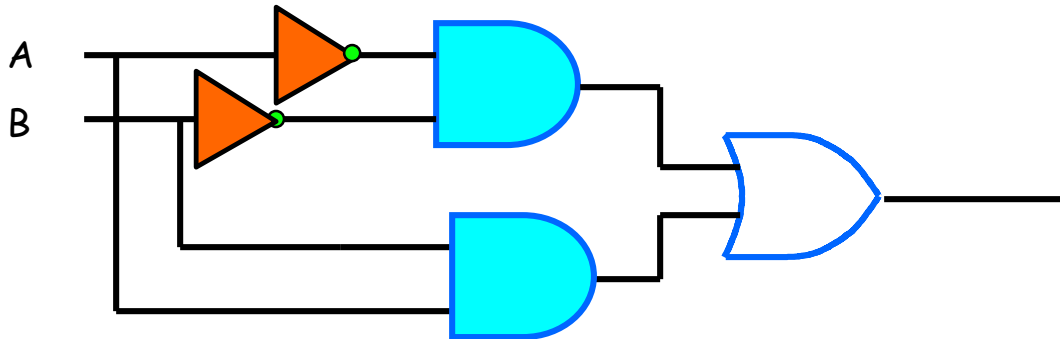3. Second implementation

$$(\bar{A}+B)(\bar{B}+A) = \bar{A}\bar{B} + \bar{A}A + \bar{B}B + BA$$
$$= \bar{A}\bar{B} + AB$$



Both implementations are equivalent

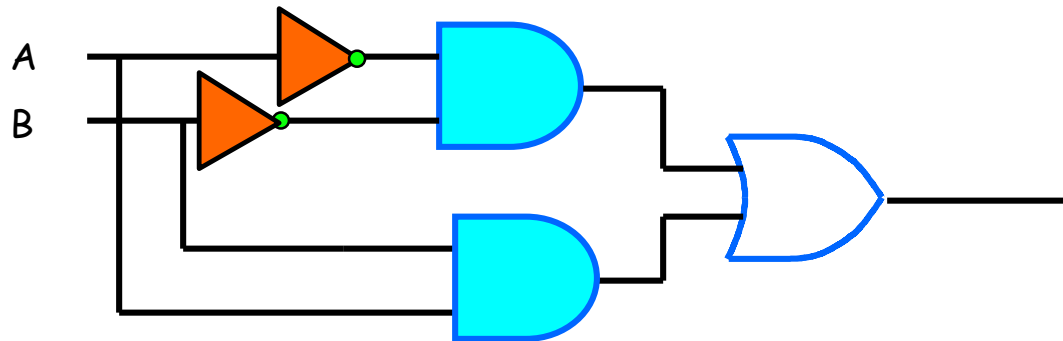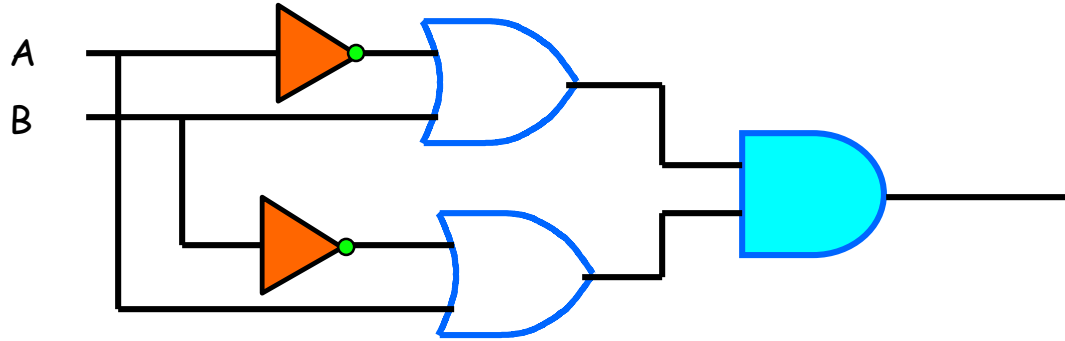

Simplify the expression

$$Z = A\bar{C}\bar{D} + \bar{A}BD + A\bar{B}CD$$

New Example

$$Z = Z$$

$$Z = A\bar{C}\bar{D} + \bar{A}BD + A\bar{B}CD$$

Can not be simplified

Therefore ... 3 cases ...

- The result is a simplified expression
- The result is an equivalent expression
- The expression can not be simplified.