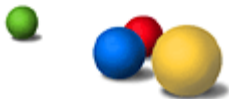


Truth Tables

Binary Logic

What do we know up to now?

- We know how to derive an output binary expression from a given ...
- ... Logic Circuit.




Today ...

- We will learn how to derive an output binary expression from ...
- ... a Truth Table.


Truth Table

Given a Truth
Table


Output expressions ...

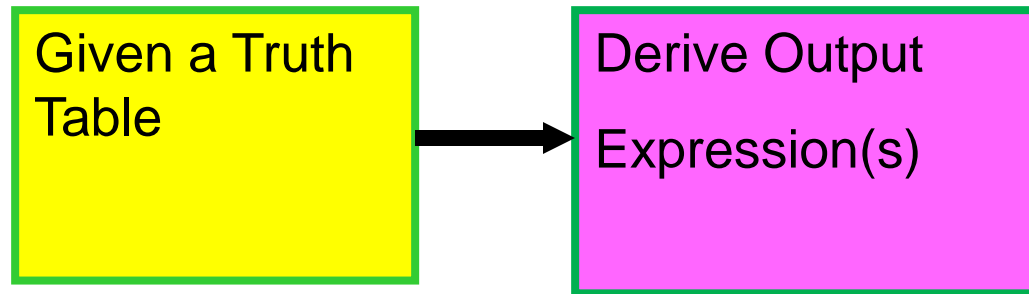


Simplify

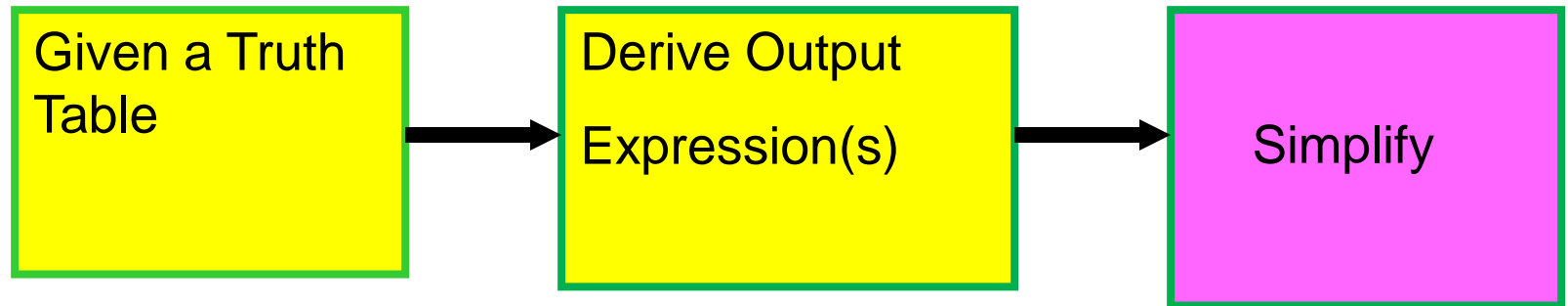

Gates

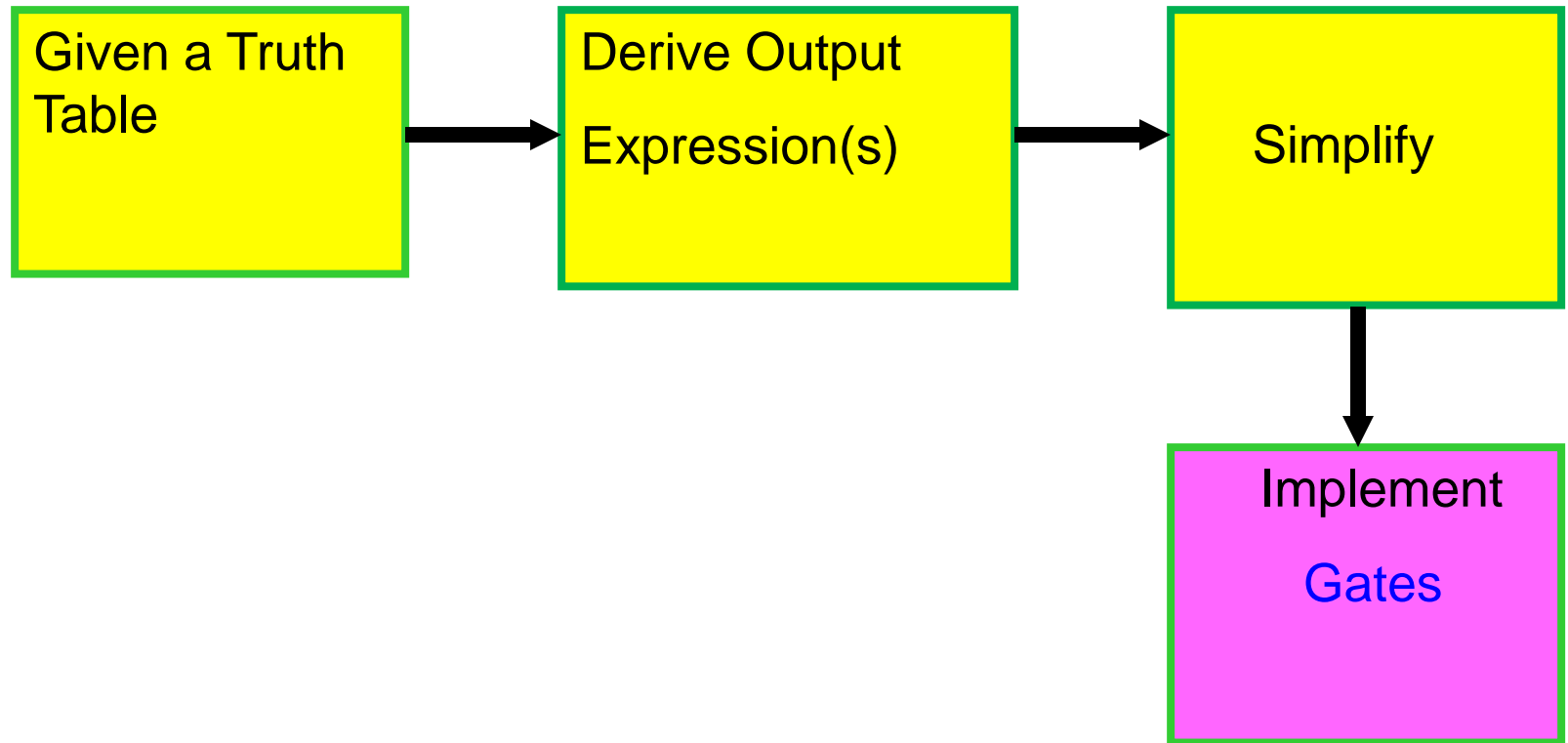

Truth Table → Simplified Circuit

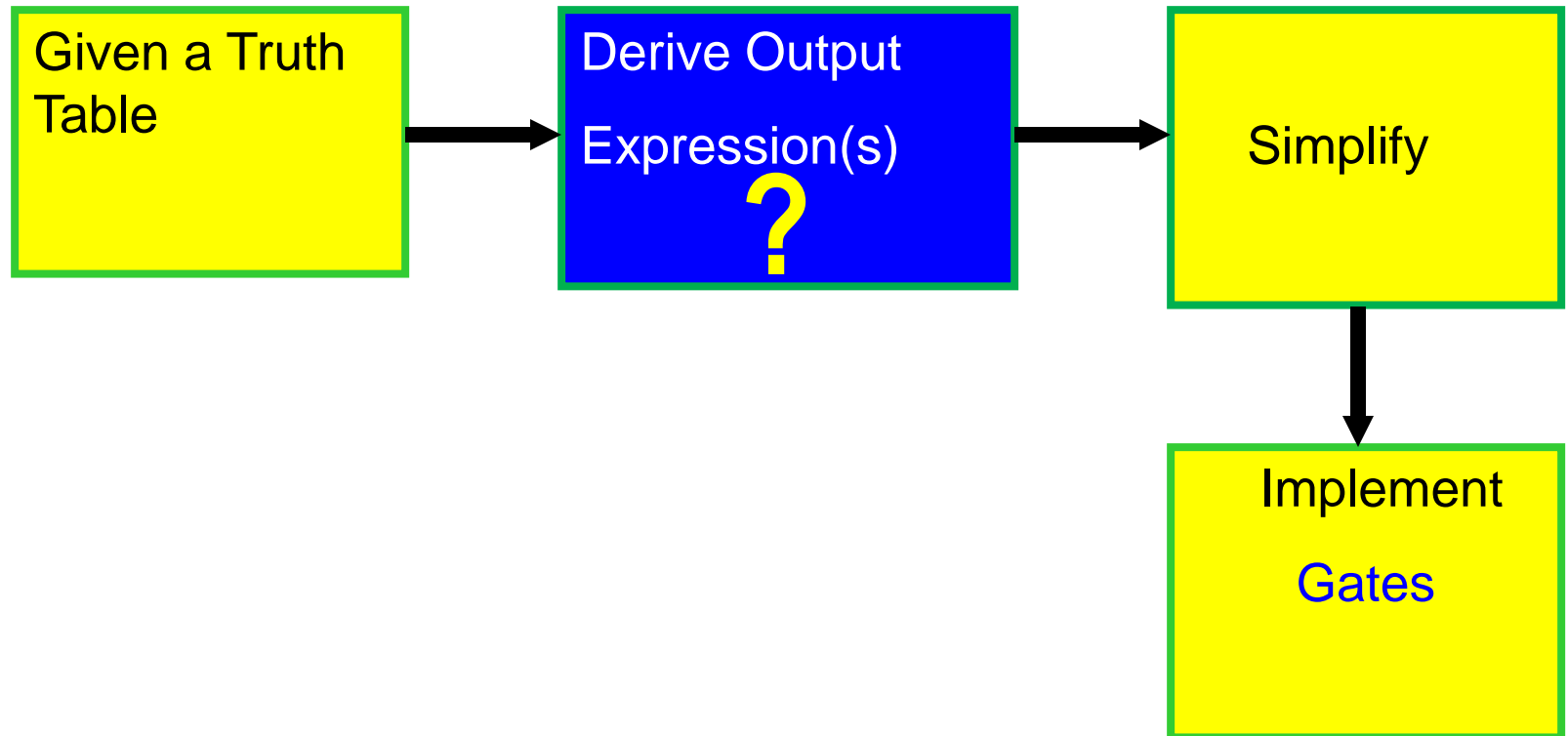

How can we derive an output expression from a Truth Table?

Truth Table → Output logic expression(s)

Algorithm:

1. Write an AND term (Boolean expression) for each case in the truth table the output is logic 1
2. All the AND terms are then ORed together to produce the final output expression.

Example: Derive the Truth Table

Word Problem:

For a three-input (A,B,C) binary system. If we have more than one high(1) inputs the output (X) is 1, otherwise it is zero(0).

Example: Truth Table

A	B	C	X
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Word Problem:

For a three-input (A,B,C) binary system. If we have more than one high(1) inputs the output (X) is 1, otherwise it is zero(0).

Example: Truth Table: *Done*



A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Word Problem:

For a three-input (A,B,C) binary system. If we have more than one high(1) inputs the output (X) is 1, otherwise it is zero(0).

Example: Write Terms for $X = 1$

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$\bar{A} B C$

$A \bar{B} C$

$A B \bar{C}$

$A B C$

Example: Output expression

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$\bar{A} B C$

$A \bar{B} C$

$A B \bar{C}$

$A B C$

$$X = \bar{A} B C + A \bar{B} C + A B \bar{C} + A B C$$

SOP = Sum-Of-Products

Example: Simplify

$$X = \bar{A} B C + A \bar{B} C + A B \bar{C} + A B C$$

Lets simplify...

5 Minutes...

Simplification using Boolean Theorems

$$X = \bar{A} B C + A \bar{B} C + A B \bar{C} + A B C$$

$$= \bar{A} B C + A \bar{B} C + A B \bar{C} + A B C + A B C + A B C$$

Note// $A B C = A B C + A B C + A B C$

Simplification using Boolean Theorems


$$\begin{aligned} X &= \overline{A} B C + A \overline{B} C + A B \overline{C} + A B C \\ &= \overline{A} B C + \overline{A} B C + A \overline{B} C + A \overline{B} C + A B \overline{C} + A B \overline{C} + A B C + A B C \end{aligned}$$

Result

$$\begin{aligned} X &= \overline{A} B C + A \overline{B} C + A B \overline{C} + A B C \\ &= \overline{A} B C + \overline{A} B C + A \overline{B} C + A \overline{B} C + A B \overline{C} + A B C \\ &= B C (\overline{A} + A) + A C (\overline{B} + B) + A B (\overline{C} + C) \\ &= B C + A C + A B \end{aligned}$$



Implementation: Logic Circuit

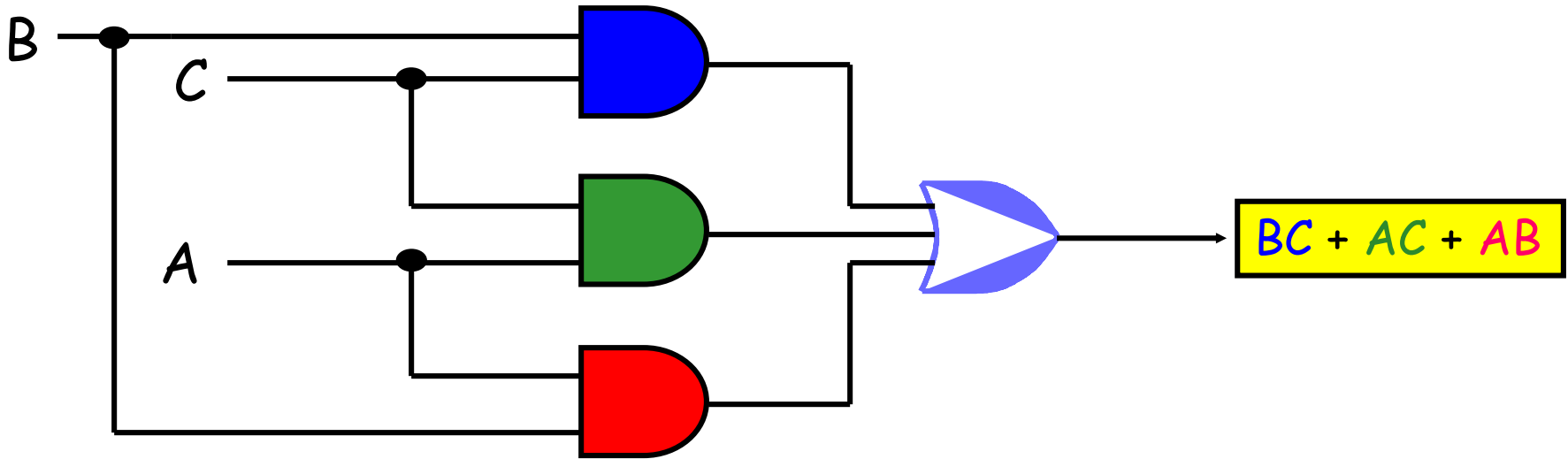

Conclusion

- The algebraic simplification procedure is very **unsystematic** ... not easy to be implemented using a programming language
- Next a more systematic simplification procedure is presented.