

# Binary Adders




# SoC & CPU

- A system-on-a-chip (**SoC**) contains a **CPU** (Central Processing Unit), GPU (Graphics Processing Unit), memory, USB controller, power management circuits, wireless radios (WiFi, 3G, 4G LTE, 5G ...), ...
- A **CPU** contains: ALU (Arithmetic Logic Unit), CU (Control Unit), ...


 
# Binary Adder

- The binary Adder is the main component of the Arithmetic Logic Unit (ALU)
- Adders are also used to calculate addresses, table indices, increment and decrement operators...



# Problem: 1-bit binary Adder

- Design a binary logic circuit to **ADD** 2-binary digits: (a, b) ... (This is 1-bit Adder).

1-bit Addition

$$\begin{array}{r} a \\ + b \\ \hline \end{array}$$

1-bit Addition

$$\begin{array}{r} 1 \\ + 0 \\ \hline \end{array}$$

# 1-bit Adder: Truth table

---

- How many inputs = ?
- How many outputs = ?

# 1-bit Adder: Truth table

- How many inputs = 2
- How many outputs = 2

a	b	c	s
0	0		
0	1		
1	0		
1	1		

# 1-bit Adder: Truth table

---

a	b	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# 1-bit Adder: Carry logic equation

a	b	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Therefore,

$$C = a b$$



# 1-bit Adder: Sum logic equation

a	b	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Therefore,

$$C = a b$$

$$S = \bar{a} b + a \bar{b}$$


$$= a \oplus b$$


# 1-bit Adder: Logic circuit

$$C = a b$$

$$S = \overline{a} b + a \overline{b}$$

$$= a \oplus b$$

 

 


# 1-bit Adder: Graphical Symbol

$$C = a b$$


$$S = \bar{a} b + a \bar{b}$$

$$= a \oplus b$$

 

# Example-1


---

 

# Example-1

$$\begin{array}{r} 1 \\ + 0 \\ \hline \end{array}$$

0 is the **carry** and 1 is the **sum**

 

# Example-2

---

$$\begin{array}{r} 11 \\ + 01 \\ \hline ?? \end{array}$$

## Example-2: Addition

---


$$\begin{array}{r} 1 \\ 11 \\ + 01 \\ \hline 100 \end{array}$$

What about the logic circuit ?



 
## Example-2: Logic circuit

$$\begin{array}{r} \textcolor{red}{1} \\ 1\textcolor{violet}{1} \\ + \textcolor{teal}{01} \\ \hline 100 \end{array}$$


 
## Example-2: Logic circuit


$$\begin{array}{r} \textcolor{red}{1} \\ 1\textcolor{violet}{1} \\ + \textcolor{teal}{01} \\ \hline 100 \end{array}$$



HA-2 should have 3 inputs in order to add the carry  $\textcolor{red}{1}$  (of the HA-1) + 1 +  $\textcolor{teal}{0}$
 
## Example-2: Logic circuit


$$\begin{array}{r} 1 \\ 11 \\ + 01 \\ \hline 100 \end{array}$$



Therefore we need logic adders with three inputs = ?
 
# Full-Adder ?


$$\begin{array}{r} 1 \\ 11 \\ + 01 \\ \hline 100 \end{array}$$



Therefore we need logic adders with three inputs = **Full Adders**
 
# Result

$$\begin{array}{r} 1 \\ 11 \\ + 01 \\ \hline 100 \end{array}$$




Therefore we need logic adders with three inputs = **Full Adders**

# Design a Full Adder

3 inputs and 2 outputs

# Full-Adder

 

# Full-Adder: Truth table

$C_i$	$x_i$	$y_i$	$C_{i+1}$	$S_i$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		



# Full-Adder: Truth table

$C_i$	$x_i$	$y_i$	$C_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

# Full-Adder: Truth table

$C_i$	$x_i$	$y_i$	$C_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# Full-Adder: Logic equations

$C_i$	$x_i$	$y_i$	$C_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$C_{i+1} = \overline{C_i} x_i y_i + C_i \overline{x_i} y_i + C_i x_i \overline{y_i} + C_i x_i y_i$$

$$S_i = \overline{C_i} \overline{x_i} y_i + \overline{C_i} x_i \overline{y_i} + C_i \overline{x_i} \overline{y_i} + C_i x_i y_i$$

# Full-Adder: Simplification: $C_{i+1}$

Carry

# Full-Adder: Simplification ... $C_{i+1}$

---

$$C_{i+1} = \overline{C_i} x_i y_i + C_i \overline{x_i} y_i + C_i x_i \overline{y_i} + C_i x_i y_i$$

# Full-Adder: Simplification ... $C_{i+1}$

---

$$\begin{aligned} C_{i+1} &= \overline{C_i} x_i y_i + C_i \overline{x_i} y_i + C_i x_i \overline{y_i} + C_i x_i y_i \\ &= C_i (\overline{x_i} y_i + x_i \overline{y_i}) + x_i y_i (\overline{C_i} + C_i) \end{aligned}$$

# Full-Adder: Simplification ... $C_{i+1}$

$$\begin{aligned}C_{i+1} &= \overline{C_i} x_i y_i + C_i \overline{x_i} y_i + C_i x_i \overline{y_i} + C_i x_i y_i \\&= C_i(\overline{x_i} y_i + x_i \overline{y_i}) + x_i y_i (\overline{C_i} + C_i)\end{aligned}$$

$$C_{i+1} = C_i(x_i \oplus y_i) + x_i y_i$$

# Full-Adder: Simplification: $S_i$

Sum



# Simplify: $S_i$

---

$$S_i = \overline{C_i} \overline{x_i} y_i + \overline{C_i} x_i \overline{y_i} + C_i \overline{x_i} \overline{y_i} + C_i x_i y_i$$

Simplify:  $S_i$

---

$$S_i = \underbrace{\bar{C}_i \bar{x}_i y_i + \bar{C}_i x_i \bar{y}_i}_{\text{blue}} + \underbrace{C_i \bar{x}_i \bar{y}_i + C_i x_i y_i}_{\text{red}}$$

# Simplify: $S_i$

$$S_i = \underbrace{\bar{C}_i \bar{x}_i y_i + \bar{C}_i x_i \bar{y}_i}_{\text{XOR}} + \underbrace{C_i \bar{x}_i \bar{y}_i + C_i x_i y_i}_{\text{AND}}$$

$$S_i = \bar{C}_i (x_i \oplus y_i) + C_i (\bar{x}_i \bar{y}_i + x_i y_i)$$

Simplify:  $S_i$

$$S_i = \underbrace{\bar{C}_i \bar{x}_i y_i + \bar{C}_i x_i \bar{y}_i}_{\text{}} + \underbrace{C_i \bar{x}_i \bar{y}_i + C_i x_i y_i}_{\text{}}$$

$$S_i = \bar{C}_i (x_i \oplus y_i) + C_i (\bar{x}_i \bar{y}_i + x_i y_i)$$


$$S_i = \underbrace{\bar{C}_i (x_i \oplus y_i)}_{\text{}} + \underbrace{C_i \overline{(x_i \oplus y_i)}}_{\text{}}$$

# Done...

$$S_i = \underbrace{\bar{C}_i \bar{x}_i y_i + \bar{C}_i x_i \bar{y}_i}_{\text{}} + \underbrace{C_i \bar{x}_i \bar{y}_i + C_i x_i y_i}_{\text{}} = C_i \oplus x_i \oplus y_i$$

$$S_i = \bar{C}_i (x_i \oplus y_i) + C_i (\bar{x}_i \bar{y}_i + x_i y_i)$$
 
$$S_i = \underbrace{\bar{C}_i (x_i \oplus y_i)}_{\text{}} + C_i \underbrace{(\bar{x}_i \bar{y}_i + x_i y_i)}_{\text{}}$$



# K-maps and XOR gates ...

---

$$S_i = \underbrace{\bar{C}_i \bar{x}_i y_i + \bar{C}_i x_i \bar{y}_i}_{\text{XOR}} + \underbrace{C_i \bar{x}_i \bar{y}_i + C_i x_i y_i}_{\text{XOR}}$$

What is the K-map of the above logical expression?

# All equivalent ... “diagonal” looping ...

$$S_i = \bar{C}_i \bar{x}_i y_i + \bar{C}_i x_i \bar{y}_i + C_i \bar{x}_i \bar{y}_i + C_i x_i y_i = C_i \oplus x_i \oplus y_i$$

$C_i x_i \backslash y_i$	0	1
00		1
01	1	
11		1
10	1	

$C_i \oplus x_i \oplus y_i$

# Finally ... Full-adder equations


$$C_{i+1} = C_i(x_i \oplus y_i) + x_i y_i$$

$$S_i = C_i \oplus x_i \oplus y_i$$



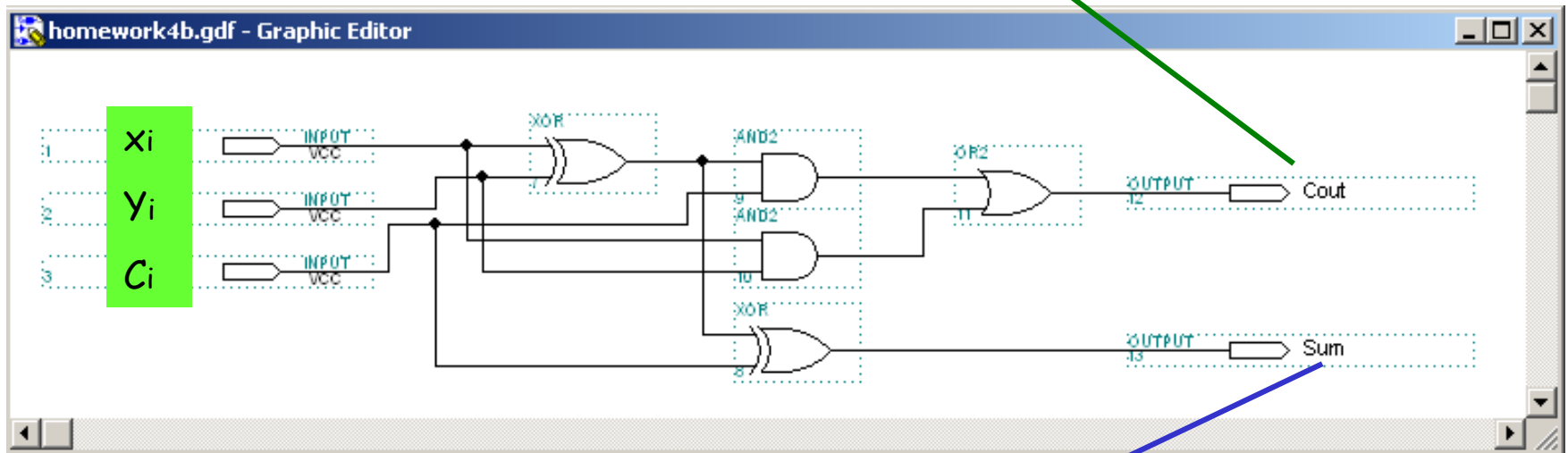
# Full-adder ... circuit

$$C_{i+1} = C_i(x_i \oplus y_i) + x_i y_i$$




$$S_i = C_i \oplus x_i \oplus y_i$$

# 1-bit Full-Adder (3-inputs, 2-outputs)

 

# 4-Bit Adder

# 4-bit Adder

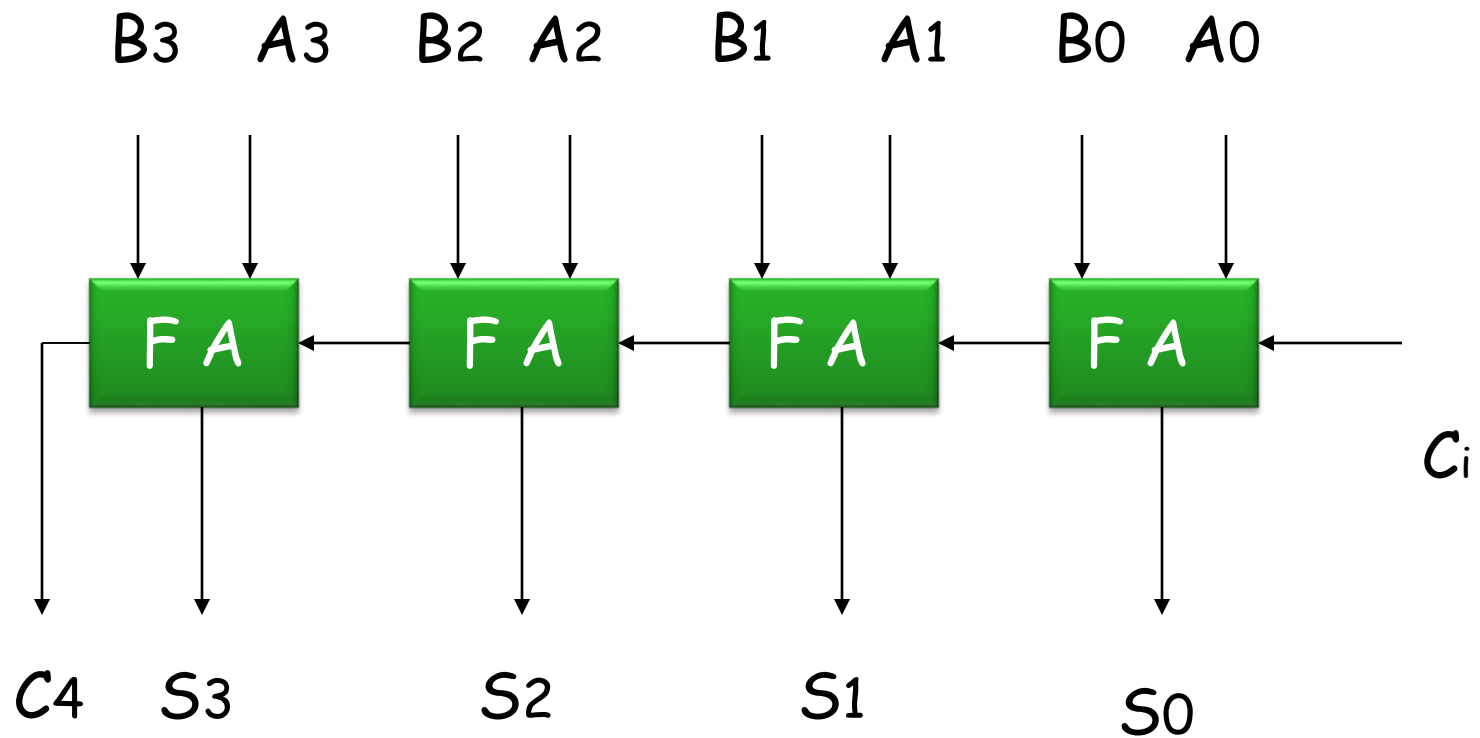

## 4-Bit Adder Example


Add:  $A+B$

---


- $0111 = A$

- $1010 = B$

# 4-bit Adder example

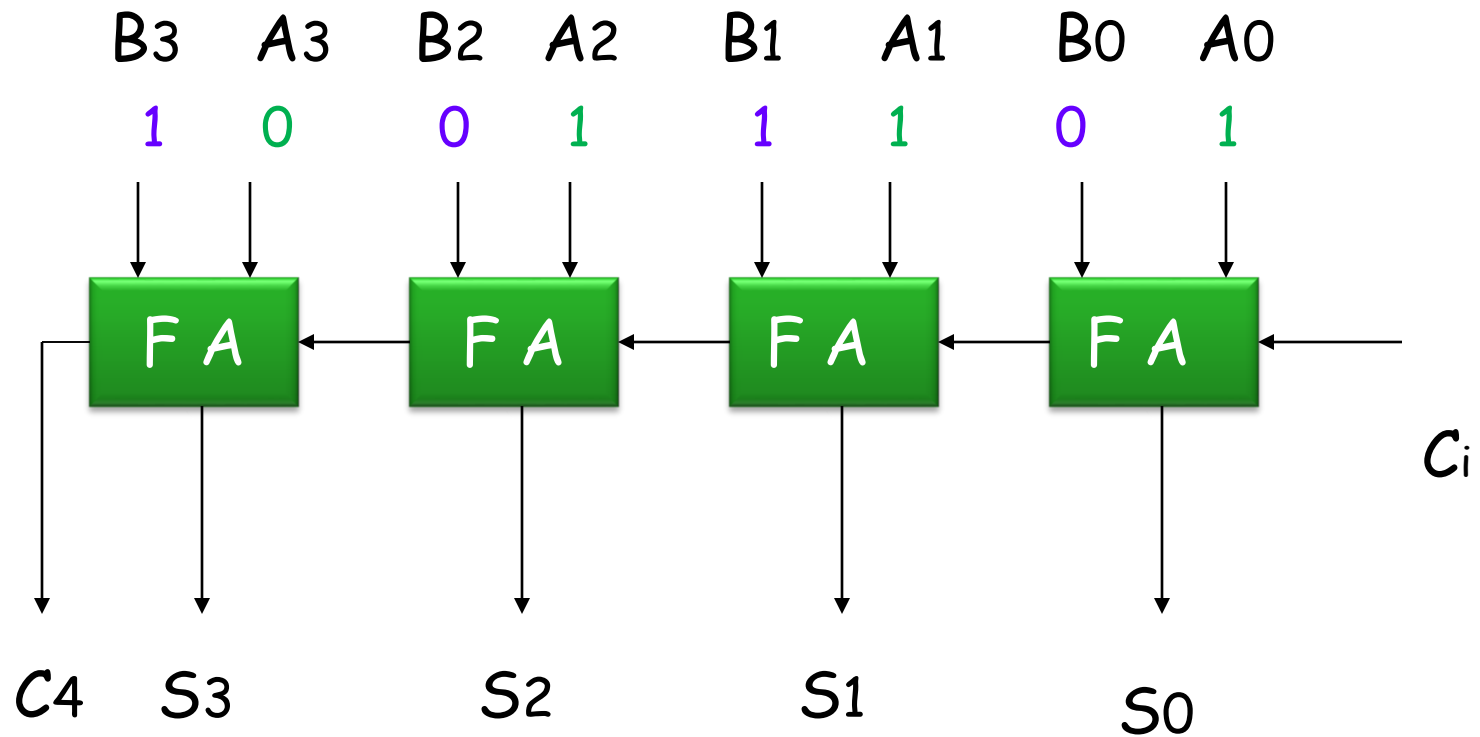


# 4-bit Adder example

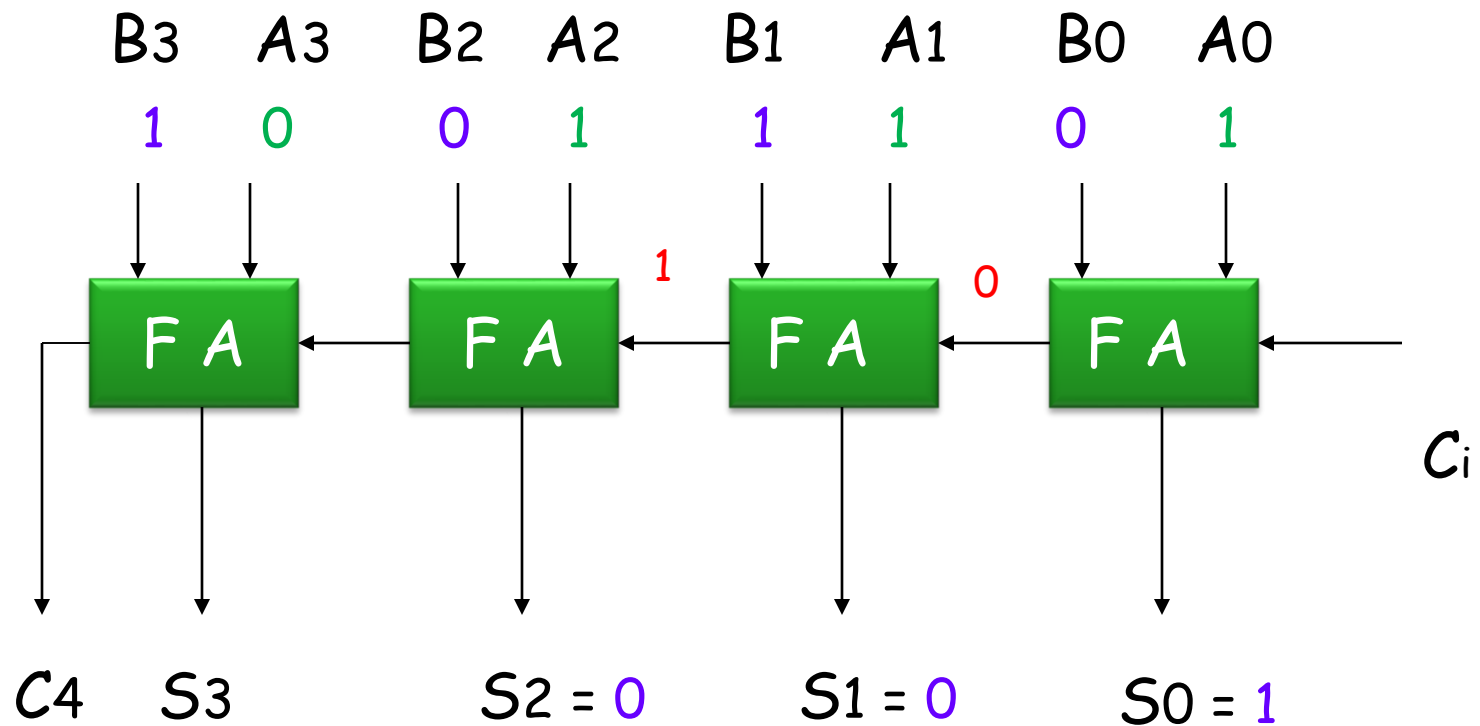




# 4-bit Adder example

 


# 4-bit Carry Ripple Adder (CRA)

 

The carry "ripples" through the full adders

# 4-bit CRA: Compact form

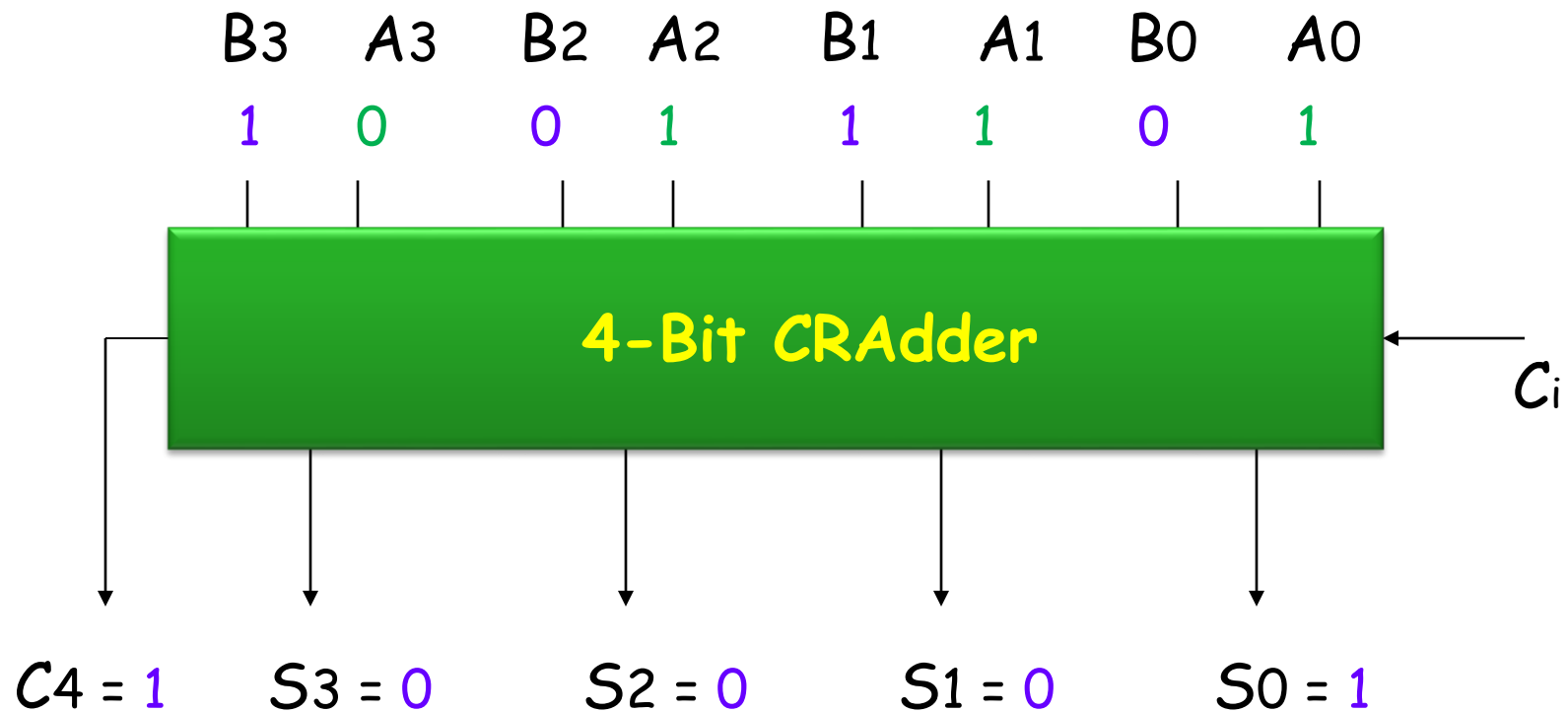


Overflow ...the result is 5-bits and the input is 4-bits

# Overflow ...


---

- When the addition result has an extra bit (5-bits) than the inputs (4-bits), this is called **overflow**
- Overflow occurs in case where the carry-out is one (unsigned numbers addition)
- Overflow is a hardware related “problem”...


# 4-bit CRA ...

 

# 4-bit CRA ... circuit

 
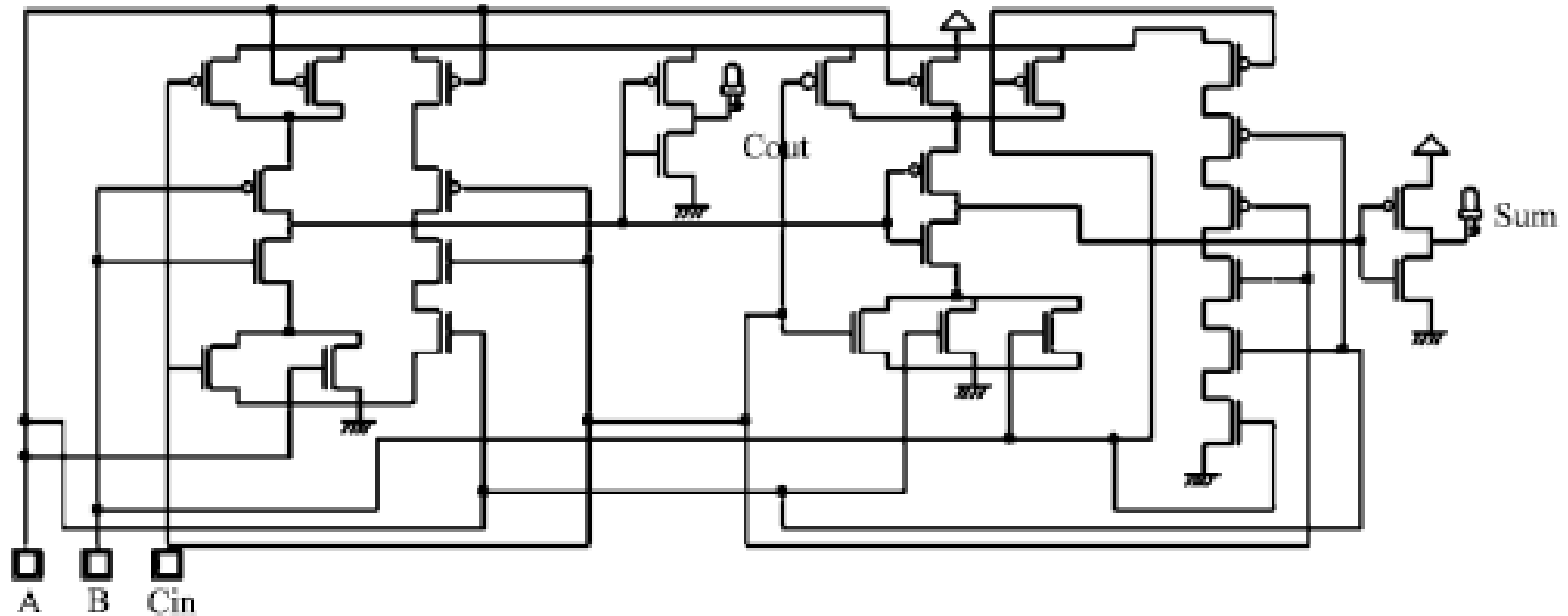
# CMOS Carry Ripple Adder, with transistors



$$\text{Sum} = A \oplus B \oplus \text{Cin}$$

$$\text{Cout} = A.B + \text{Cin}.(A \oplus B)$$

# High Speed CMOS logic 4-bit Binary Full Adder

---



CD74HC283