

Multiplexer (MUX)

1-bit ALU design


Multiplexer

- A logic circuit that accepts data from more than one inputs and routes the data to a **SINGLE output**.



16-Channel Analog Multiplexer/Demultiplexer

Multiplexer: Block Diagram

 


Data inputs = data = 2^n

Select lines = address lines = n

Output = 1

Multiplexer: Block Diagram

 


Data inputs = data = 2^n

Select lines = address lines = n

Output = 1

Multiplexer: Block Diagram

 

Data inputs = data = 2^n

Select lines = address lines = n

Output = 1


Multiplexer: Characteristic

The multiplexer is programmed through the select inputs to establish a connection between the output and the data inputs.

Design a 2-1 Multiplexer

Inputs = 2


Output = 1

 

Design a 2-1 Multiplexer

Inputs = 2


Output = 1

 

Therefore we need $n=1$ select line.

Logic: Truth Table


S	D1	D0	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 

If $S = 0 \Rightarrow Y = D0$
If $S = 1 \Rightarrow Y = D1$

Logic: Truth Table


S	D1	D0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 

If $S = 0 \Rightarrow Y = D0$
If $S = 1$

Logic: Truth Table

S	D1	D0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

If $S = 0 \Rightarrow Y = D0$
If $S = 1 \Rightarrow Y = D1$

Logic: Truth Table; K-Map

S	D1	D0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

D1D0	S=0	S=1
00		
01		
11		
10		

Y

Logic: Truth Table; K-Map

S	D1	D0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

D1D0	S=0	S=1
	0	0
00	0	0
01	1	0
11	1	1
10	0	1


Y

Simplified logic equation

		Y	
		S=0	S=1
D1D0	00	0	0
	01	1	0
	11	1	1
	10	0	1

$$Y = D0 \bar{S} + D1 S$$

Logic Diagram

 

$$Y = D0 \bar{S} + D1 S$$

Applications

- Computer Switcher
 - Many PC's to use a single printer
- Security Monitoring System
 - Use many cameras to monitor an area; 1 computer monitor for the security person
- Data Communications
 - Many users transmit to a single line.

A logic circuit can be implemented with:

Basic logic gates (AND, OR, NOT)

NAND gates (universal gate)

NOR gates (universal gate)

Decoders

and ... Multiplexers


A MULTIPLEXER CAN IMPLEMENT LOGIC FUNCTIONS

Demultiplexer (DMUX)

Demultiplexer

- Is an electronic switch that routes incoming data signals to one of several lines.

Demultiplexer: Block Diagram

 


Data input = 1

Select lines = address lines = n

Output lines = 2^n

Demultiplexer: Block Diagram

 


Data input = 1

Select lines = address lines = n

Output lines = 2^n

Demultiplexer: Block Diagram

 

Data input = 1

Select lines = address lines = n

Output lines = 2^n

Design a 1-2 demultiplexer


Input = 1

Outputs = 2

Design a 1-2 demultiplexer

Input = 1

Outputs = 2

 


Therefore we need $n = 1$ select line.

Truth Table

D	S	Y0	Y1
D	0	D	O
D	1	0	D

Logic Equations


D	S	Y0	Y1
D	0	D	0
D	1	0	D

 

$$Y0 = \bar{S} D$$

$$Y1 = S D$$


Logic Diagram

 

$$Y0 = \bar{S} D$$

$$Y1 = S D$$

Logic Diagram

 


Application; Data Routing

From a digital computer route data to all electronic devices:

- Plotter
- Color Laser Printer
- 3D Printer
- Monitor
- Sensors

(next ALU design)

 

DESIGN: 1-BIT ALU

1-bit ALU

Design: 1-bit ALU, to perform the following logical and arithmetic operations:

$a \text{ AND } b$
 $\text{NOT } b$
 $a + b$
 $a - b$

Just an academic ALU


1-bit ALU

Design: 1-bit ALU, to perform the following logical and arithmetic operations:

$a \text{ AND } b$
 $\text{NOT } b$
 $a + b$
 $a - b$


How many inputs ... how many outputs ?

(?)-inputs; (?)-output

 


$a \text{ AND } b$
 $\text{NOT } b$
 $a + b$
 $a - b$

a AND b

 

$a \text{ AND } b$
 $\text{NOT } b$
 $a + b$
 $a - b$


NOT b

 

$a \text{ AND } b$
 $\text{NOT } b$
 $a + b$
 $a - b$


$$a + b \quad (C_{in} = 0)$$

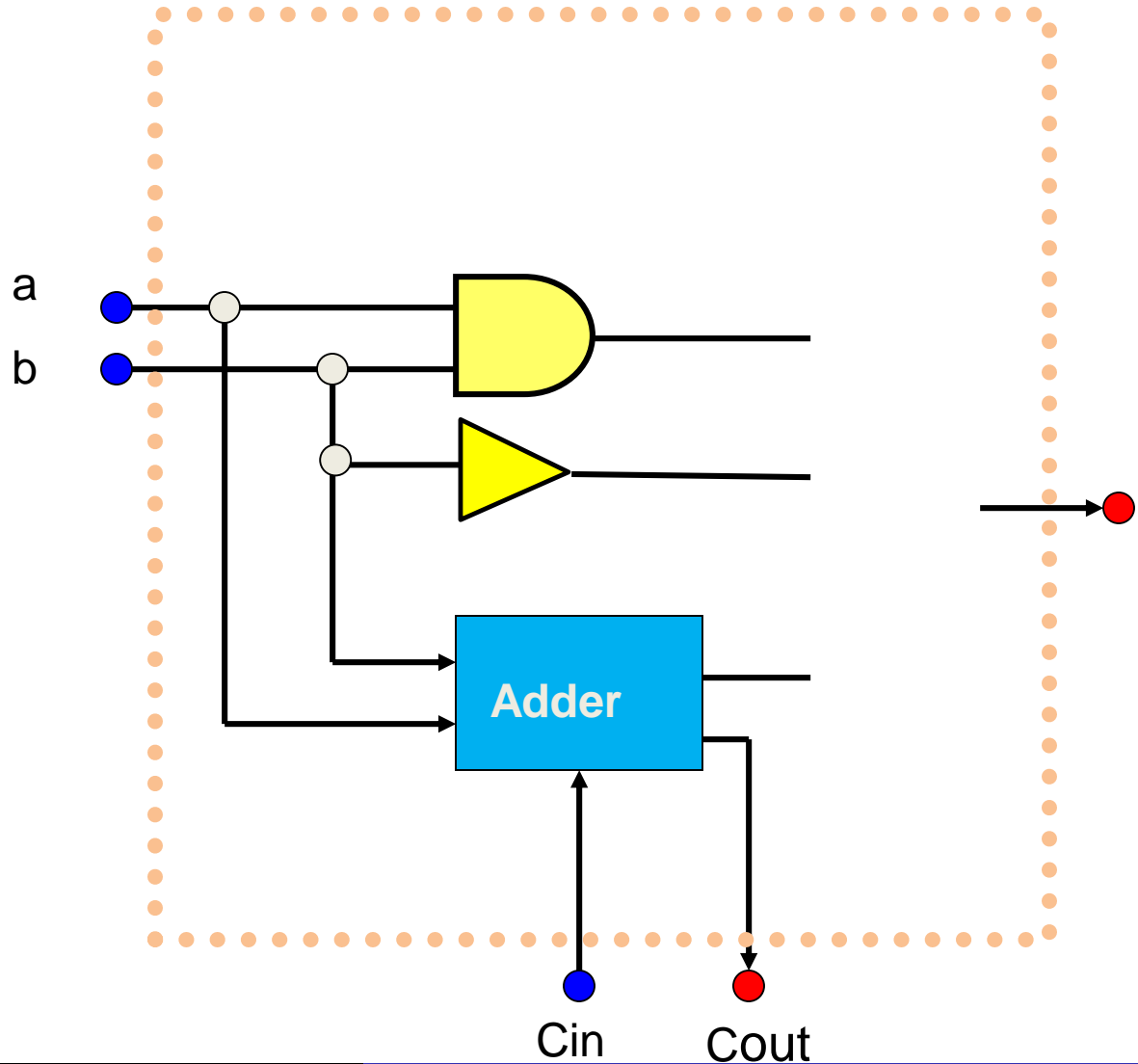$a \text{ AND } b$
 $\text{NOT } b$
 $a + b$
 $a - b$




a-b ($C_{in} = 1$)

a AND b
NOT b
a + b
a - b

 

... and a

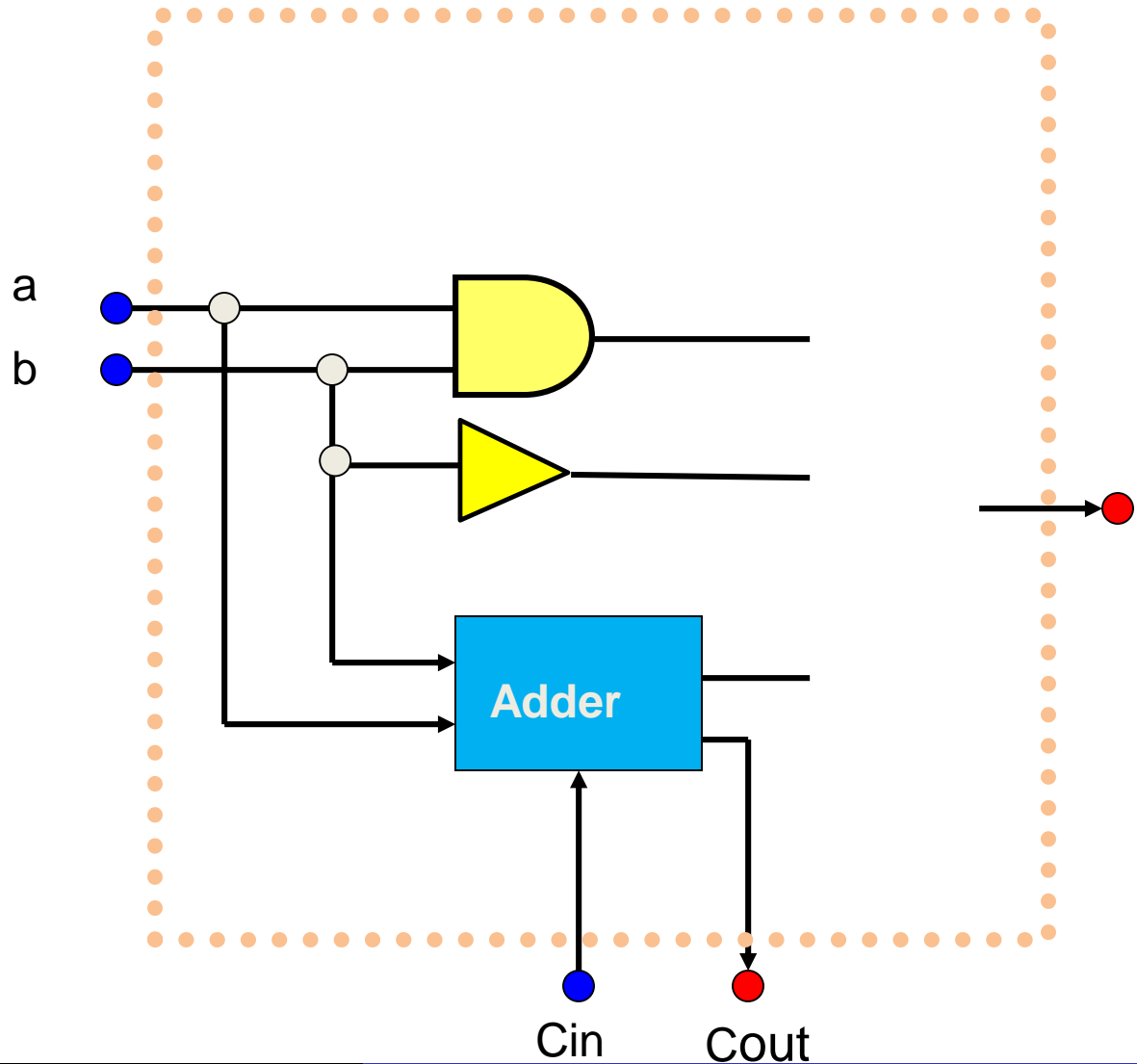
$a \text{ AND } b$
 $\text{NOT } b$
 $a + b$
 $a - b$



... and a 4-1 MUX

s_0	s_1	Out
0	0	AND
0	1	NOT
1	0	Add & Sub
1	1	x


a AND b
NOT b
 $a + b$
 $a - b$

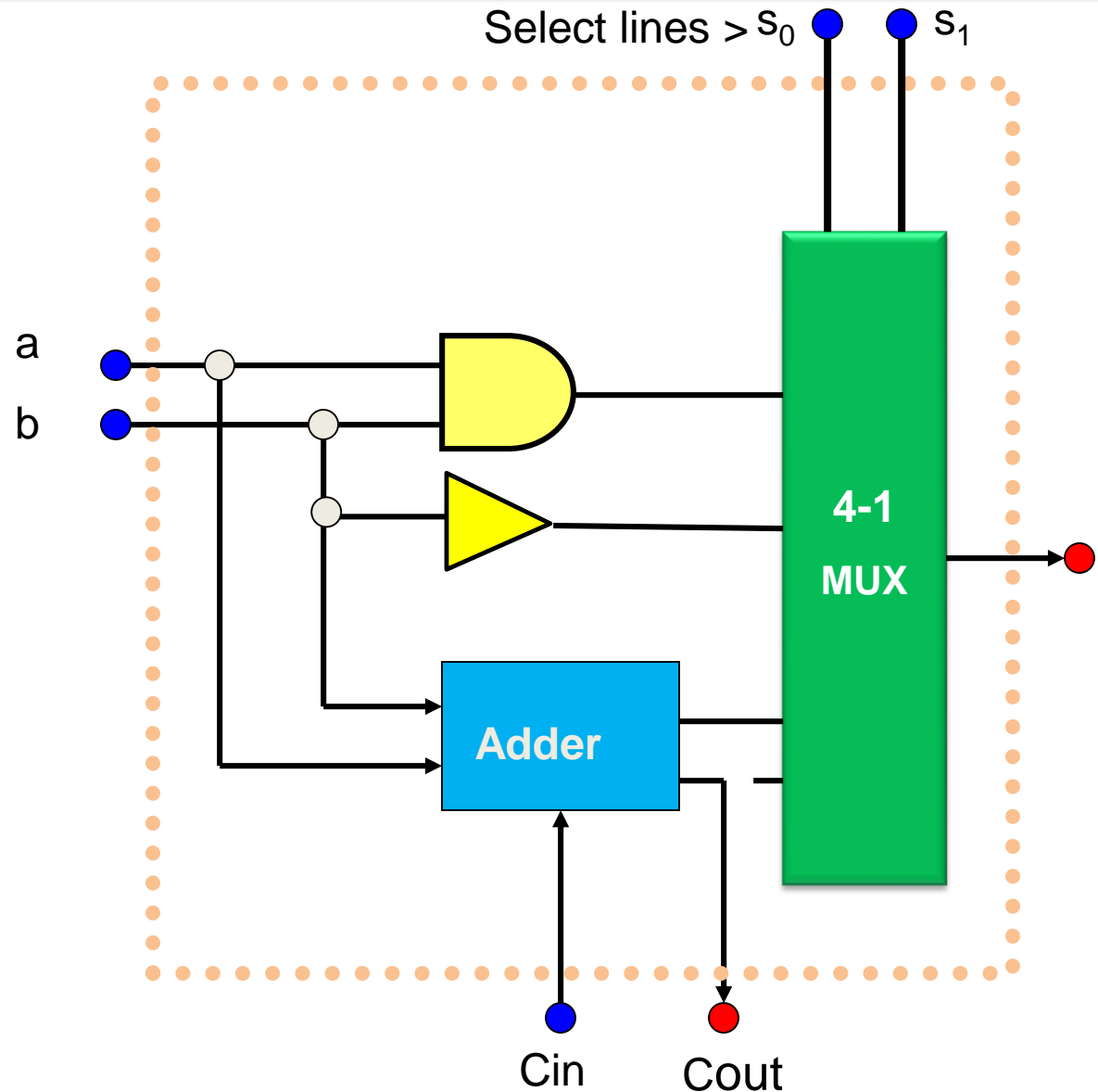


Therefore

s_0	s_1	Out
0	0	AND
0	1	NOT
1	0	Add & Sub
1	1	x

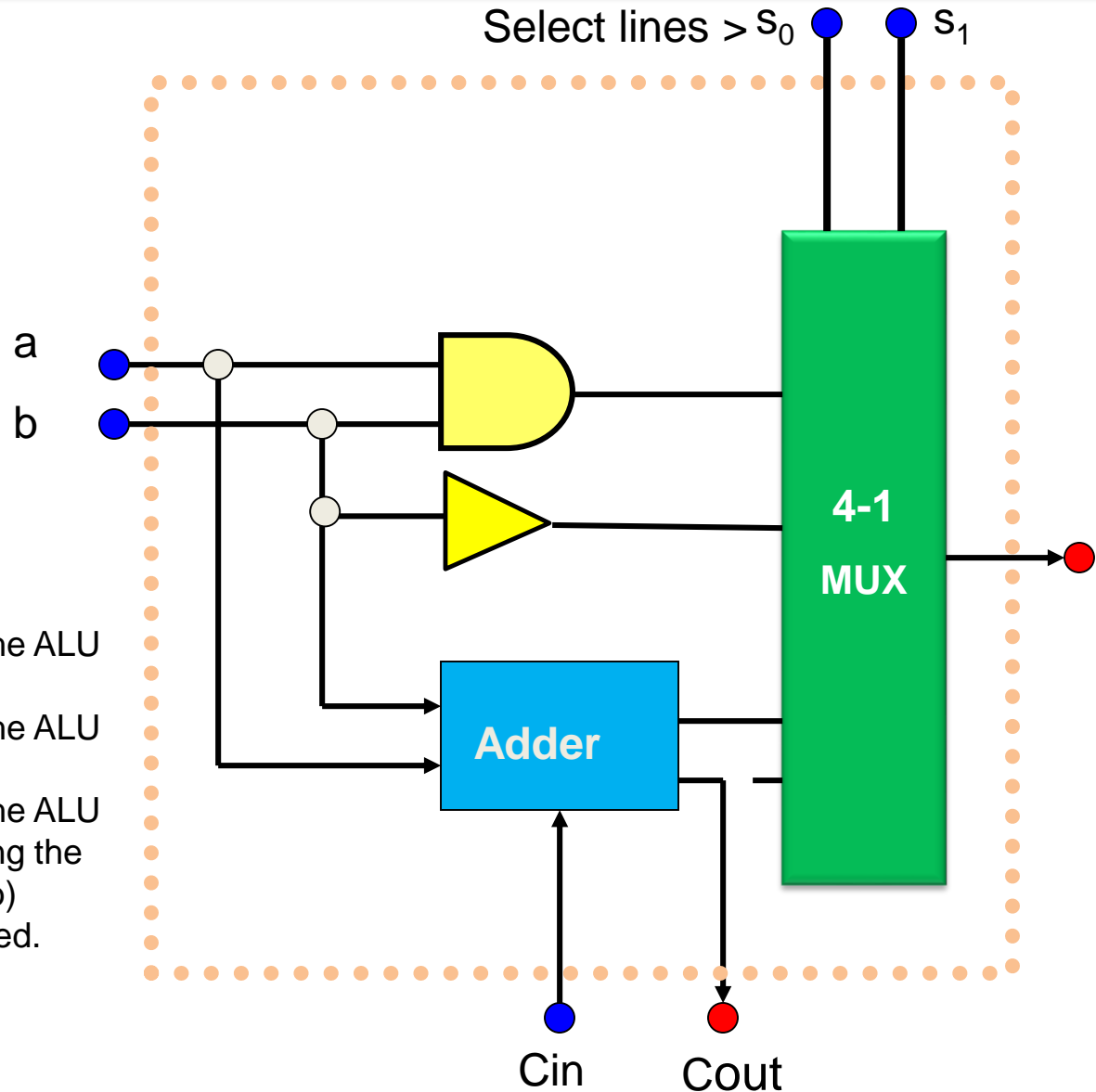
- If the select lines are: (00), the ALU will perform: ADD
- If the select lines are: (01), the ALU will perform: NOT
- If the select lines are: (10), the ALU will perform: Add & Sub (using the Cin, 0 and 1 for Add and Sub)
- The select state (11) is unused.




1-bit ALU

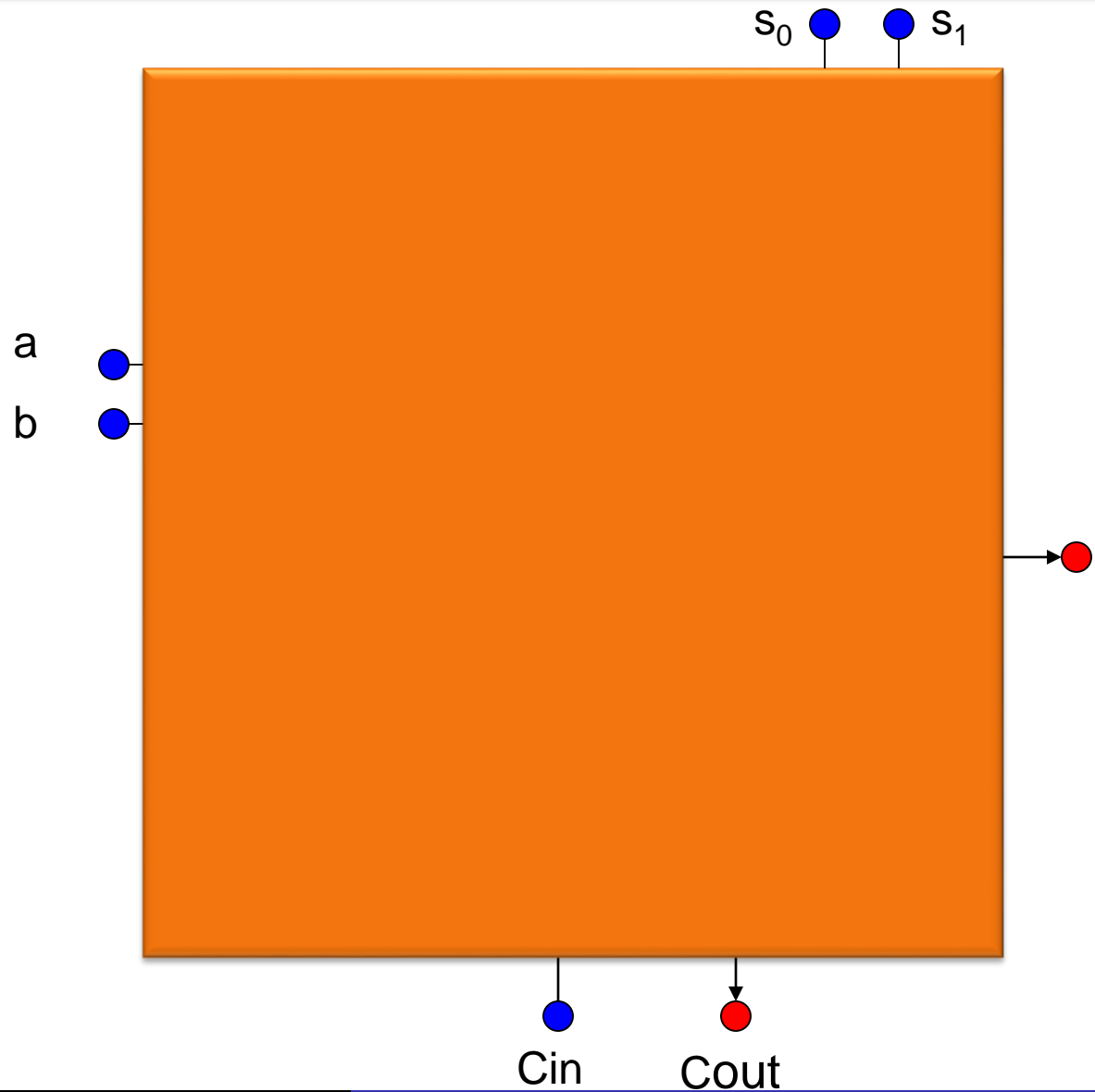

1-bit ALU

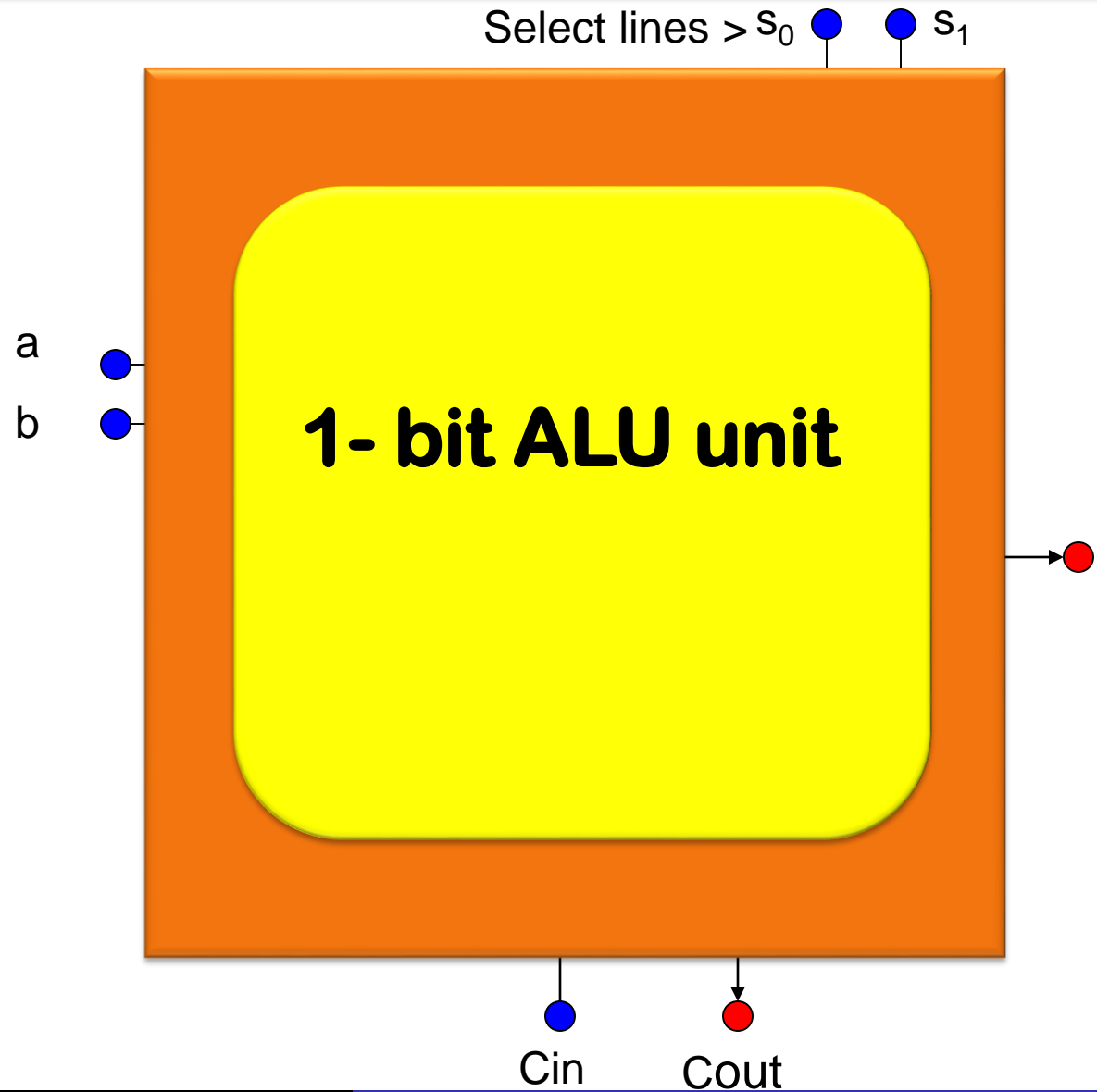


74181 ALU

 


<http://www.righto.com/2017/01/die-photos-and-reverse-engineering.html>

74181 ALU die

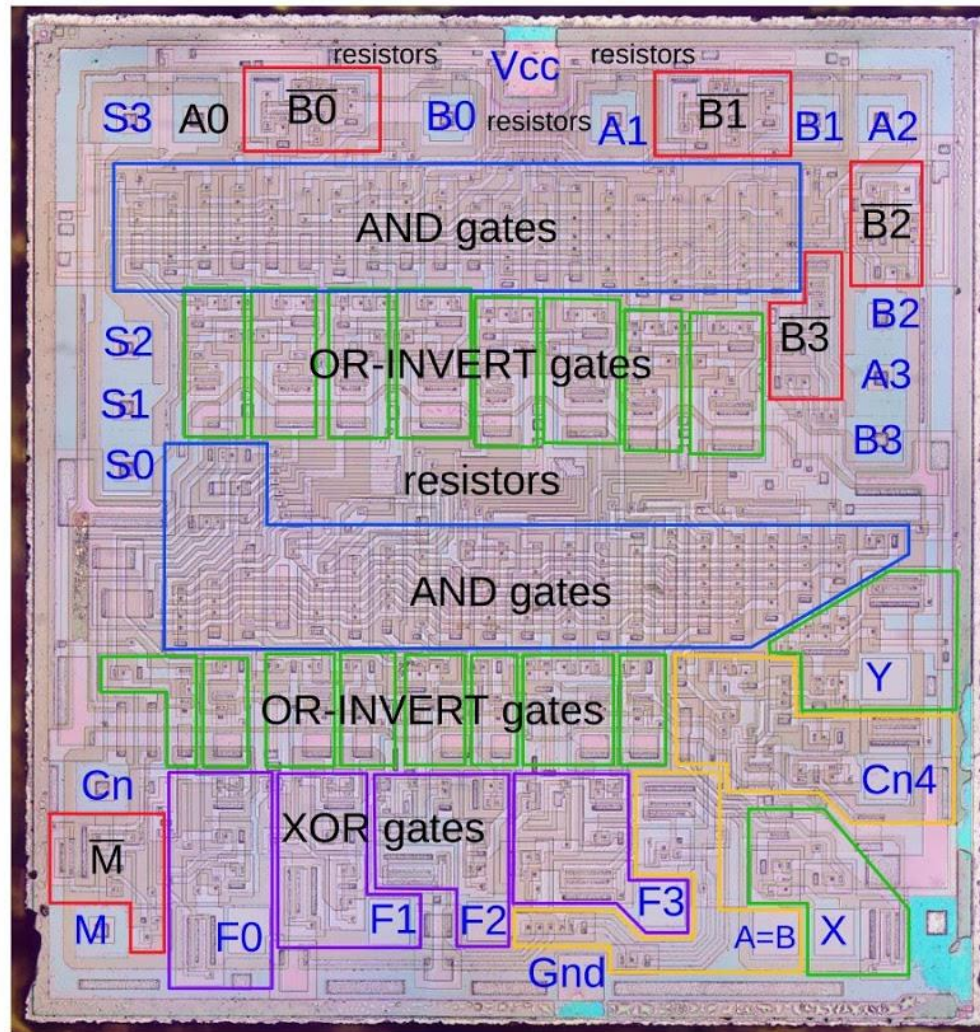


INTEL 8008 8-bit CPU

 


http://www.righto.com/2016/12/die-photos-and-analysis-of_24.html


ALU

 

VHDL ... 1-bit ALU;

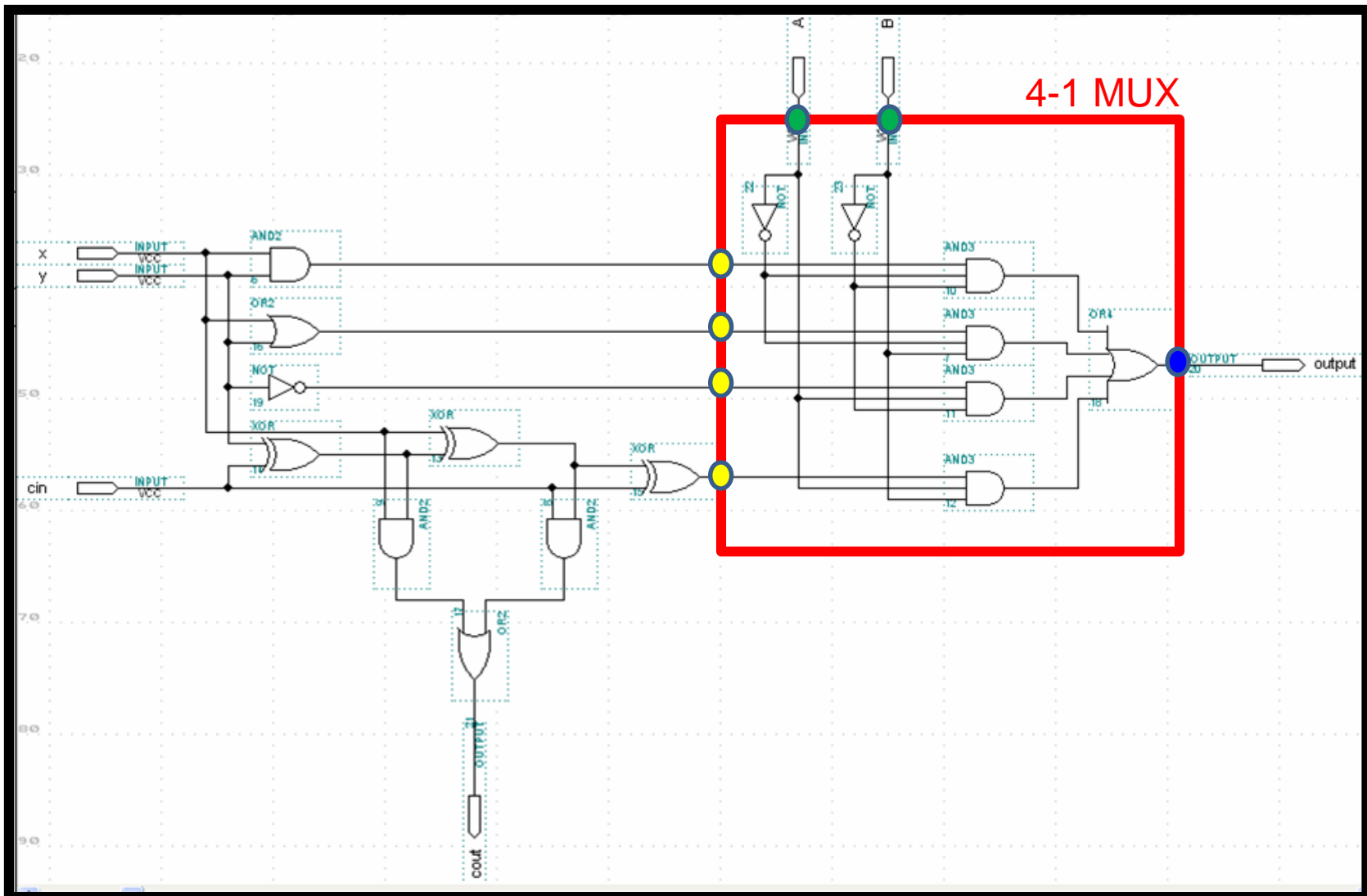


Timing

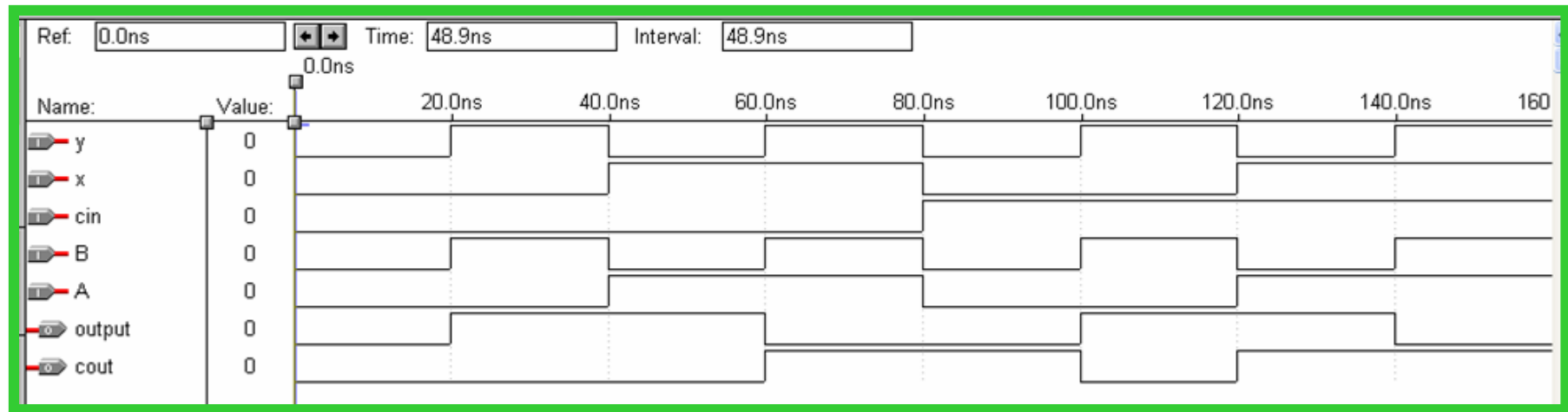

VHDL code

```
ENTITY aluvhdl IS
    PORT ( x, y, A, B, cin : IN BIT ;
          cout, output : OUT BIT ) ;
END aluvhdl ;

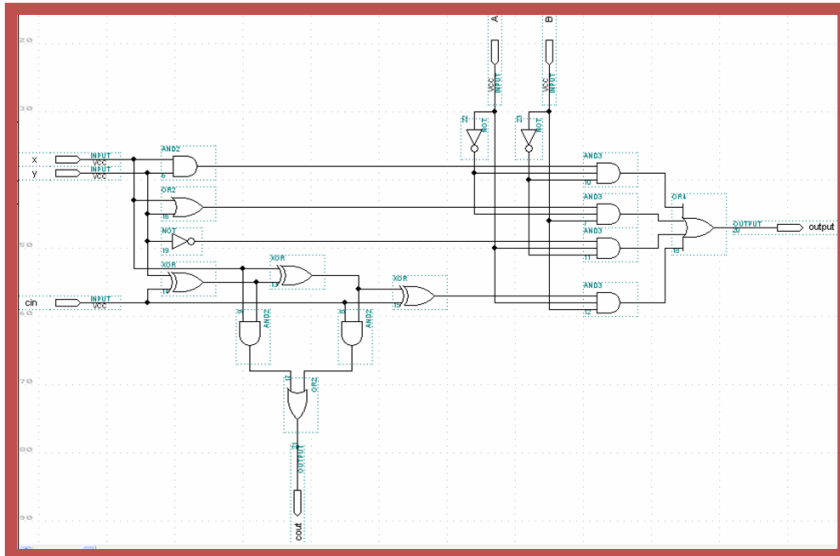ARCHITECTURE LogicFunc OF aluvhdl IS
BEGIN
    cout <= (x AND (y XOR cin)) OR (cin AND (x XOR (y XOR cin))) ;
    output <= (x AND y AND (NOT A) AND (NOT B)) OR ((x OR y) AND (NOT A) AND B) OR ((NOT y) AND A AND (NOT B))
              OR (A AND B AND (cin XOR (x XOR (y XOR cin)))) ;
END LogicFunc ;
```



... are the same

