

Binary Subtractor

(Multiplier)

Binary Subtractor: Principle

$$A - B = ?$$



Binary Subtractor: Principle

$$A - B = A + 2's \text{ comp. of } B$$



Minus



Adder


Read the Lecture about complements

Binary Subtractor: Principle

$$\begin{aligned} A - B &= A + 2's \text{ comp. of } B \\ &= A + \{ (1's \text{ comp. of } B) + 1 \} \end{aligned}$$



Adder



Add

Read the Lecture about complements

Binary Subtractor: 2's

$$A - B = A + \{ (\text{1's comp. of } B) + 1 \}$$

Therefore,


- 1's complement can be implemented with an Inverter.
- The +1 can be implemented by adding 1, or making the Carry-in equal to 1.

4-Bit Subtractor


4-bit binary subtraction: $A - B$

4-bit Binary Subtractor

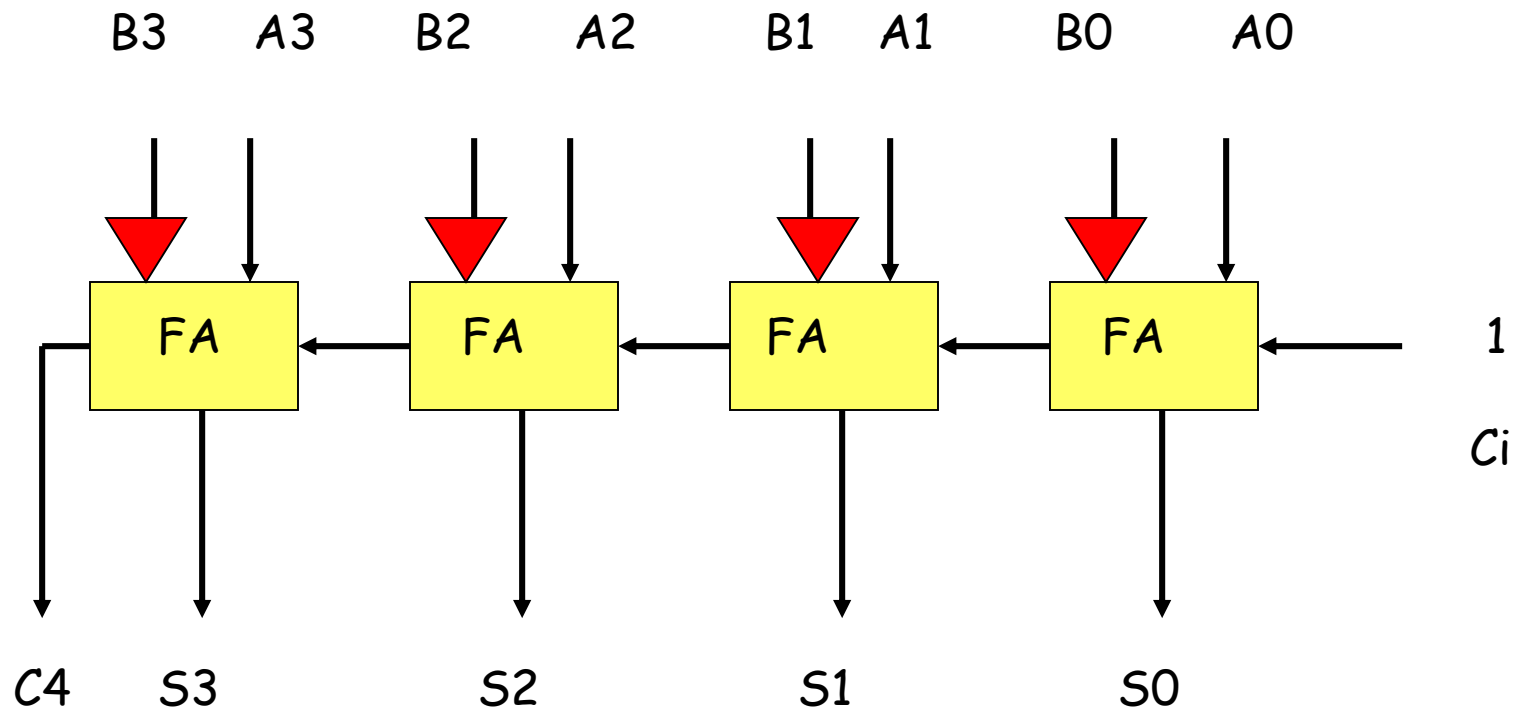
$$A - B = A + \{ (1's \text{ comp. of } B) + 1 \}$$




If $C4 = 1$; $S3S2S1S0$

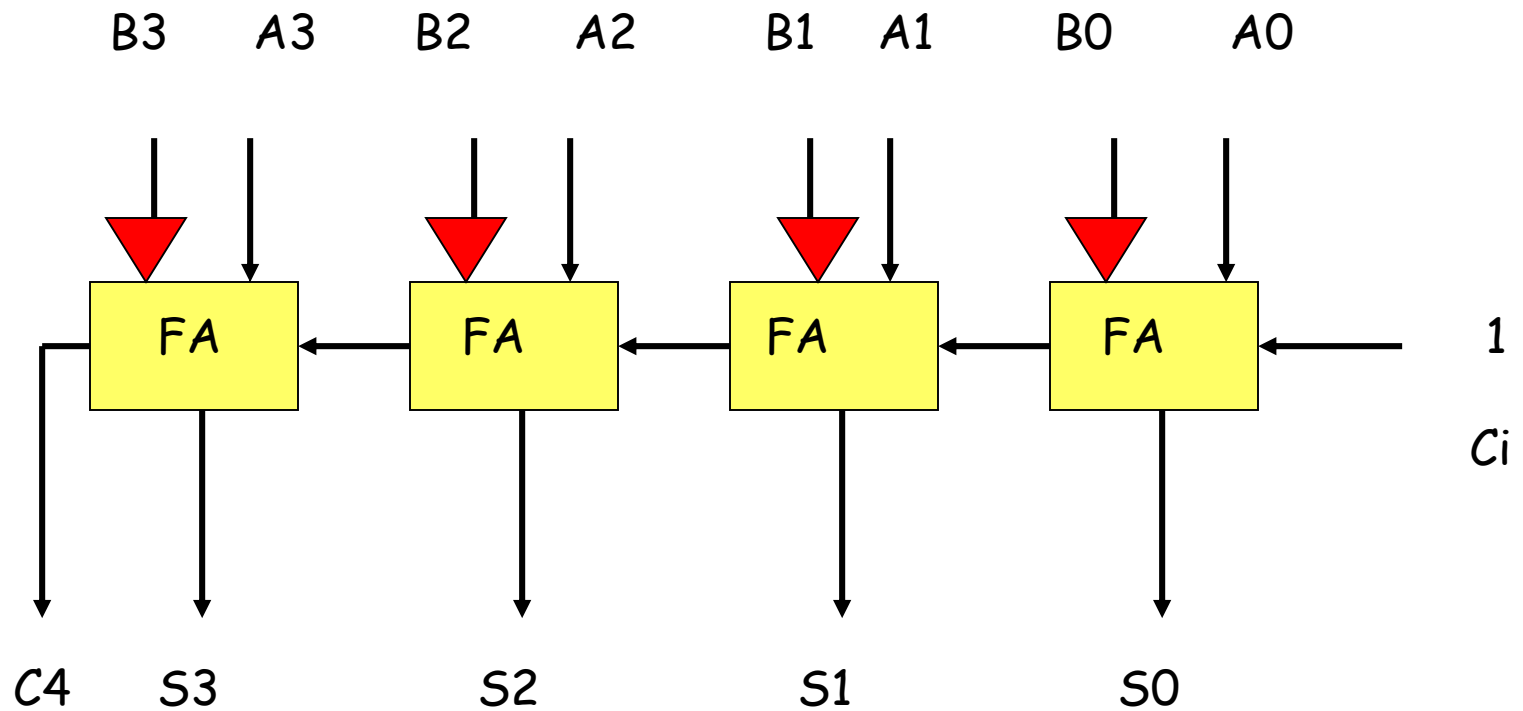


Numerical example-1: 7 (0111) – 3 (0011)

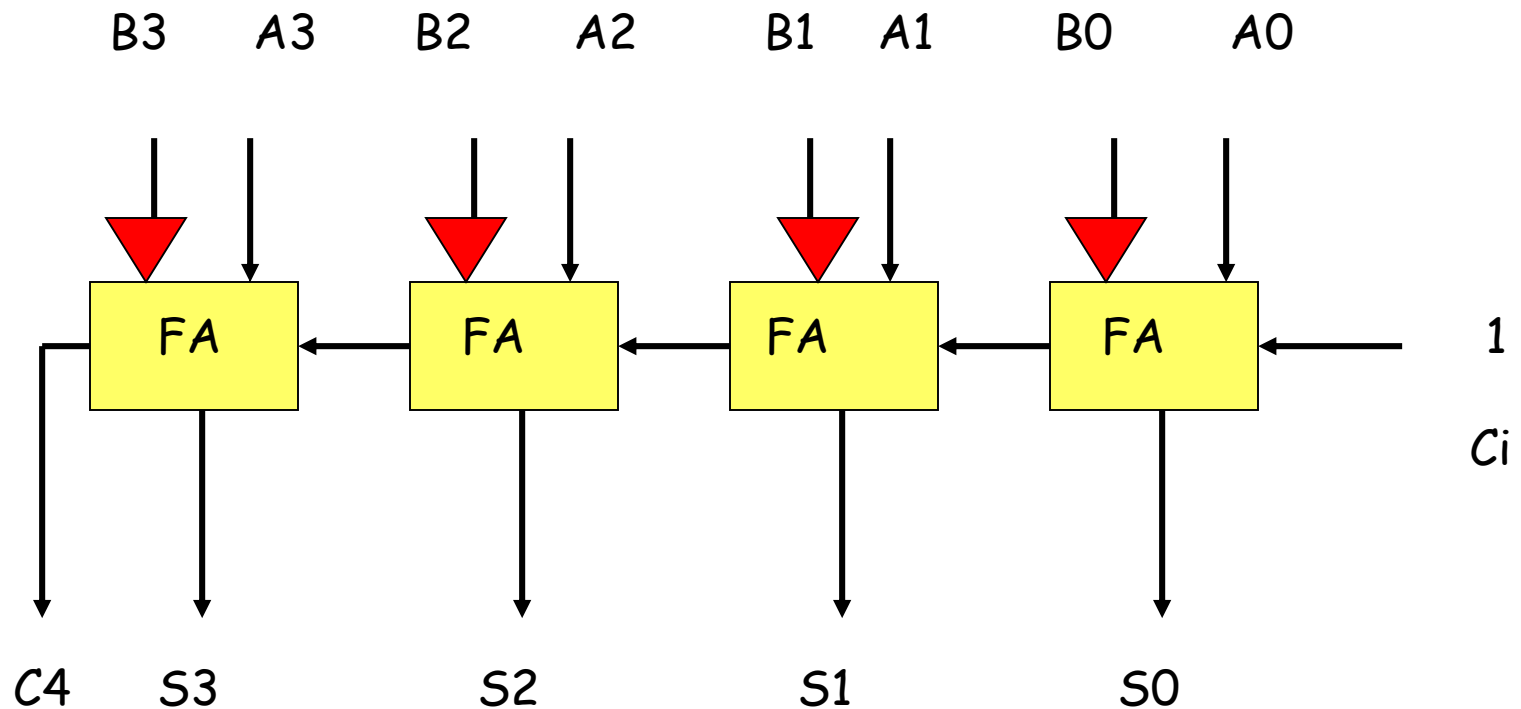


Numerical example-1: 7 (0111) – 3 (0011)

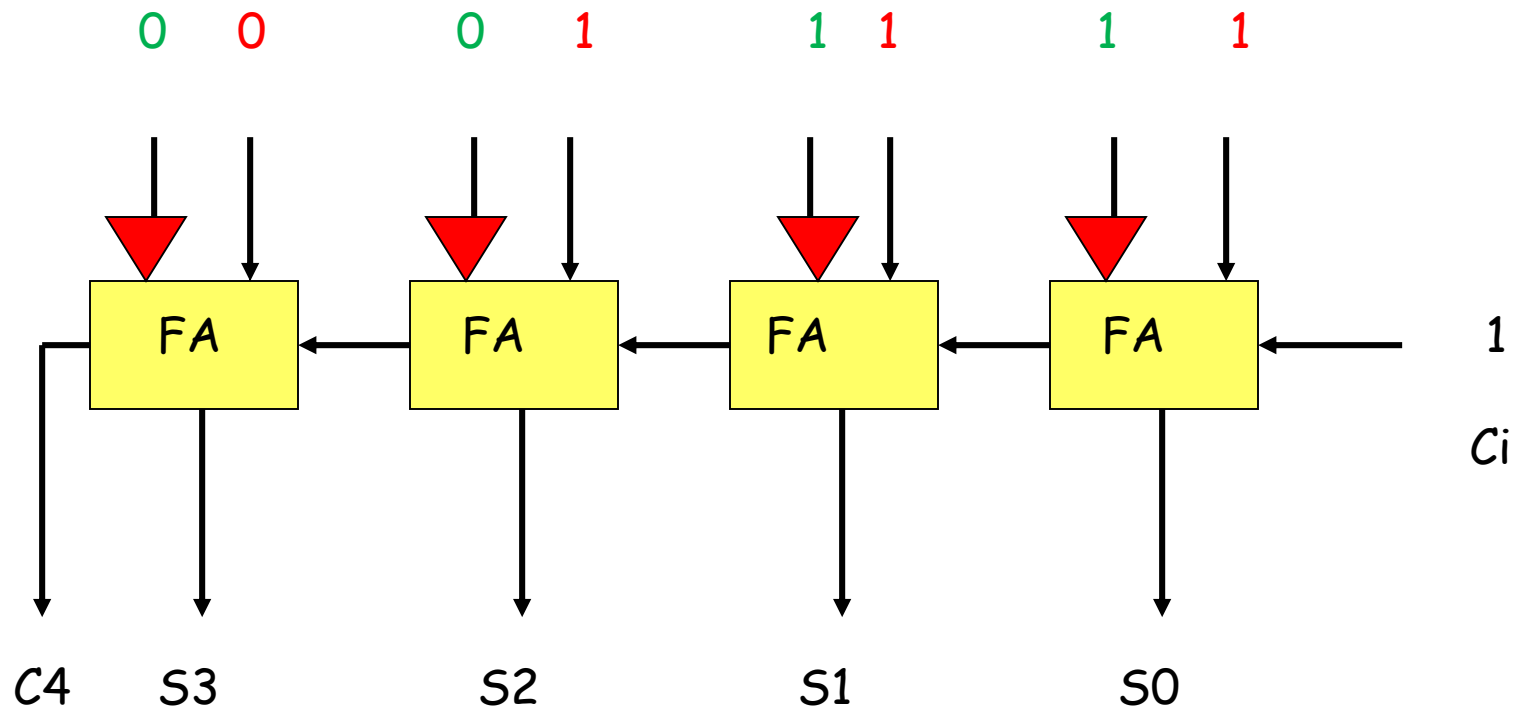


Numerical example-1: 7 (0111) – 3 (0011)

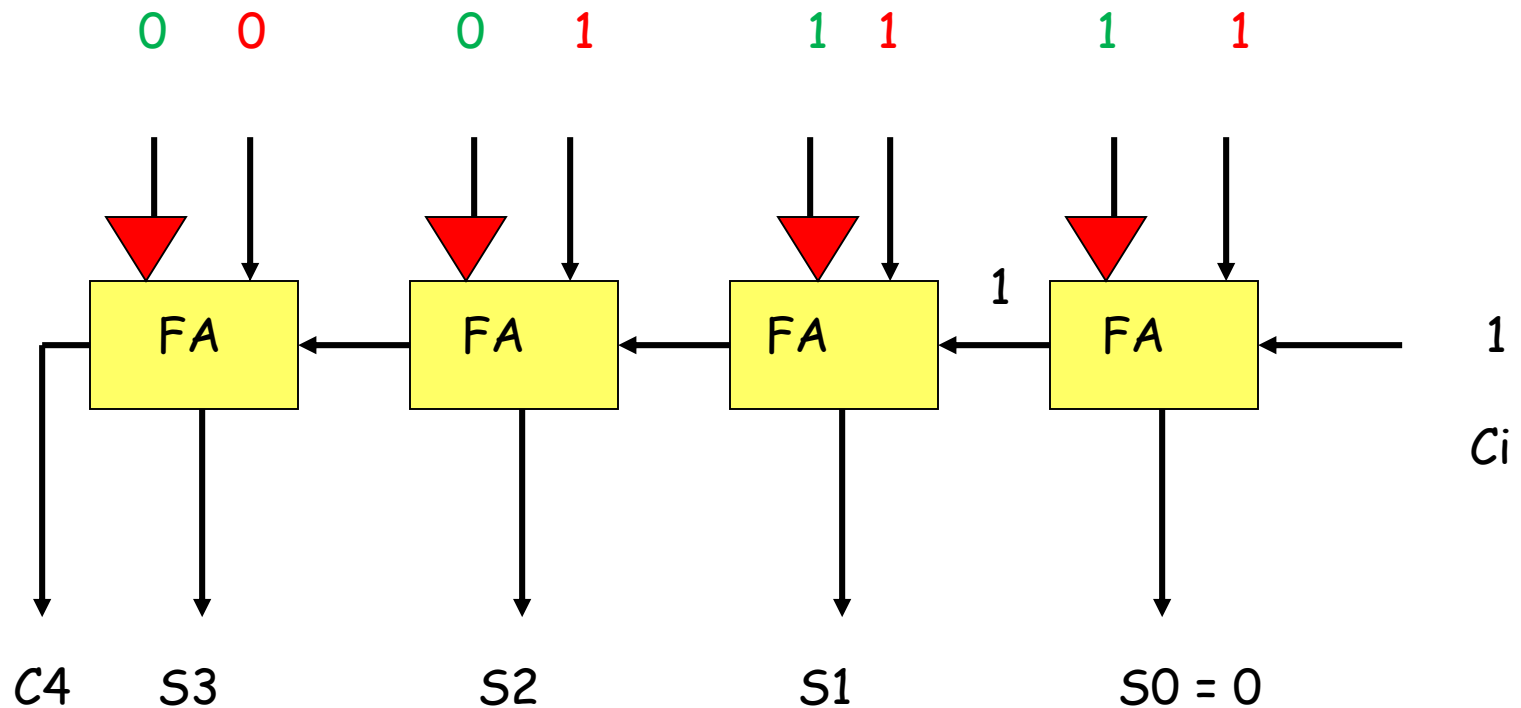


Numerical example-1: 7 (0111) – 3 (0011)

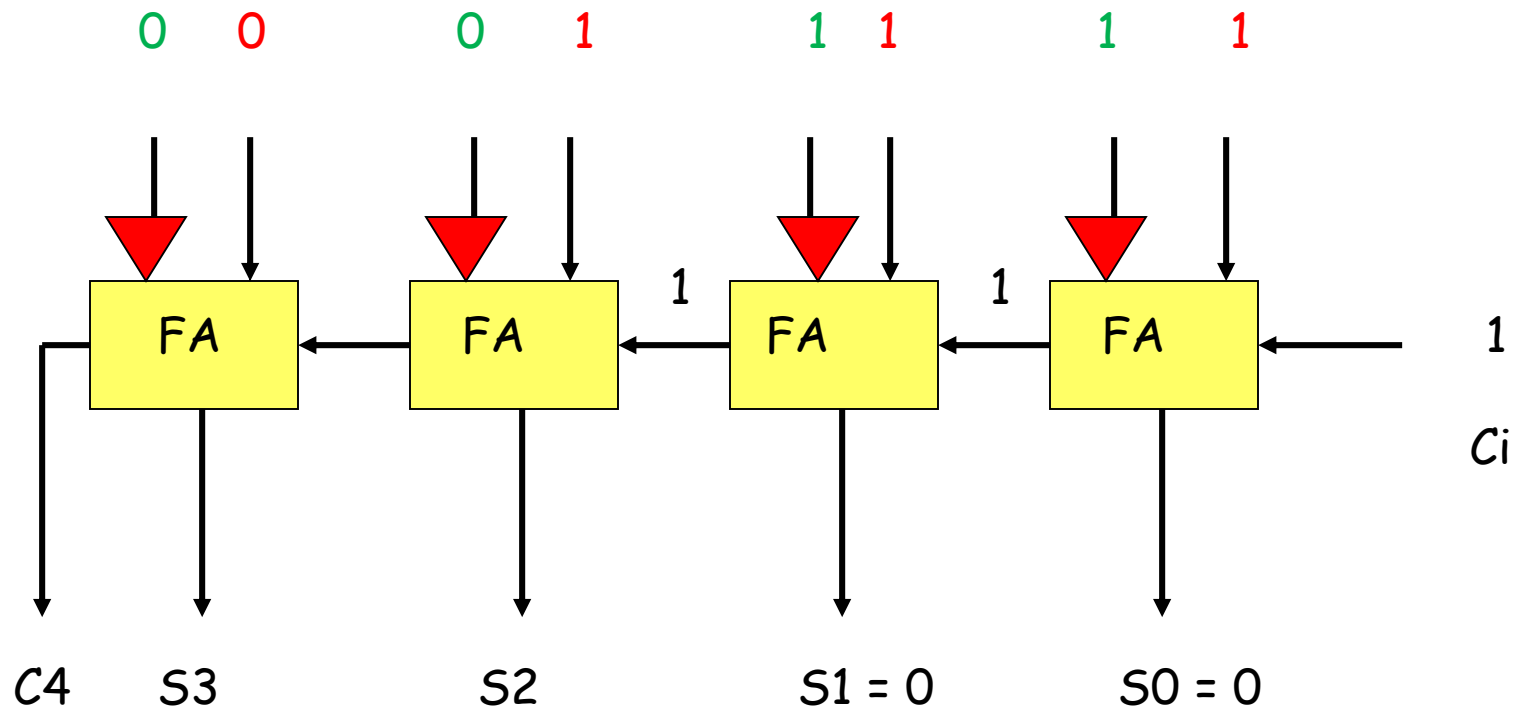

Numerical example-1: 7 (0111) – 3 (0011)

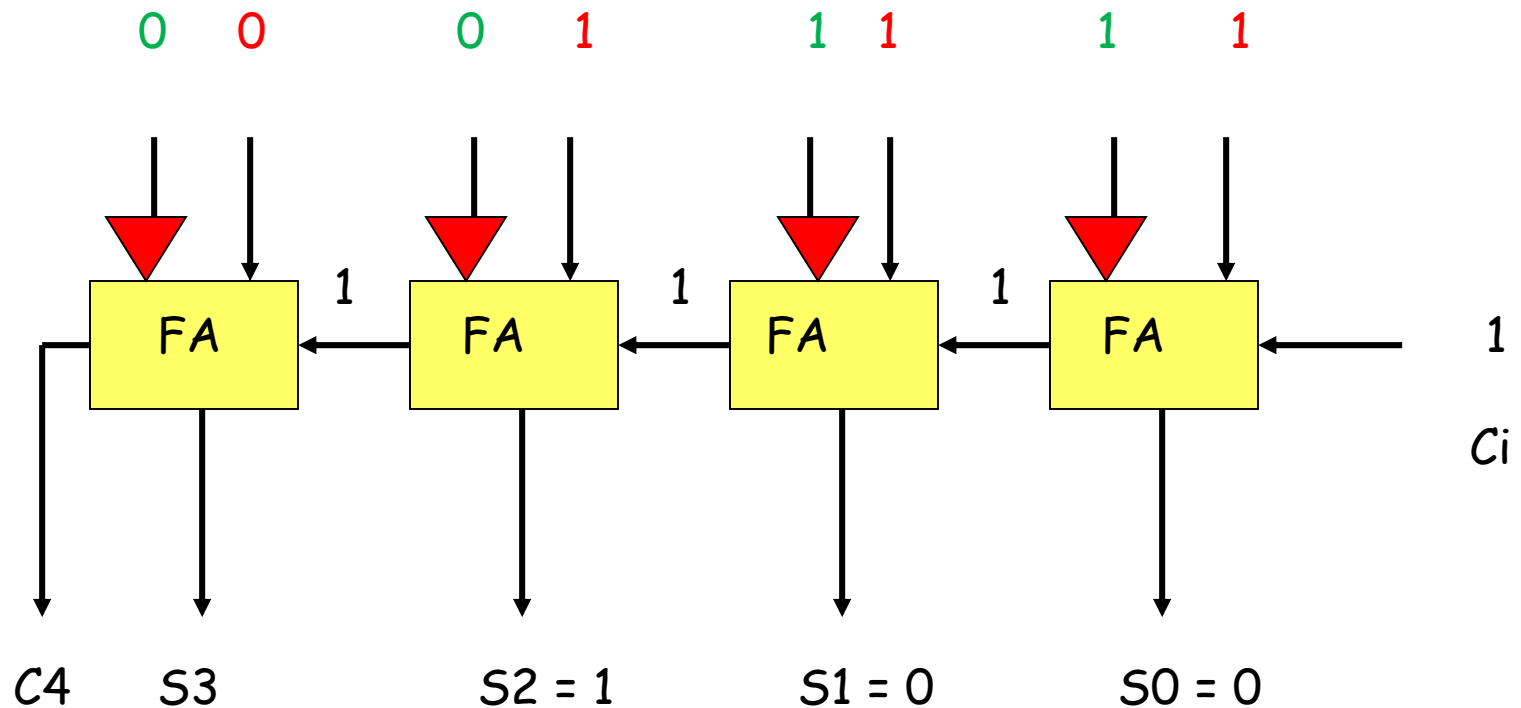

Numerical example-1: 7 (0111) – 3 (0011)

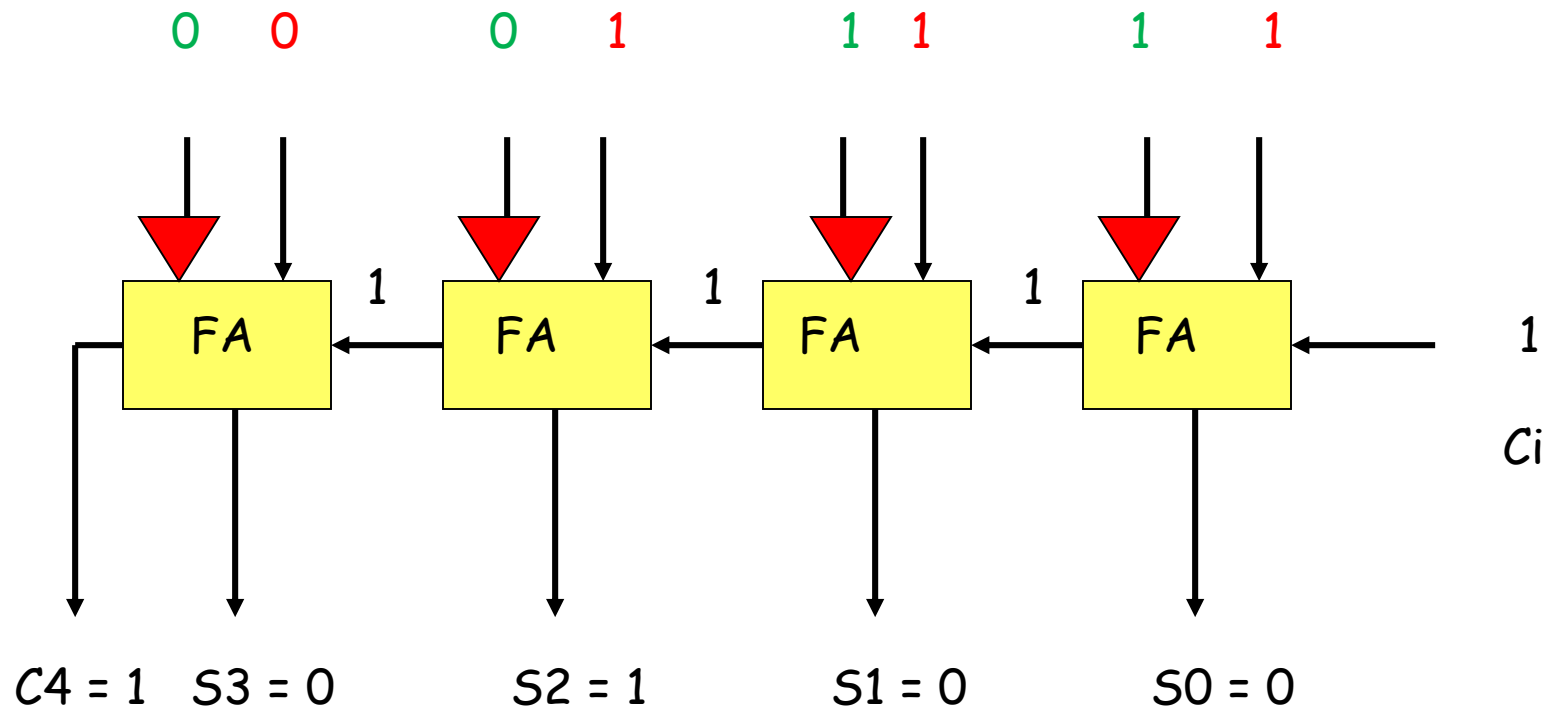

Answer = $0100_2 = 4_{10}$

Remember !

0111

+1101

10100




Discard carry

Numerical Example-2

- $3 - 7 = ?$

Numerical example-1: 3 (0011) – 7 (0111)

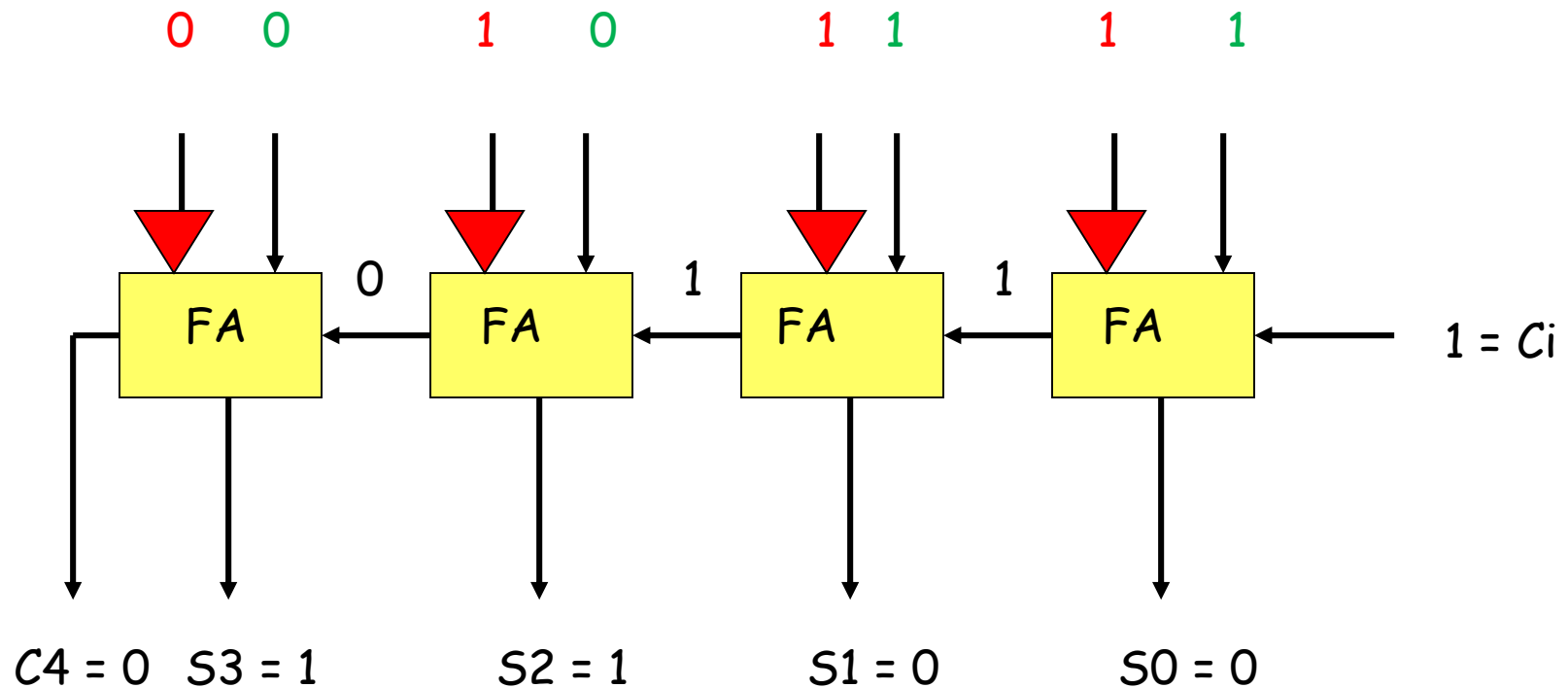

Answer = 1100_2

3 (0011) – 7 (0111)

- In our example, the result of the 2's complement binary subtraction is in 2's complement form: $(1100)_2$
- $(0011 + 1)_2 = (0100)_2 = 4_{10}$
- Since there is no carry out, the final result: -4_{10}

Why do we prefer 2's complement?


- For subtraction, the 2's complement is used over the 1's complement
- 2's complement magnitude representation has only one zero for representing negative numbers and it is used in today's computing technology.

4-bit (2's Complement uses **one zero**)

Decimal	S.Mag	1's Mag.	2's Mag.
7	0111	0111	0111
6	0110	0110	0110
5	0101	0101	0101
4	0100	0100	0100
3	0011	0011	0011
2	0010	0010	0010
1	0001	0001	0001
0	0000	0000	0000
-0	1000	1111	—
-1	1001	1110	1111
-2	1010	1101	1110
-3	1011	1100	1101
-4	1100	1011	1100
-5	1101	1010	1011
-6	1110	1001	1010
-7	1111	1000	1001
-8	—	—	1000

Combined (Subtractor/Adder)

Combined (Subtractor/Adder)

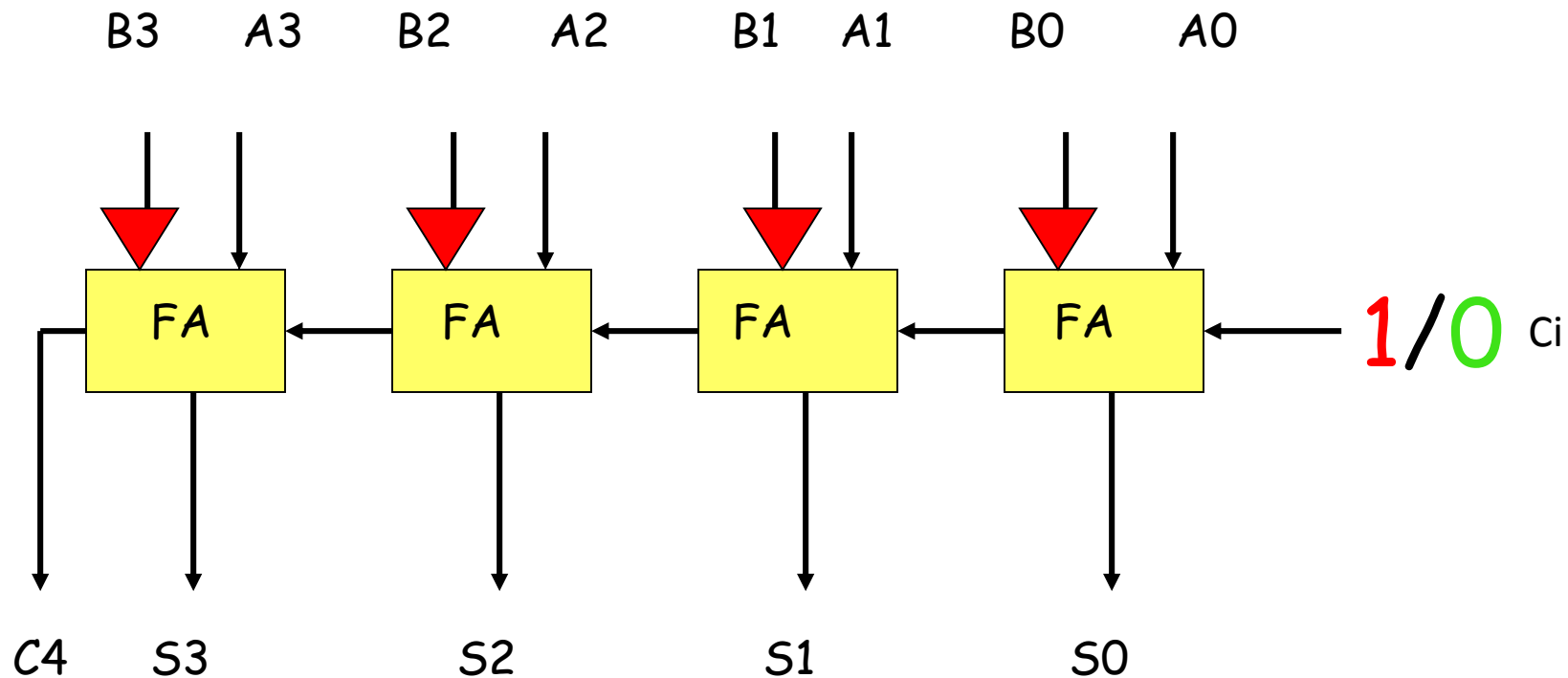

A trick with the input: B_i ($i = 0, \dots, n$)

$$B_i \oplus 1 = ?$$

$$B_i \oplus 0 = ?$$

 \oplus

Prove it ... 5 min



Logic Circuit?

$$B_i \oplus 1 = \overline{B_i}$$


$$B_i \oplus 0 = B_i$$

\oplus

Just a XOR gate


$$Bi \oplus 1 = \bar{Bi}$$

$$Bi \oplus 0 = Bi$$

 


If 1 (**Subtraction**); then the Bi = Negated as should be
If 0 (**Addition**); then the Bi is the same as should be

Combined 2's(**S**ubtractor/**A**dder)

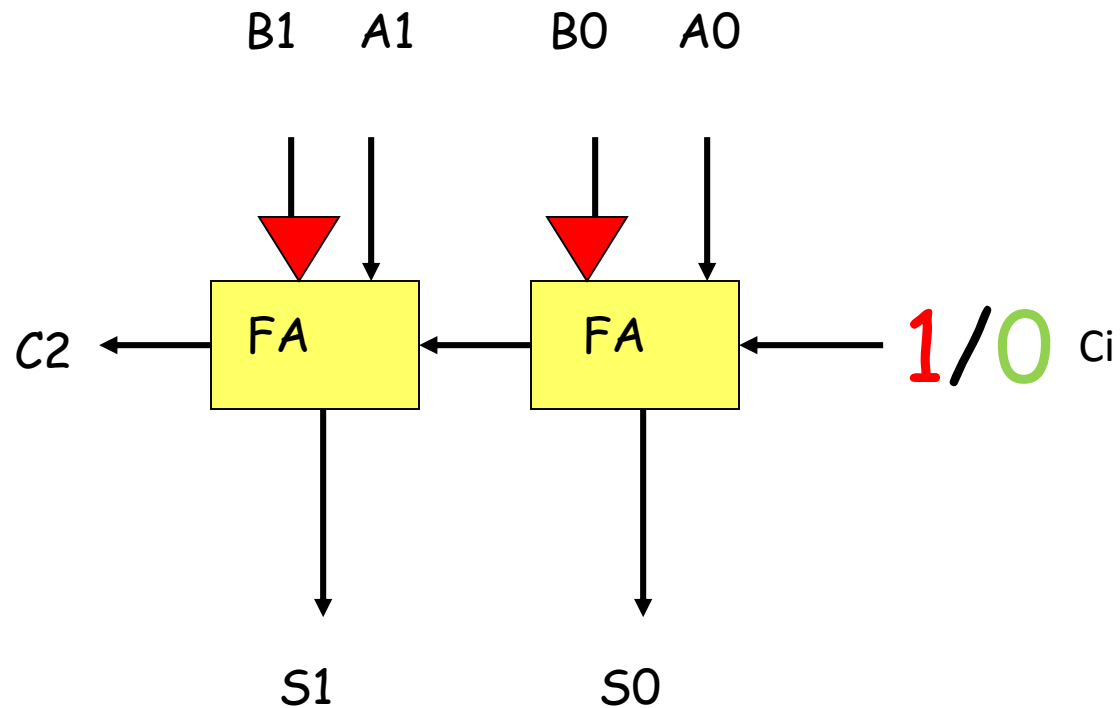


Combined 2's(Subtractor/Adder)

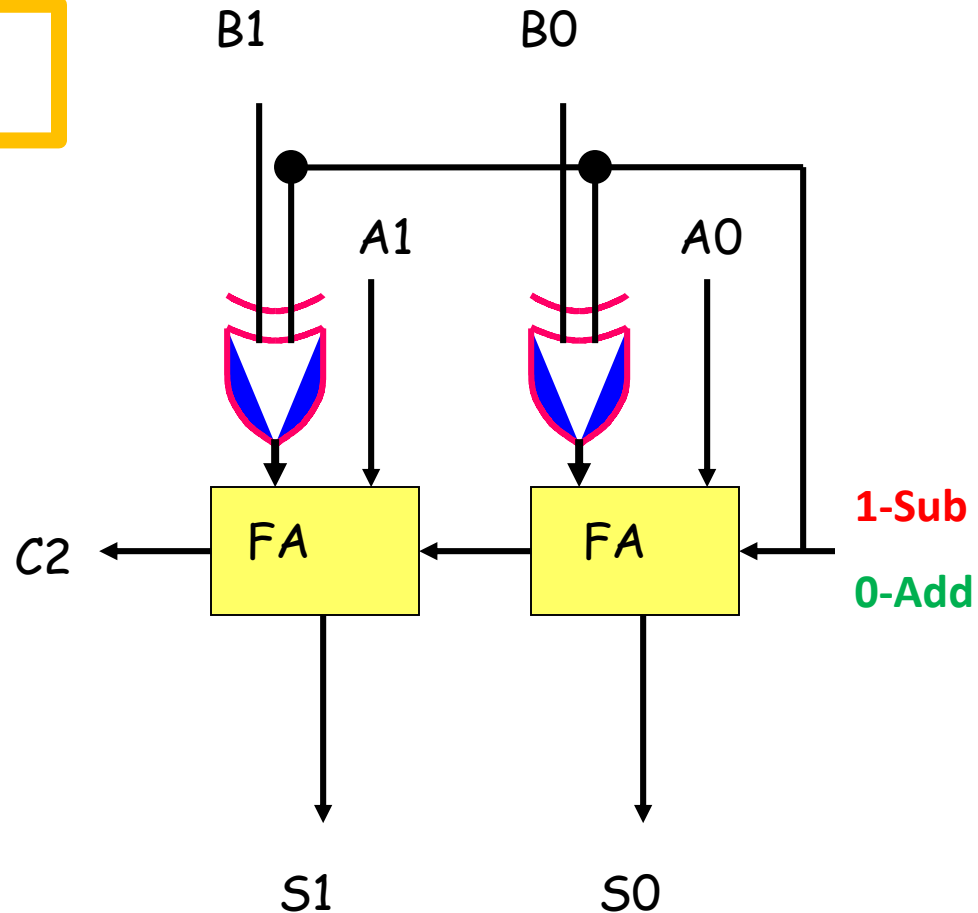
Carry input (C_i) = 1; for subtraction
Carry input (C_i) = 0, for addition




Live proof! (LogiSim freeware)

 

Combined 2's(Subtractor/Adder)

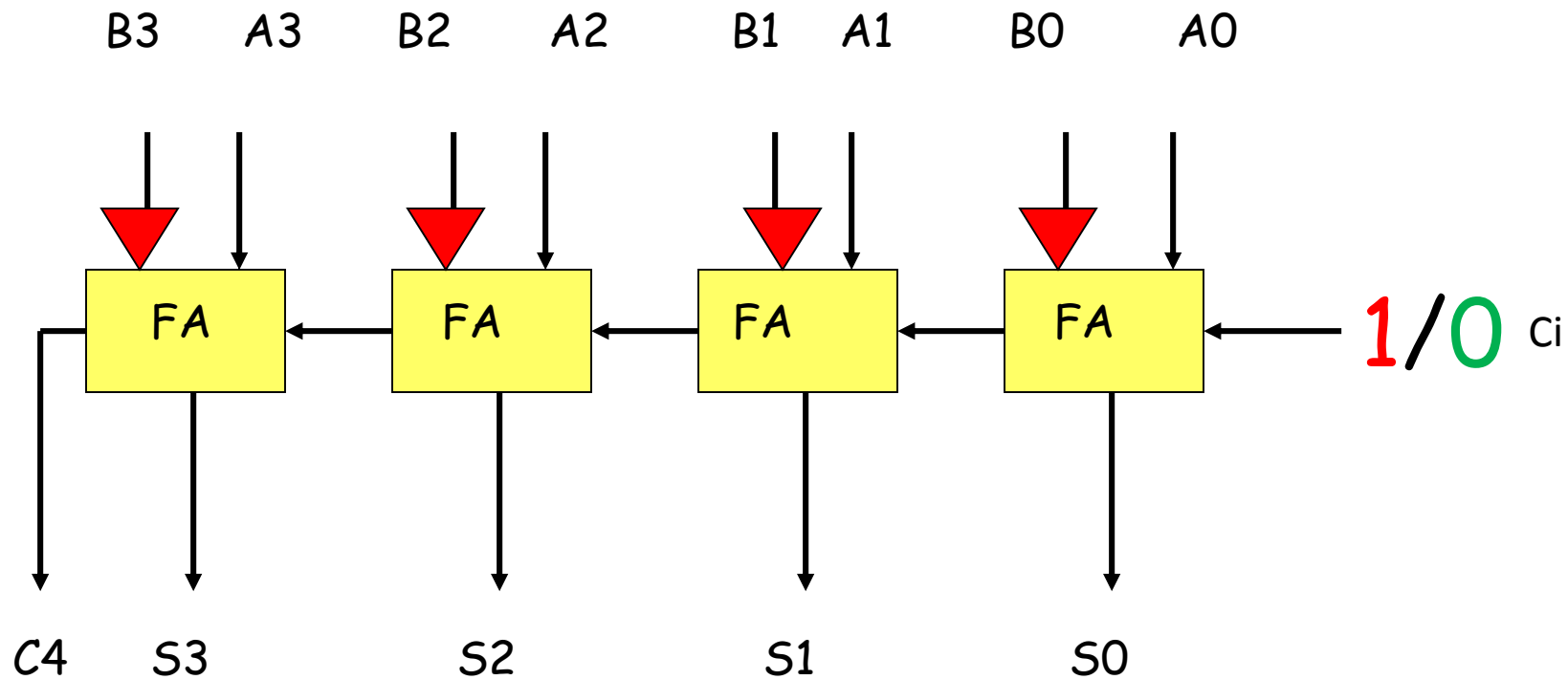

Combined 2's(Subtractor/Adder)

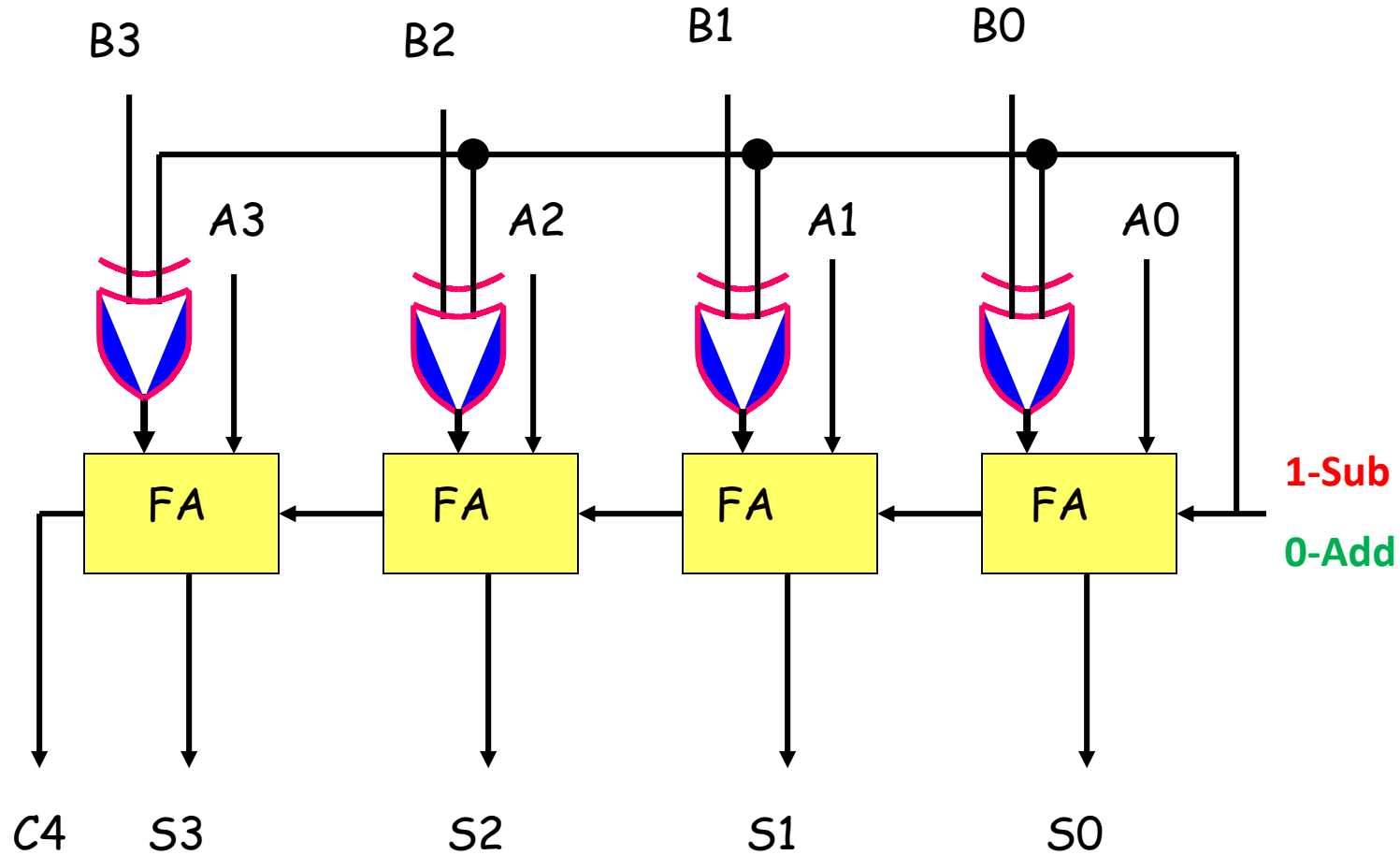

Design a 2-bit Multiplier

$$\begin{array}{r} B_1 B_0 \\ x A_1 A_0 \\ \hline \end{array}$$

2-bit Multiplication

$$\begin{array}{r} B_1 B_0 \\ A_1 A_0 \\ \hline A_0 B_1 A_0 B_0 \\ A_1 B_1 A_1 B_0 \\ \hline C_3 C_2 C_0 \end{array}$$

$$C_0 = A_0 B_0$$

$$C_1 = A_1 B_0 + A_0 B_1 \text{ (carry)}$$

$$C_2 = A_1 B_1 \text{ (carry)}$$

$$C_3 = \text{carry}$$


Design a 2-bit Multiplier using Adders and gates

2-bit Multiplier using: Adders+Gates

$$\begin{array}{r} B_1 \quad B_0 \\ A_1 \quad A_0 \\ \hline A_0B_1 \quad A_0B_0 \\ A_1B_1 \quad A_1B_0 \\ \hline C_3 \quad C_2 \quad C_1 \quad C_0 \end{array}$$

$C_0 = A_0B_0$ [AND gate]
 $C_1 = A_1B_0 + A_0B_1$ (carry) [HALF ADDER] and AND gates
 $C_2 = A_1B_1$ (carry) [HALF ADDER] and AND gate
 $C_3 = \text{carry}$

Only use Half-Adders and AND gates

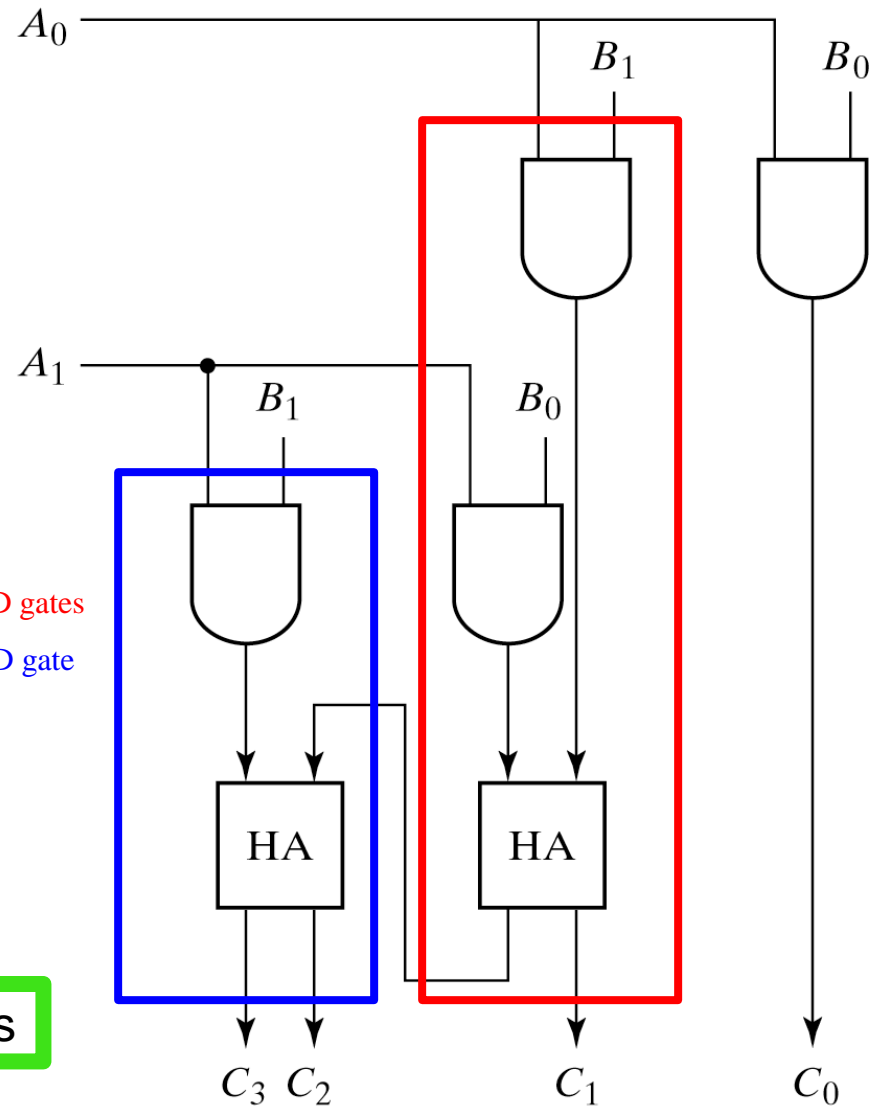

Divider (Division Operation)

Division

- Division is the fourth mathematical operation. The binary division operation consists of multiplications and subtractions. Circuits that perform binary division are more complex than adders. Division and multiplication algorithms is an important subject of computer organization.

<http://www.wikihow.com/Divide-Binary-Numbers>

David Patterson and John L. Hennessy, "Computer Organization and Design: the Hardware/Software Interface", Morgan Kaufmann Publishers, 2017.